

EE 313 –Design Problem Last names between I and P  
Fall 2010  
Due Tuesday, November 23<sup>rd</sup>.  
Accepted without penalty by November 30<sup>th</sup>.

A balanced, three-phase, Y-connected source has a line voltage of 250 Vrms. The source frequency is 60 Hz. The balanced, three-phase loads have the following characteristics:

$Z_{\Delta 1}$ :  $P_1 = 45 \text{ kW}$  and  $Q_1 = +63 \text{ kVAR}$

$Z_{y2}$ :  $4\angle 35^\circ \Omega$

$Z_{\Delta 3}$ :  $\text{PF}_3 = 0.15$  lagging and  $I_{p3} = 100 \text{ A rms}$

$Z_{y4}$ :  $S_4 = 15\angle 50^\circ \text{ kVA}$

1. Determine the phasor value of each impedance and the current for each load.
2. Determine the total line current,  $I_{aA}$ .
3. Determine the total complex power, average power, and reactive power delivered by the source to the loads.
4. What is the power factor of the three loads combined?
5. It is necessary to add a parallel load in the Y configuration to the circuit to reduce the magnitude of the line current by 50%. The line voltage and total average power delivered by the source may not change. What are the impedance and the component value of this load?
6. What is the power factor of the additional load?
7. What is the power factor of the four loads combined?