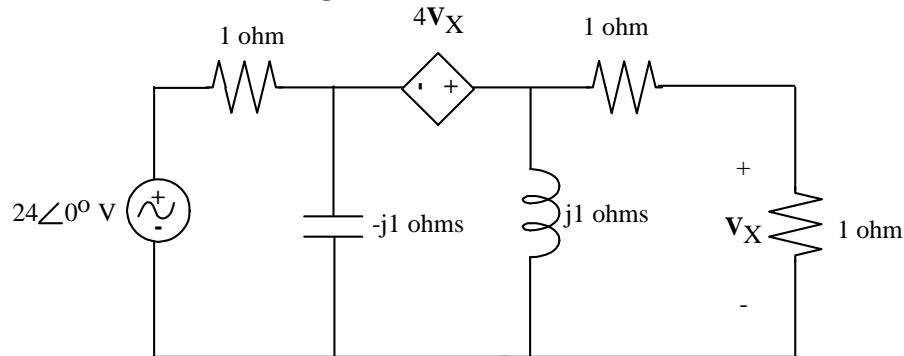


You must show your work to receive credit


1. [2 points] Consider the following circuit:

What is the total complex power delivered by each source?

 $24\angle 0^\circ$ delivers _____ $4V_X$ delivers _____

What is the real power absorbed by the left-most 1 ohm resistor and the j1 ohm inductor?

1 ohm absorbs _____ j1 ohm absorbs _____

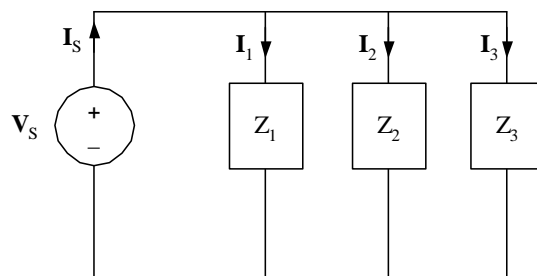2. [3 points] Consider the following single phase circuit:

Load 1 – 10kVA at PF=.6 lagging

Load 2 – 10kW at PF = 1

Load 3 – -6kVAR at PF=.2 leading

- Find the total complex power delivered by the source. $S_S =$ _____
- What is the source current magnitude? $I_S =$ _____
- Can the source current magnitude be reduced by 50% (circle) yes or no without changing the real power delivered or the source voltage magnitude? What will the power factor of the source be? PF_S _____

3. [3 points] You are given a balanced three phase Y-connected source where $V_{an} = 208\angle 0^\circ$ V rms. It is connected to two balanced three phase loads:

Load 1: 3 kVA at PF=.7 lagging

Load 2: 2 kVA at PF=0.75 leading

What are the values of the loads in the delta configuration?

$Z_{\Delta 1}$ _____


$Z_{\Delta 2}$ _____

What is the magnitude of the line current? I_L _____

If a third load is added to correct the power factor to PF=.8 lagging, will the load be capacitive or inductive?

(circle one) inductive or capacitive

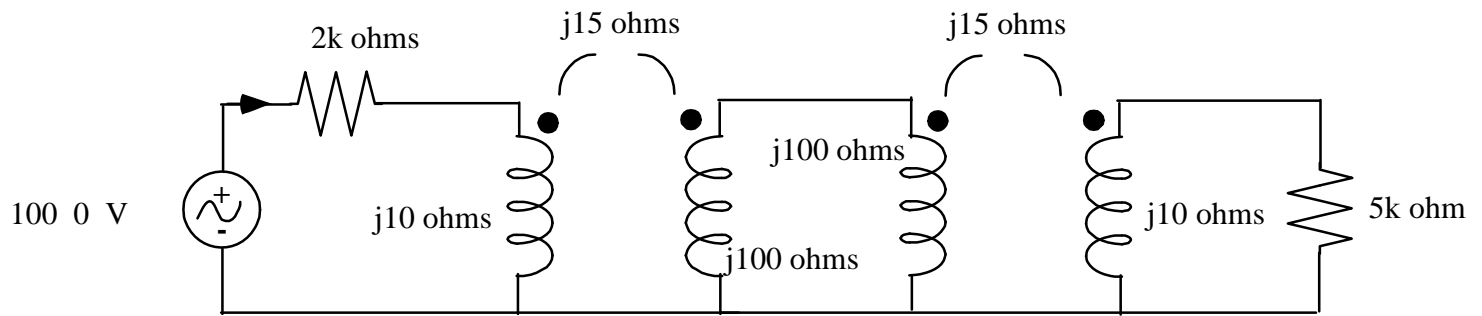4. [2 points] Consider the following circuit:



What is the power absorbed by the 5 k ohm resistor? $P =$ _____

Suppose the transformer pairs were removed from the circuit and the 5 k ohm resistor connected directly to the source (i.e. voltage source and 2k ohm source resistance). What is the power absorbed by the 5k ohm resistor? $P =$ _____

Explain why this occurs?