

EE 313 Extra Credit Option – 10 points

Due October 14th – no exceptions

You must make a reasonable effort on ALL parts of the problem to receive ANY credit.

1. For the following circuit, find the complex power and the average power and the reactive power delivered/absorbed by each circuit element. Show that the power delivered is equal (within round off error) to the power absorbed.

