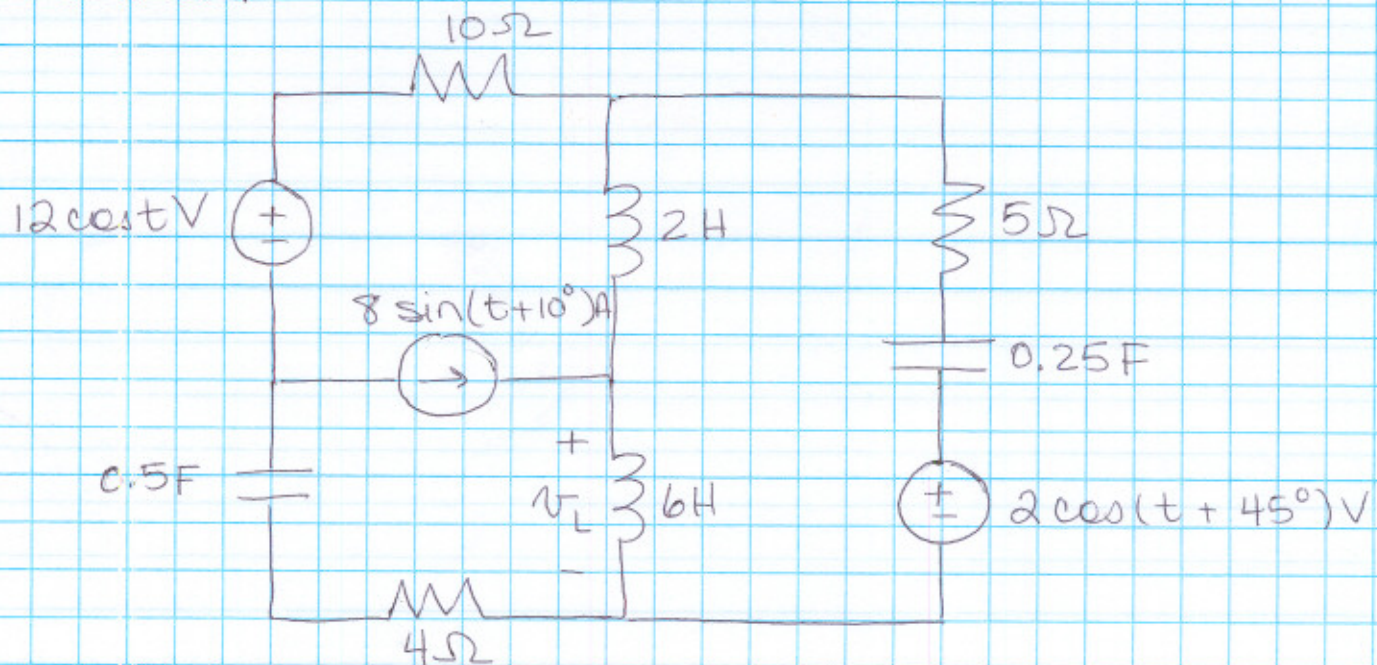


Practice Problems

Consider the circuit given in the time domain.




a) Convert the circuit to the frequency domain.
 $\omega = 1 \text{ rad/s}$

$$\begin{aligned} 12 \cos t &\rightarrow 12 \angle 0^\circ \text{ V} \\ 2 \cos(t + 45^\circ) &\rightarrow 2 \angle 45^\circ \text{ V} \\ 8 \sin(t + 10^\circ) &\rightarrow 8 \angle -80^\circ \text{ A} \\ 10 \Omega &\rightarrow 10 \Omega \\ 2 \text{ H} &\rightarrow j2 \Omega \\ 6 \text{ H} &\rightarrow j6 \Omega \\ 0.5 \text{ F} &\rightarrow -j2 \Omega \\ 4 \Omega &\rightarrow 4 \Omega \\ 5 \Omega &\rightarrow 5 \Omega \\ 0.25 \text{ F} &\rightarrow -j4 \Omega \end{aligned}$$

b) Solve for the real part of the time domain voltage using nodal analysis, mesh analysis, superposition and Thevenin equivalent ckt.

Nodal

page 2
Prac. Prob

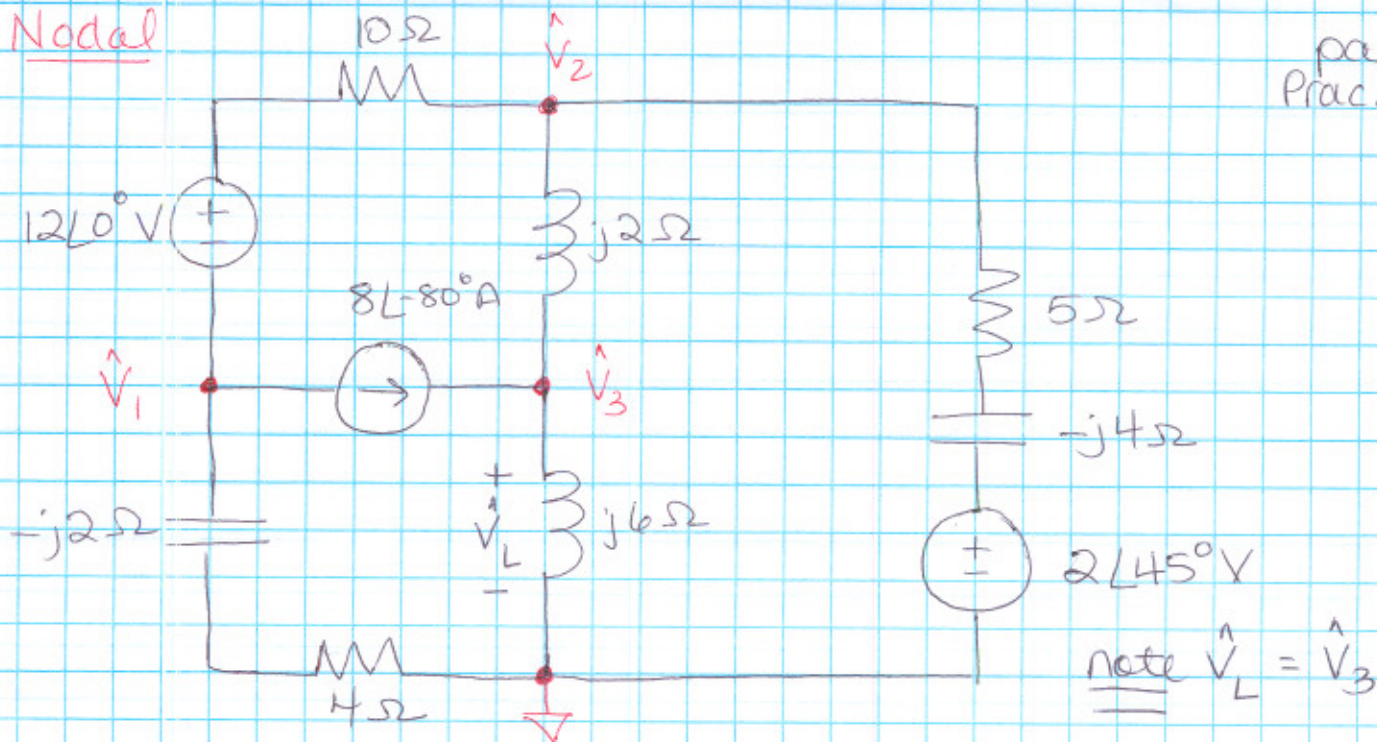

$$N1: \frac{\hat{V}_1 + 12\angle 0 - \hat{V}_2}{10} + \frac{\hat{V}_1}{4-j2} + 8\angle -80^\circ = 0$$

$$N2: \frac{\hat{V}_2 - \hat{V}_1 - 12\angle 0}{10} + \frac{\hat{V}_2 - 2\angle 45}{5-j4} + \frac{\hat{V}_2 - \hat{V}_3}{j2} = 0$$

$$N3: \frac{\hat{V}_3 - \hat{V}_2}{j2} + \frac{\hat{V}_3}{j6} + 8\angle 100 = 0$$

Simplify

$$N1: \hat{V}_1 \left(\frac{1}{10} + \frac{1}{4-j2} \right) + \hat{V}_2 \left(\frac{-1}{10} \right) = 1.2\angle 180 + 8\angle 100$$

$$\hat{V}_1 \left(\frac{4-j2+10}{10(4-j2)} \right) + \hat{V}_2 (-.1) = 8.29\angle 108.19$$

$$\hat{V}_1 \left(\frac{14-j2}{40-j20} \right) + \hat{V}_2 (-.1) = 8.29\angle 108.19$$

$$\hat{V}_1 (.316\angle 18.43) + \hat{V}_2 (-.1) = 8.29\angle 108.19$$

$$N2: \hat{V}_1(-.1) + \hat{V}_2\left(\frac{1}{10} + \frac{1}{5-j4} + \frac{1}{j2}\right) + \hat{V}_3\left(\frac{-1}{j2}\right) = \frac{12\angle 0}{10} + \frac{2\angle 45}{5-j4}$$

$$\hat{V}_1(-.1) + \hat{V}_2\left(\frac{(8+j10) + (j20) + (50-j40)}{10(5-j4)(j2)}\right) + \hat{V}_3(j0.5) = 1.27\angle 14.11^\circ$$

$$\hat{V}_1(-.1) + \hat{V}_2\left(\frac{58-j10}{80+j100}\right) + \hat{V}_3(j.5) = 1.27\angle 14.11^\circ$$

$$\hat{V}_1(-.1) + \hat{V}_2(.46\angle -61.12) + \hat{V}_3(j.5) = 1.27\angle 14.11^\circ$$

$$N3: \hat{V}_2\left(\frac{-1}{j2}\right) + \hat{V}_3\left(\frac{1}{j2} + \frac{1}{j6}\right) = 8\angle -80^\circ$$

$$\hat{V}_2(j.5) + \hat{V}_3\left(\frac{j8}{(j2)(j6)}\right) = 8\angle -80^\circ$$

$$\hat{V}_2(j.5) + \hat{V}_3\left(\frac{j8}{-12}\right) = 8\angle -80^\circ$$

$$\hat{V}_2(j.5) + \hat{V}_3(.667\angle -90) = 8\angle -80^\circ$$

3 equations / 3 unknowns

note $j.5 = .5\angle 90^\circ$

$$\begin{bmatrix} .316\angle 18.43 & -.1 & 0 \\ -.1 & .46\angle -61.12 & j.5 \\ 0 & j.5 & .667\angle -90 \end{bmatrix} \begin{bmatrix} \hat{V}_1 \\ \hat{V}_2 \\ \hat{V}_3 \end{bmatrix} = \begin{bmatrix} 8.29\angle 108.19 \\ 1.27\angle 14.11 \\ 8\angle -80^\circ \end{bmatrix}$$

$$\hat{V}_1 = 20.81\angle 82.67^\circ \text{ V}$$


$$\hat{V}_2 = 19.43\angle -47.12^\circ \text{ V}$$

$$\hat{V}_3 = 23.36\angle -21.57^\circ \text{ V}$$

$$\hat{V}_L = \hat{V}_3 = 23.36 \angle -21.57^\circ \text{ V}$$

$$v_L(t) = 23.36 \cos(t - 21.57^\circ) \text{ V}$$

mesh analysis

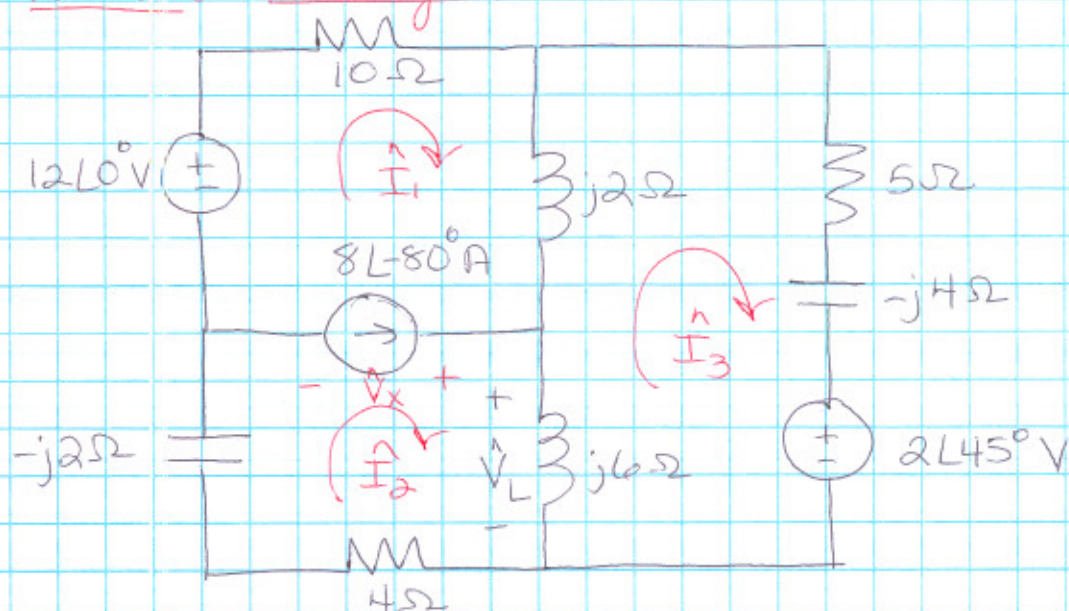

note

$$\hat{V}_L = j6(\hat{I}_2 - \hat{I}_3)$$

$$\hat{I}_2 - \hat{I}_1 = 8 \angle -80^\circ \text{ A}$$

(I labeled $\hat{V}_x$)

$$m1: 12 \angle 0 - 10 \hat{I}_1 - j2(\hat{I}_1 - \hat{I}_3) - \hat{V}_x = 0$$

$$m2: -(j2)(\hat{I}_2) + \hat{V}_x - j6(\hat{I}_2 - \hat{I}_3) - 4\hat{I}_2 = 0$$

$$m3: -j2(\hat{I}_3 - \hat{I}_1) - (5 - j4)\hat{I}_3 - (2 \angle 45) - j6(\hat{I}_3 - \hat{I}_2) = 0$$

Simplify

$$m1: \hat{I}_1(-10 - j2) + \hat{I}_3(j2) - \hat{V}_x = 12 \angle 180^\circ$$

$$m2: \hat{I}_2(-4 - j4) + \hat{I}_3(j6) + \hat{V}_x = 0$$

$$m3: \hat{I}_1(j2) + \hat{I}_2(j6) + \hat{I}_3(-5 - j4) = 2 \angle 45$$

Mesh Analysis

pg 5

Solve: w/ the 3 mesh equations and the known equation about the current source, there are 4 equations and 4 unknowns

However: we don't need $\hat{V}_x$ so I will add m1 and m2 together.

$$(m1+m2) \hat{I}_1 (-10-j2) + \hat{I}_2 (4-j4) + \hat{I}_3 (j8) = 12 \angle 180^\circ$$

$$(m3) \hat{I}_1 (j2) + \hat{I}_2 (j6) + \hat{I}_3 (-5-j4) = 2 \angle 45^\circ$$

$$\text{Known } \hat{I}_1 (-1) + \hat{I}_2 (1) = 8 \angle -80^\circ$$

$$\begin{bmatrix} -10-j2 & -4-j4 & j8 \\ j2 & j6 & -5-j4 \\ -1 & 1 & 0 \end{bmatrix} \begin{bmatrix} \hat{I}_1 \\ \hat{I}_2 \\ \hat{I}_3 \end{bmatrix} = \begin{bmatrix} 12 \angle 180^\circ \\ 2 \angle 45^\circ \\ 8 \angle -80^\circ \end{bmatrix}$$

$$\hat{I}_1 = 3.49 \angle 87.66^\circ \text{ A}$$

$$\hat{I}_2 = 4.65 \angle -70.75^\circ \text{ A}$$

$$\hat{I}_3 = 3.07 \angle -14.43^\circ \text{ A}$$

$$\hat{V}_L = j6(\hat{I}_2 - \hat{I}_3)$$

$$= 23.40 \angle -21.67^\circ \text{ V}$$


$$v_L(t) = 23.40 \cos(t - 21.67^\circ) \text{ V}$$

checks w/ nodal 😊


Superposition

12L0° ON

pg 6

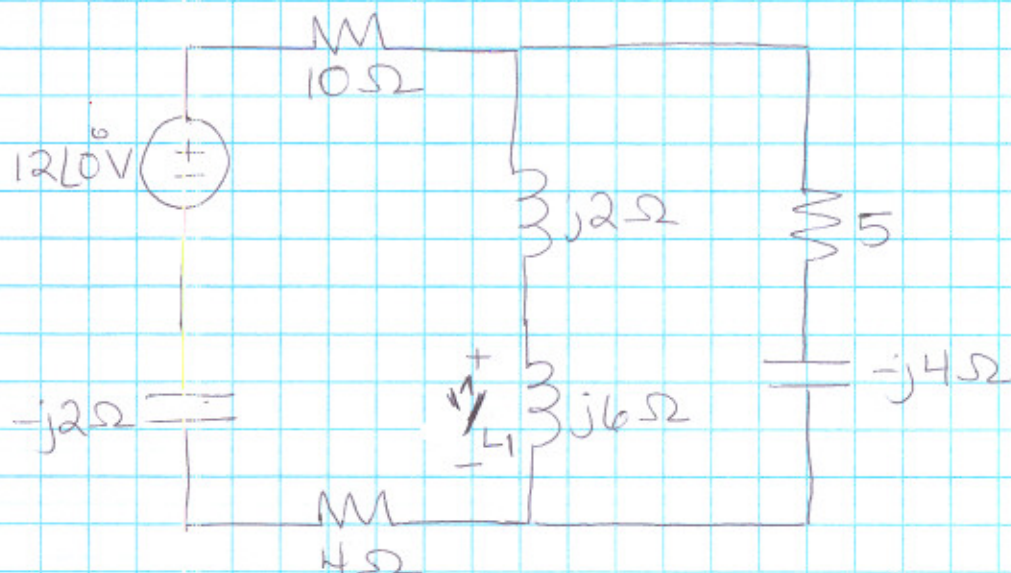

Simplify

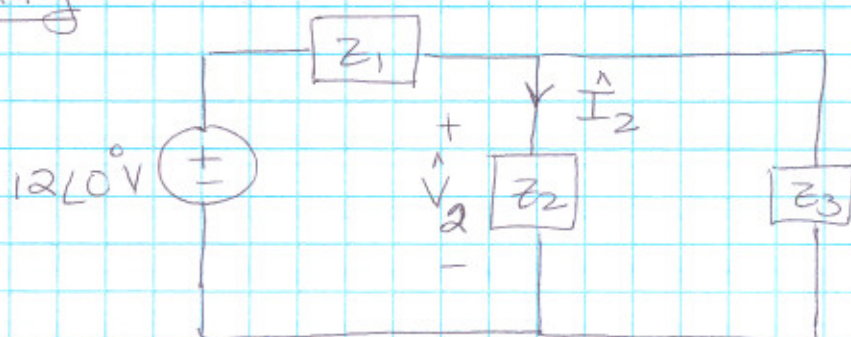

note $\hat{V}_{L1} = \hat{I}_2(j6)$

$$Z_1 = 14 - j2\Omega$$

$$Z_2 = j8\Omega$$


$$Z_3 = 5 - j4\Omega$$

using voltage division to solve for $\hat{V}_2$


$$\hat{V}_2 = 12\angle 0^\circ \cdot \frac{Z_2 \parallel Z_3}{Z_1 + (Z_2 \parallel Z_3)} = 4.40\angle 13.32^\circ \text{ V}$$

$$\hat{I}_2 = \frac{\hat{V}_2}{Z_2} = 0.55\angle -76.68^\circ \text{ A}$$

$$\hat{V}_{L1} = \hat{I}_2(j6) = 3.30\angle 13.32^\circ \text{ V}$$

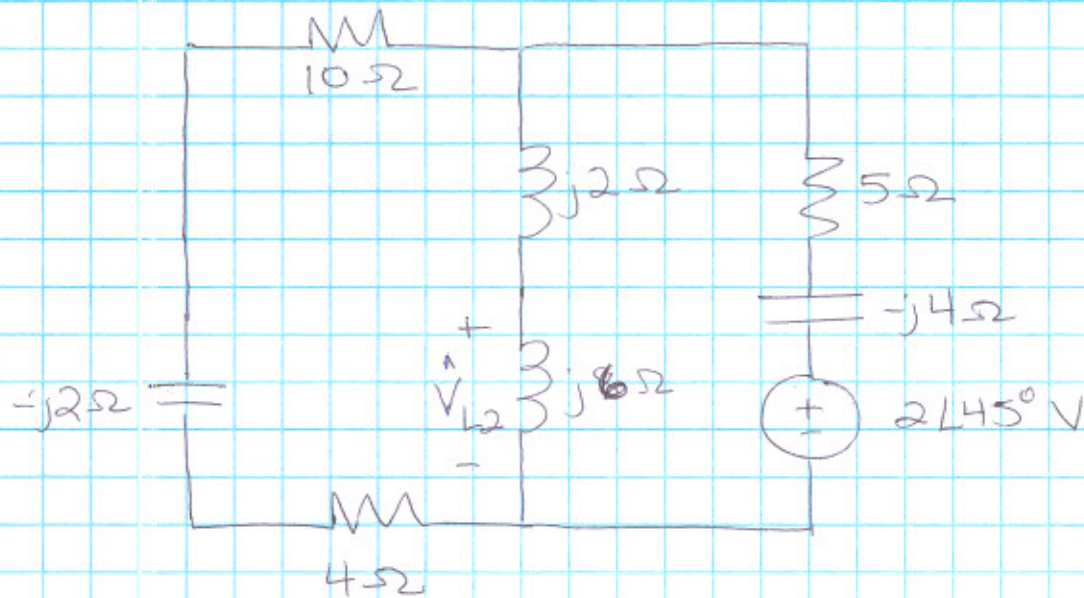Superposition $2\angle 45^\circ \text{ V}$ ON

Simplify

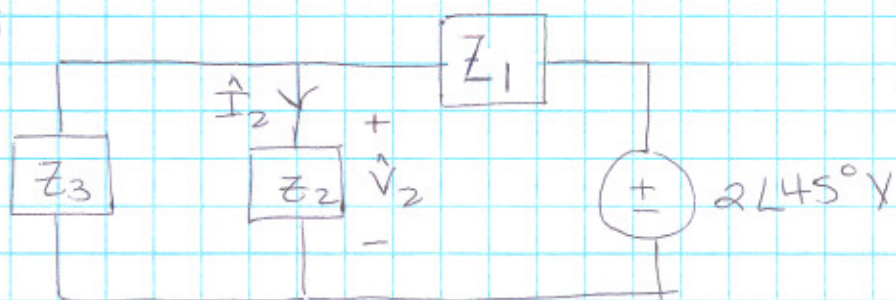

$$\begin{aligned} Z_1 &= 5 - j4\Omega \\ Z_2 &= j8\Omega \\ Z_3 &= 4 - j2\Omega \end{aligned}$$

again: $\hat{V}_{L2} = \hat{I}_2(j6)$

by voltage division

$$\hat{V}_2 = 2\angle 45^\circ \cdot \frac{Z_2 \parallel Z_3}{Z_1 + (Z_2 \parallel Z_3)}$$

$$\hat{V}_2 = 1.62 \angle 88.85^\circ \text{ V}$$

$$\hat{I}_2 = \frac{\hat{V}_2}{Z_2} = 0.202 \angle -1.15^\circ \text{ A}$$


$$\hat{V}_{L2} = \hat{I}_2(j6)$$

$$\hat{V}_{L2} = 1.21 \angle 88.85^\circ \text{ V}$$

Superposition

pg 8

$8 \angle -80^\circ \text{ A}$ ON

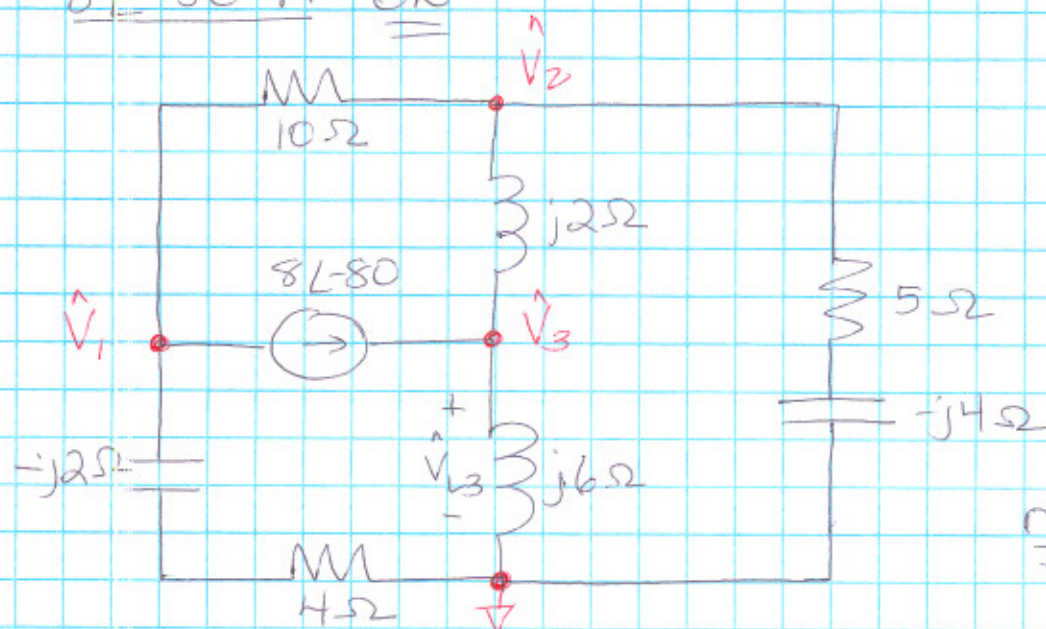

Simplification is not a good option. I'm going to use nodal analysis.

note $\hat{V}_{L3} = \hat{V}_3$

N1 $\frac{\hat{V}_1 - \hat{V}_2}{10} + \frac{\hat{V}_1}{4 - j2} + 8 \angle -80 = 0$ $\hat{V}_1 (.316 \angle 18.43) + \hat{V}_2 (-.1) = 8 \angle 100$

N2 $\frac{\hat{V}_2 - \hat{V}_1}{10} + \frac{\hat{V}_2 - \hat{V}_3}{j2} + \frac{\hat{V}_2}{5 - j4} = 0$ $\hat{V}_1 (-.1) + \hat{V}_2 (.46 \angle -61.12) + \hat{V}_3 (.5 \angle 90) = 0$

N3 $\frac{\hat{V}_3 - \hat{V}_2}{j2} + \frac{\hat{V}_3}{j6} + 8 \angle 100 = 0$ $\hat{V}_2 (.5 \angle 90) + \hat{V}_3 (.67 \angle 90) = 8 \angle -80$

solving

$$\begin{bmatrix} .316 \angle 18.43 & -.1 & 0 \\ -.1 & .46 \angle -61.12 & .5 \angle 90 \\ 0 & .5 \angle 90 & .67 \angle 90 \end{bmatrix} \begin{bmatrix} \hat{V}_1 \\ \hat{V}_2 \\ \hat{V}_3 \end{bmatrix} = \begin{bmatrix} 8 \angle 100 \\ 0 \\ 8 \angle -80 \end{bmatrix}$$

$\hat{V}_1 = 19.72 \angle 76.04^\circ \text{ V}$

$\hat{V}_2 = 18.93 \angle -61.52^\circ \text{ V}$

$\hat{V}_3 = 21.19 \angle -29.22^\circ \text{ V}$

check w/ nodal mesh

$\hat{V}_{L3} = 21.19 \angle -29.22^\circ \text{ V}$

$\hat{V}_L = \hat{V}_{L1} + \hat{V}_{L2} + \hat{V}_{L3}$


$= 23.29 \angle -21.08^\circ \text{ V}$

$v_L(t) = 23.29 \cos(t - 21.08^\circ) \text{ V}$

Thevenin's

pg 9

Ckt network (load is $j6\Omega$)

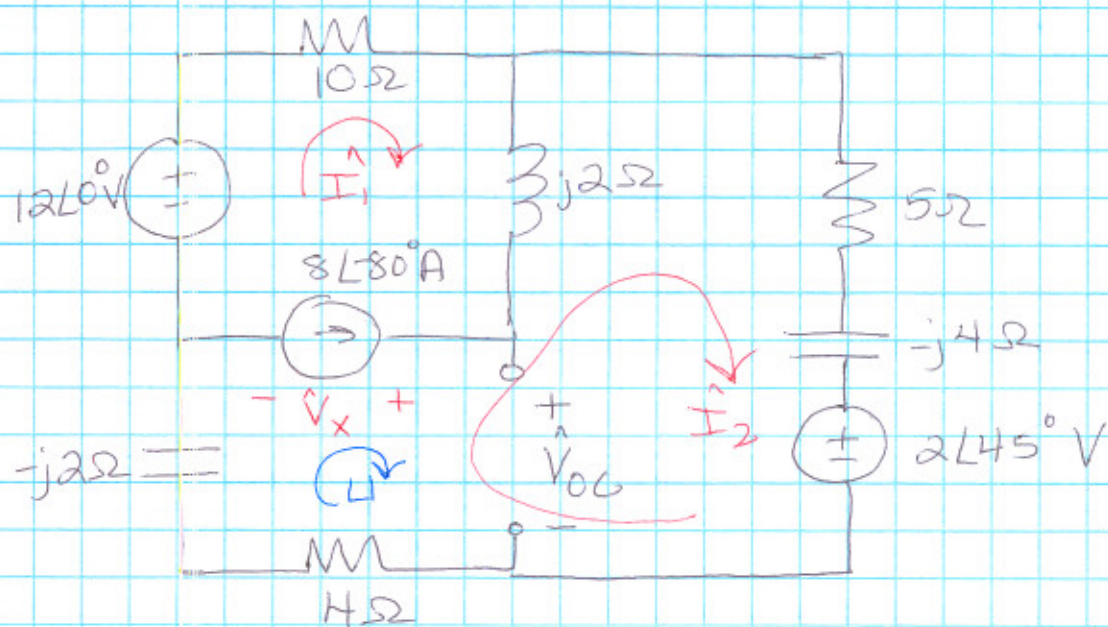

note

I will use mesh analysis to solve

$$\hat{I}_2 - \hat{I}_1 = 8L-80^\circ \text{ (Known)}$$

$$\underline{m1} \quad 12L0 - 10\hat{I}_1 - j2(\hat{I}_1 - \hat{I}_2) - \hat{V}_x = 0$$

$$\underline{m2} \quad -(4-j2)\hat{I}_2 + \hat{V}_x - j2(\hat{I}_2 - \hat{I}_1) - (5-j4)\hat{I}_2 - 2L45^\circ = 0$$

* write a KVL loop (see L1 in circuit) to find $\hat{V}_{oc}$

$$-(4-j2)\hat{I}_2 + \hat{V}_x - \hat{V}_{oc} = 0$$

using $m1$ & $m2$ and known

$$\underline{m1} \quad \hat{I}_1(-10-j2) + \hat{I}_2(j2) - \hat{V}_x = 12L180$$

$$\underline{m2} \quad \hat{I}_1(j2) + \hat{I}_2(-9+j4) + \hat{V}_x = 2L45$$

$$\text{known} \quad \hat{I}_1(-1) + \hat{I}_2(1) = 8L-80$$

$$\text{solve} \quad \begin{bmatrix} -10-j2 & j2 & -1 \\ j2 & -9+j4 & 1 \\ -1 & 1 & 0 \end{bmatrix} \begin{bmatrix} \hat{I}_1 \\ \hat{I}_2 \\ \hat{V}_x \end{bmatrix} = \begin{bmatrix} 12L180 \\ 2L45 \\ 8L-80 \end{bmatrix}$$

$$\hat{I}_1 = 4.52L77.29^\circ \text{ A} \quad \hat{I}_2 = 4.21L-55.50^\circ \text{ A} \quad \hat{V}_x = 45L-66.68^\circ \text{ V}$$

Thevenin's ckt


p10

solving for $\hat{V}_{oc}$


$$\hat{V}_{oc} = \hat{V}_x - (4 - j2)\hat{I}_2 = 27.31 \angle -56.14^\circ \text{ V}$$

$$\hat{V}_{TH} = \hat{V}_{oc}$$

Find Z_{TH} using Quick method.

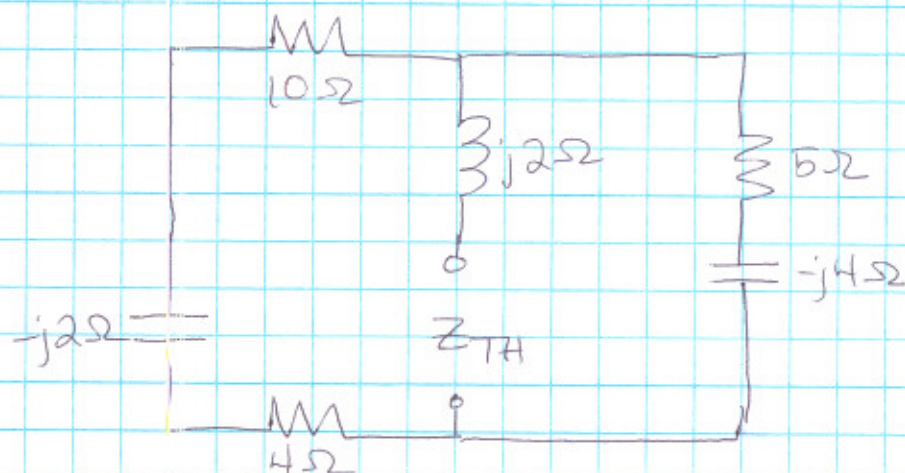

Simplify

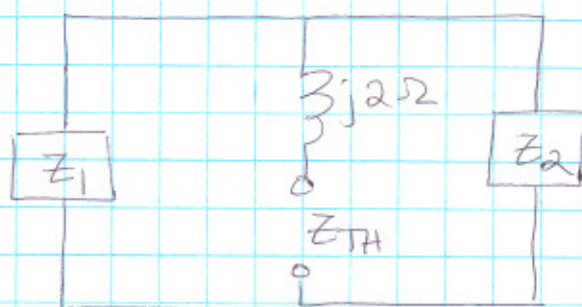

$$Z_1 = 14 - j2 \Omega$$


$$Z_2 = 5 - j4 \Omega$$

$$Z_{TH} = (Z_1 || Z_2) + j2$$

$$= 3.97 \angle -3.20^\circ \Omega$$

$$\text{or } 3.96 - j0.22 \Omega$$

Build Thev. Equiv. ckt

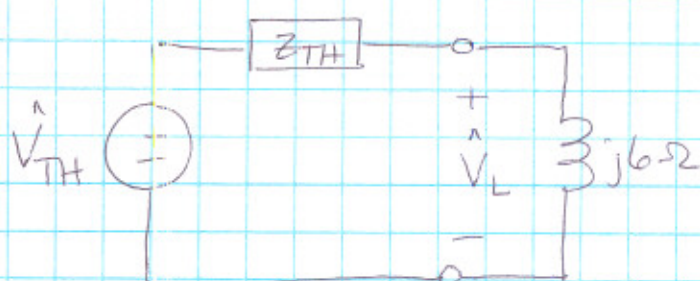

$$\hat{V}_L = \hat{V}_{TH} \cdot \frac{j6}{Z_{TH} + j6}$$

$$= 23.38 \angle -21.69^\circ \text{ V}$$

$$v_L(t) = 23.38 \cos(t - 21.69^\circ) \text{ V}$$

checks w/ other techniques
(smiley face)