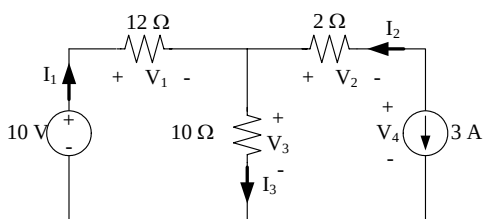


## Review of DC Circuit Analysis


I expect that you already know how to solve these problems. If you are having trouble with these, you need to review your EE 213/EE 300 notes. I will review techniques like KCL, KVL, nodal analysis, mesh analysis, superposition, equivalent circuits and source transformation, but it should be a refresher for you.

- Consider the following circuit, use nodal, mesh and superposition to find each labeled current and voltage, and the power delivered or absorbed by each element.




| Element    | I (A) | V (V)  | P (W)   |
|------------|-------|--------|---------|
| 10V source | 1.82  | 10     | 18.20 D |
| 12 ohm     | 1.82  | 21.82  | 39.75 A |
| 10 ohm     | -1.18 | -11.82 | 13.92 A |
| 2 ohm      | -3    | 6      | 18 A    |
| 3A source  | 3     | -17.82 | 53.46 D |

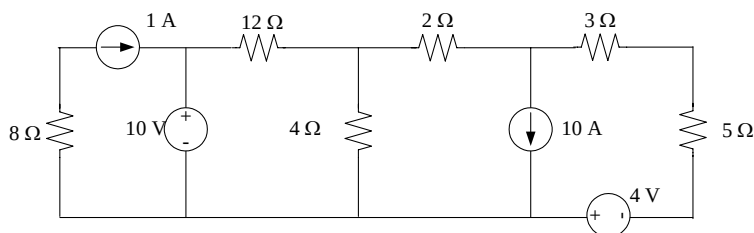- Solve for all the currents, voltages and power associated with each element in the circuit given below. Unless given, label the current directions and voltage polarities.



| Element    | V (V)  | I (A) | P (W)    |
|------------|--------|-------|----------|
| 8 ohm      | 8      | 1     | 8 A      |
| 1A source  | -18    | 1     | 18 D     |
| 10V source | 10     | -1.29 | 12.90 D  |
| 12 ohm     | 27.48  | 2.29  | 62.93 A  |
| 4 ohm      | -17.48 | -4.37 | 76.39 A  |
| 2 ohm      | 13.30  | 6.65  | 88.45 A  |
| 10A source | -30.77 | 10    | 307.70 D |
| 3 ohm      | -10.05 | -3.35 | 33.67 A  |
| 5 ohm      | -16.75 | -3.35 | 56.11 A  |
| 4V source  | 4      | -3.35 | 13.40 A  |

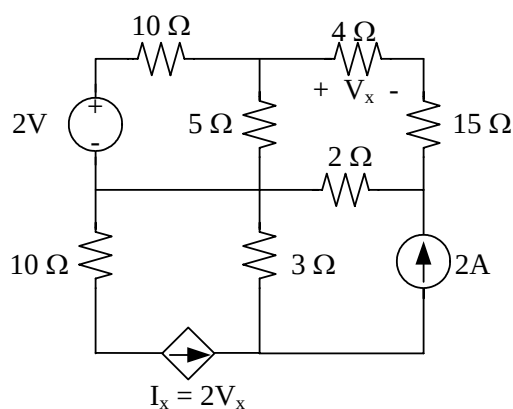- Solve for all the currents, voltages and power associated with each element in the circuit given below. Unless given, label the current directions and voltage polarities.



| Element     | V (V)  | I (A) | P (W)   |
|-------------|--------|-------|---------|
| 10 ohm top  | 0.88   | 0.09  | 0.08 A  |
| 2A source   | 13.01  | 2     | 26.03 D |
| 2V source   | 2      | 0.09  | 0.18 D  |
| 15 ohm      | -2.06  | -0.14 | 0.28 A  |
| 4 ohm       | -0.55  | -0.14 | 0.08 A  |
| 2 ohm       | 3.73   | 1.86  | 6.94 A  |
| Dep source  | -20.25 | -1.10 | 22.19 D |
| 3 ohm       | -9.29  | 3.10  | 28.75 A |
| 5 ohm       | 1.12   | 0.22  | 0.25 A  |
| 10 ohm left | -10.96 | -1.10 | 12.01 A |