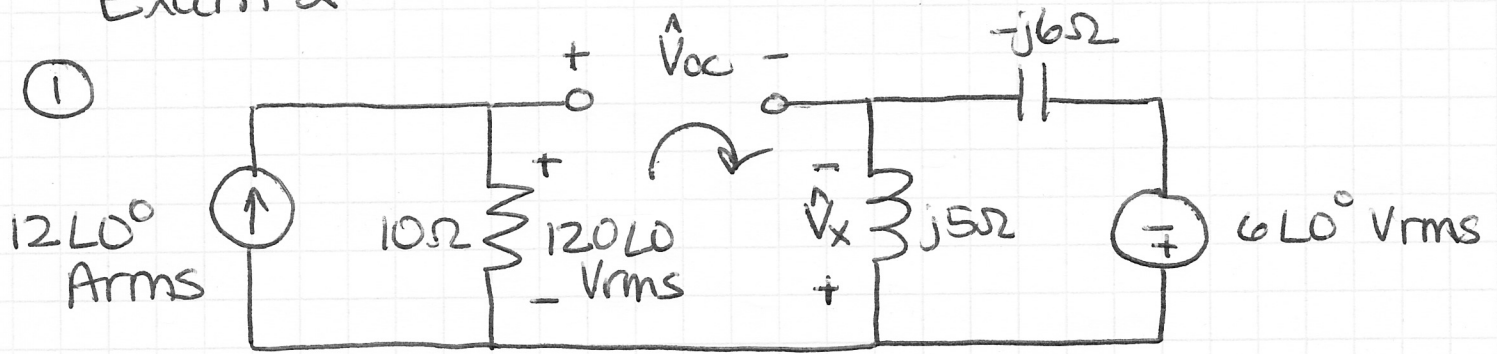


Practice Problems

Exam 2


①



$$\hat{V}_x = (6\angle 0) \left(\frac{j5}{j5 - j6} \right) = 30 \angle 180^\circ \text{ Vrms}$$


by KVL: $120\angle 0 - \hat{V}_{oc} + \hat{V}_x = 0$
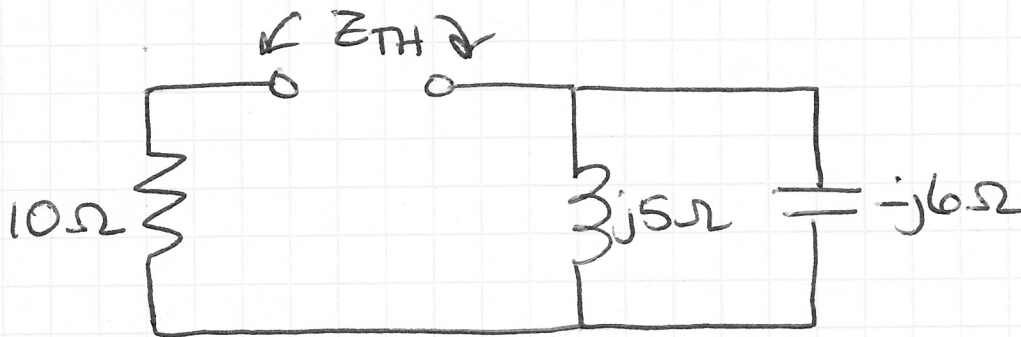
$$\begin{aligned} \hat{V}_{oc} &= 120\angle 0 + \hat{V}_x \\ &= 90\angle 0^\circ \text{ Vrms} \end{aligned}$$



$$Z_{TH} = 10 + (j5 \parallel -j6) = 31.62 \angle 71.56^\circ \Omega$$

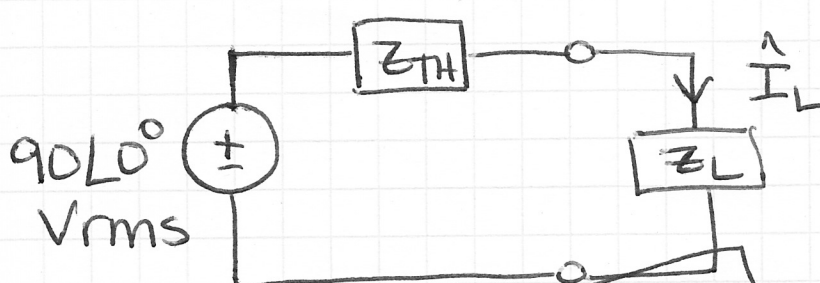
$$Z_L = Z_{TH}^* = 31.62 \angle -71.56^\circ \Omega$$



$$\begin{aligned} \hat{I}_L &= \frac{90\angle 0}{Z_{TH} + Z_L} \\ &= 4.5\angle 0^\circ \text{ Arms} \end{aligned}$$

$P_L = 202.5 \text{ W, Abs}$
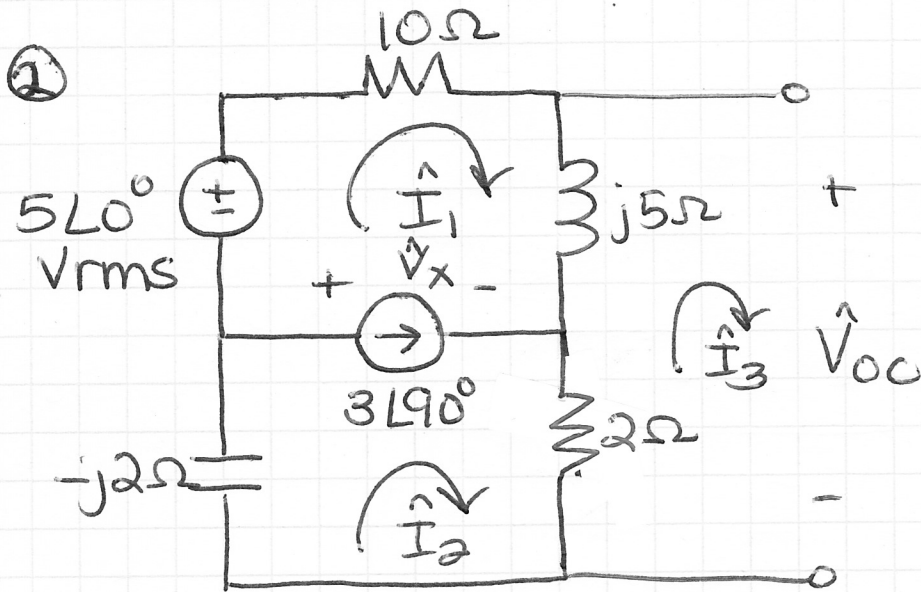
$$\begin{aligned} P_L &= (I_L)^2 \text{Re}[Z_L] \\ &= (4.5)^2 (10) \end{aligned}$$



$$\hat{I}_3 = 0$$

$$\hat{I}_2 - \hat{I}_1 = 3\angle 90^\circ$$

$$5\angle 0 - 10\hat{I}_1 - j5(\hat{I}_1 - \hat{I}_3) + \hat{V}_x = 0$$

$$-\hat{V}_x - 2(\hat{I}_2 - \hat{I}_3) - (-j2)\hat{I}_2 = 0$$

add $\nearrow$

$$5\angle 0 - 10\hat{I}_1 - j5\hat{I}_1 - 2\hat{I}_2 + j2\hat{I}_2 = 0$$

$$\hat{I}_1(-10 - j5) + \hat{I}_2(-2 + j2) = 5\angle 80^\circ$$

$$\hat{I}_1(1\angle 180) + \hat{I}_2(1) = 3\angle 90^\circ$$

$$\hat{I}_1 = 0.49\angle -113.50^\circ \text{ Arms}$$

$$\hat{I}_2 = 2.56\angle 94.40^\circ \text{ Arms}$$


m3:

$$-\hat{V}_{oc} - 2(\hat{I}_3 - \hat{I}_2) - j5(\hat{I}_3 - \hat{I}_2)$$

$$\hat{V}_{oc} = 2\hat{I}_2 + j5\hat{I}_2$$

$$= 13.79\angle 162.60^\circ \text{ Vrms}$$


②

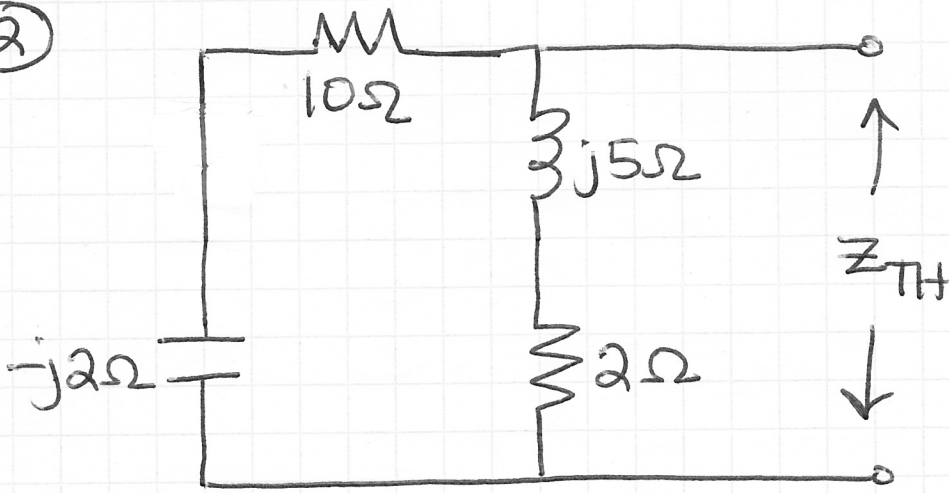

$$Z_{TH} = (10 - j2) \parallel (2 + j5)$$

$$= 4.44 \angle 42.85^\circ \Omega$$
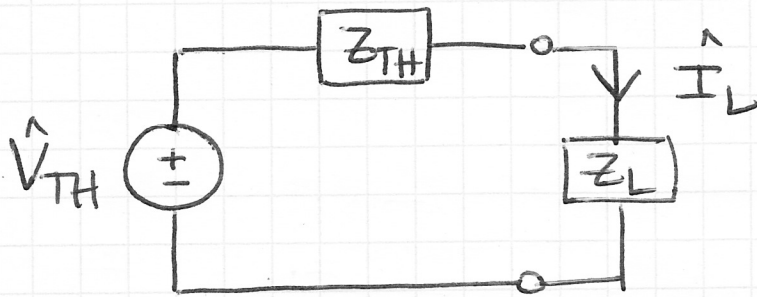
$$Z_L = Z_{TH}^* = 4.44 \angle -42.85^\circ \Omega$$



$$\hat{I}_L = \frac{13.79 \angle 162.60}{4.44 \angle 42.85 + 4.44 \angle -42.85}$$

$$= 2.12 \angle 162.60^\circ \text{ Arms}$$

$$P_L = (2.12)^2 \text{Re}[Z_L]$$

$$= 14.63 \text{ W, Abs}$$

③

$$a) Z_1: P+jQ = 48+j27 \text{ kVA} \\ = 55.07 \angle 29.36^\circ \text{ kVA}$$

$$55.07 \angle 29.36^\circ \text{ kVA} = (120 \angle 0^\circ) \hat{I}_1^*$$

$$\hat{I}_1 = 458.94 \angle -29.36^\circ \text{ Arms}$$

$$Z_2: \hat{S}_2 = 32 \angle 65^\circ \text{ kVA} = (120 \angle 0^\circ) (\hat{I}_2^*)$$

$$\hat{I}_2 = 266.67 \angle -65^\circ \text{ Arms}$$

$$Z_3: \angle Z_3 = \cos^{-1}(0.4) = 66.42^\circ$$

$$\hat{I}_3 = 20 \angle -66.42^\circ \text{ Arms}$$

$$\hat{I}_S = \hat{I}_1 + \hat{I}_2 + \hat{I}_3 = 711.59 \angle -42.97^\circ \text{ Arms}$$

$$b) Z_1 = \frac{120 \angle 0^\circ}{\hat{I}_1} = 0.261 \angle 29.36^\circ \Omega$$

$$Z_2 = \frac{120 \angle 0^\circ}{\hat{I}_2} = 0.45 \angle 65^\circ \Omega$$

$$Z_3 = \frac{120 \angle 0^\circ}{\hat{I}_3} = 6 \angle 66.42^\circ \Omega$$

$$c) \hat{S}_S = (120 \angle 0^\circ) (\hat{I}_S^*) = 85.39 \angle 42.97^\circ \text{ kVA}$$

$$P_S = \text{Re}[\hat{S}_S] = 62.48 \text{ kW}$$

$$Q_S = \text{Im}[\hat{S}_S] = 58.20 \text{ kVAR}$$

cont

pg 5

③ $P_S = 62.48 \text{ kW}$

d) $\hat{I}_{\text{old}} = 711.59 \angle -42.97^\circ \text{ Arms}$

$$62.48 \times 10^3 = 120 (I_{\text{new}}) (0.95)$$

$$I_{\text{new}} = 548.07 \text{ Arms}$$

$$\angle Z_{\text{eff}} = \cos^{-1}(0.95) = 18.19^\circ$$

$$\hat{I}_{\text{new}} = 548.07 \angle -18.19^\circ$$

$$\hat{I}_C = \hat{I}_{\text{new}} - \hat{I}_{\text{old}} = 313.94 \angle 90^\circ \text{ Arms}$$

$$Z_C = \frac{120 \angle 0}{\hat{I}_C} = 0.382 \angle -90^\circ \Omega$$

e) $\frac{1}{\omega C} = 0.382 \quad \omega = 377 \text{ rad/s}$

$$\boxed{C = 6.94 \text{ mF}}$$


f) to minimize source current mag. $P_{\text{eff}} = 1$

$$62.48 \times 10^3 = 120 (I_{\text{new}}) (1)$$

$$I_{\text{new}} = 520.67 \text{ Arms}$$

④ cont
assume both are γ -connected

pg 6

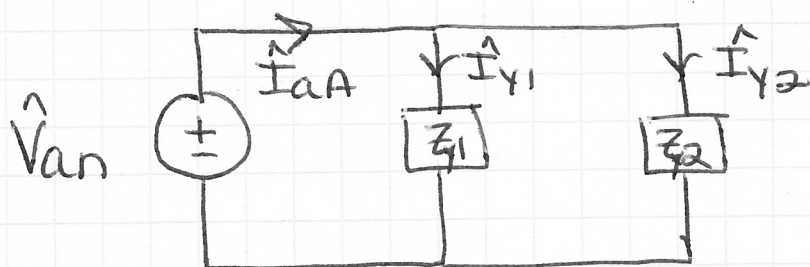

$$\hat{V}_{an} = \frac{V_L}{\sqrt{3}} \angle 0^\circ = 138.56 \angle 0^\circ \text{ Vrms}$$

$$Z_{Y1}: 30 \times 10^3 = \sqrt{3} V_L I_{L1} \quad \angle Z_{Y1} = \cos^{-1}(0.5) = 60^\circ$$

$$I_{L1} = 72.17 \text{ Arms}$$

$$\hat{I}_{Y1} = 72.17 \angle -60^\circ \text{ Arms}$$

$$Z_{Y2}: 18 \angle 20^\circ \text{ kVA}$$

$$18 \times 10^3 = \sqrt{3} V_L I_{L2} \quad \angle Z_{Y2} = 20^\circ$$

$$I_{L2} = 43.30 \text{ Arms}$$

$$\hat{I}_{Y2} = 43.30 \angle -20^\circ \text{ Arms}$$

$$\hat{I}_{aA} = \hat{I}_{Y1} + \hat{I}_{Y2} = 108.95 \angle -45.20^\circ \text{ Arms}$$

$$Z_{Y1} = \frac{\hat{V}_{an}}{\hat{I}_{Y1}} = 1.92 \angle 60^\circ \Omega$$


$$Z_{Y2} = \frac{\hat{V}_{an}}{\hat{I}_{Y2}} = 3.2 \angle 20^\circ \Omega \quad Z_{\Delta 2} = (Z_{Y2})^3 = 9.6 \angle 20^\circ \Omega$$

cont

pg 7

(5)

a) assume Δ connected

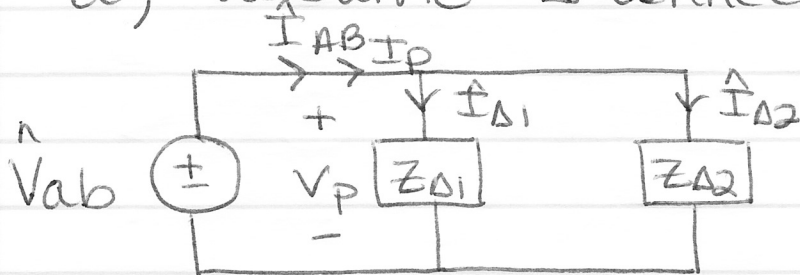

$$V_p = |\hat{V}_{ab}| = \sqrt{3} |\hat{V}_{an}| = 207.85 \text{ Vrms}$$

$$\underline{Z_{\Delta 1}}: 39 \times 10^3 = \sqrt{3} V_L I_{L1}$$

$$I_{L1} = 108.33 \text{ Arms}$$

$$I_{p1} = \frac{I_{L1}}{\sqrt{3}} = 62.55 \text{ Arms}$$

$$\angle Z_{\Delta 1} = \cos^{-1}(0.7) = 45.57^\circ$$

$$\hat{I}_{\Delta 1} = 62.55 \angle -15.57^\circ \text{ Arms}$$

$$Z_{\Delta 1} = \frac{\hat{V}_{ab}}{\hat{I}_{\Delta 1}} = 3.32 \angle 45.57^\circ \Omega$$

$$\underline{Z_{\Delta 2}}: 15 \times 10^3 = \sqrt{3} V_L I_{L2} \quad \angle Z_{\Delta 2} = 0$$

$$I_{L2} = 41.67 \text{ Arms}$$

$$I_{p2} = \frac{I_{L2}}{\sqrt{3}} = 24.05 \text{ Arms}$$

$$\hat{I}_{\Delta 2} = 24.05 \angle 30^\circ \text{ Arms}$$

cont

pg 8

⑤

$$Z_{\Delta 2} = \frac{\hat{V}_{ab}}{\hat{I}_{\Delta 2}} = 8.64 \angle 0^\circ \Omega$$

$$\hat{I}_{AB} = \hat{I}_{\Delta 1} + \hat{I}_{\Delta 2} = 81.22 \angle -3.36^\circ \text{ Arms}$$

$$I_p = |\hat{I}_{AB}| = 81.22 \text{ Arms}$$

$$\hat{I}_{aA} = \hat{I}_{AB} - \hat{I}_{cA} = 140.68 \angle -33.36^\circ \text{ Arms}$$

b) Assume Y-loads

$$\text{from part a: } \hat{I}_{Y1} = 108.33 \angle -45.57^\circ \text{ Arms}$$

$$\hat{I}_{Y2} = 41.67 \angle 0^\circ \text{ Arms}$$

$$\hat{I}_{aA} = \hat{I}_{Y1} + \hat{I}_{Y2} = 140.68 \angle -33.36^\circ \text{ Arms}$$

$$\therefore I_p = I_L = 140.68 \text{ Arms}$$

$$V_p = |\hat{V}_{an}| = 120 \text{ Vrms}$$

$$Z_{Y1} = \frac{\hat{V}_{an}}{\hat{I}_{Y1}} = 1.11 \angle 45.57^\circ \Omega$$

$$Z_{Y2} = \frac{\hat{V}_{an}}{\hat{I}_{Y2}} = 2.88 \angle 0^\circ \Omega$$