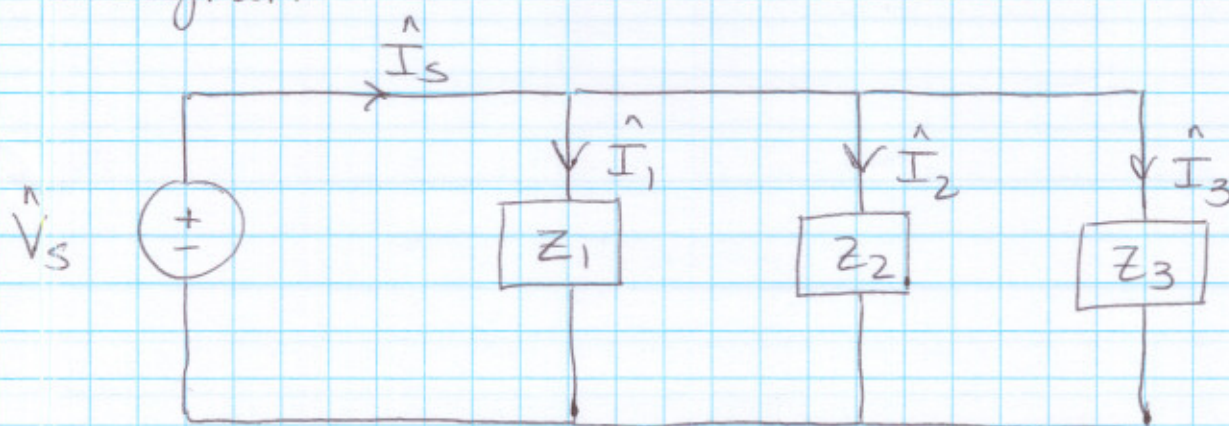


Example Power Factor Problem:

pg 1

Ckt diagram



assume 0° phase on $\hat{V}_s$ so $\hat{V}_s = 150 \angle 0^\circ \text{ Vrms}$

a) ^{a) & b)} Impedances + Currents

$$Z_1: P_1 = V_s I_1 \text{ PF}_1 \quad I_1 = \frac{25 \times 10^3}{(150)(.5)} = 333.33 \text{ Arms}$$

$$\angle Z_1 = \cos^{-1}(0.5) = 60^\circ$$

$$\cancel{Z_1} \quad |Z_1| = \frac{V_s}{I_1} = \frac{150}{333.33} = 0.45 \Omega$$

$$\hat{Z}_1 = 0.45 \angle 60^\circ \Omega$$

$$\hat{I}_1 = 333.33 \angle -60^\circ \text{ Arms}$$

$$Z_2: \hat{S}_2 = P_2 + jQ_2 = 18 - j12 \text{ kVA} \\ = 21.63 \angle -33.69^\circ \text{ kVA}$$

$$\angle Z_2 = -33.69^\circ$$

$$21.63 = V_s \cdot I_2$$

$$|Z_2| = \frac{V_s}{I_2} = 1.04$$

$$I_2 = 144.20 \text{ Arms}$$

$$Z_2 = 1.04 \angle -33.69^\circ$$

$$\hat{I}_2 = 144.20 \angle +33.69^\circ \text{ Arms}$$

Example Power Factor Problem

pg 2

a+b) (cont)

$$Z_3 : \angle Z_3 = \cos^{-1}(0.75) = 41.41^\circ$$

$$|Z_3| = \frac{V_s}{I_3} = \frac{150}{60} = 2.5$$

$$Z_3 = 2.5 \angle 41.41^\circ \Omega \quad I_3 = 60 \angle -41.41^\circ \text{ Arms}$$

c) option 1: $P_s = P_1 + P_2 + P_3$

$$P_3 = V_s I_3 \cdot PF_3 = 6.75 \text{ kW}$$

$$P_s = (25 + 18 + 6.75) = 49.75 \text{ kW}$$

or option 2: $\hat{I}_s = \hat{I}_1 + \hat{I}_2 + \hat{I}_3$
 $= 414.34 \angle -36.83^\circ \text{ Arms}$

~~or option 3:~~

$$\hat{S}_s = \hat{V}_s \cdot \hat{I}_s^* = (150 \angle 0)(414.34 \angle 36.83^\circ)$$

$$\hat{S}_s = 62.15 \angle 36.83^\circ \text{ kVA}$$

$$P_s = \text{Re}[\hat{S}_s] = 49.75 \text{ kW}$$

or option 3: combined loads = $Z_1 \parallel Z_2 \parallel Z_3$

$$= 0.362 \angle 36.83^\circ$$

$$PF_{1,2,3} = \cos(36.83) = 0.8 \text{ lag}$$

$$P_s = V_s I_s \cdot PF_{1,2,3} = (150)(414.34)(0.8)$$

$$P_s = 49.75 \text{ kW}$$

Example Power Factor Problem

pg 3

d) ~~can~~ $\hat{S}_1 = V_s I_1 \angle Z_1 = (150)(333.33) \angle 60^\circ = 50 \angle 60^\circ \text{ kVA}$

or $\hat{S}_1 = \hat{V}_s \cdot \hat{I}_1^* = (150 \angle 0)(333.33 \angle 60^\circ) = 50 \angle 60^\circ \text{ kVA}$

or $Q_1 = V_s I_1 \sin(60^\circ) = 43.30 \text{ kVAR}$

$\hat{S}_1 = P_1 + jQ_1 = 25 + j43.30 \text{ kVA} \Rightarrow 50 \angle 60^\circ \text{ kVA}$

$\hat{S}_2 = P_2 + jQ_2 = 18 - j12 \text{ kVA} \Rightarrow 21.63 \angle -33.69^\circ \text{ kVA}$

or $\hat{S}_2 = \hat{V}_s \hat{I}_2^* = 21.63 \angle -33.69^\circ \text{ kVA}$

or $\hat{S}_2 = V_s I_2 \angle Z_2 = 21.63 \angle -33.69^\circ \text{ kVA}$

$\hat{S}_3 = V_s I_3 \angle Z_3 = (150)(60) \angle 41.41^\circ = 9 \angle 41.41^\circ \text{ kVA}$

or $\hat{S}_3 = \hat{V}_s \cdot \hat{I}_3^* = \cancel{(150)(60)} 9 \angle 41.41^\circ \text{ kVA}$

or $Q_3 = V_s I_3 \sin(\angle Z_3) = 5.95 \text{ kVAR}$

$P_3 = V_s I_3 \cdot \text{PF}_3 = 6.75 \text{ kW}$

$\hat{S}_3 = P_3 + jQ_3 = 9 \angle 41.40^\circ \text{ kVA}$

e) option 1 $Z_1 \parallel Z_2 \parallel Z_3 = 0.362 \angle 36.83^\circ$

$\text{PF}_{1,2,3} = \cos(36.83) = 0.8 \text{ lagging}$

option 2 $\hat{S}_S = \hat{V}_s \cdot \hat{I}_S^* = 62.15 \angle 36.83^\circ \text{ kVA}$

angle of combined loads

$\text{PF}_{1,2,3} = \cos(36.83) = 0.8 \text{ lagging}$

Example Power factor Problem

pg 4

$$f) |\hat{I}_S| = |\hat{I}_1 + \hat{I}_2 + \hat{I}_3| = |414.34 \angle -36.83|$$

$$= 414.34 \text{ Arms}$$

note: $|\hat{I}_S| \neq |\hat{I}_1| + |\hat{I}_2| + |\hat{I}_3|$

g) the larger the power factor of the combined loads, the smaller the source current magnitude.

Note $P_S = V_S I_S \cdot PF_{CL}$, where $PF_{CL} = Z_1 || Z_2 || Z_3 || Z_C$


$$I_S = \frac{P_S}{V_S \cdot PF_{CL}}$$

↑
Corrective load

when $PF_{CL} = 1$, I_S is minimized.

$$I_S = \frac{49.75 \text{ kW}}{150} = 331.67 \text{ Arms}$$

h) new ckt diagram

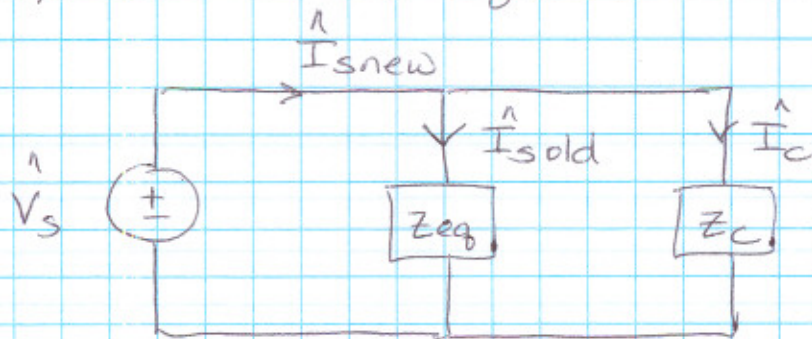

$$P_S = 49.75 \text{ kW}$$

$$\hat{I}_{Sold} = 414.34 \angle -36.83^\circ \text{ Arms}$$

$$PF_{CL} = 0.952 \text{ lag}$$

↑ power factor of all 4 loads

$$\angle Z_C = \cos^{-1}(0.952) = 17.82^\circ$$

$$I_{Snew} = \frac{P_S}{V_S \cdot PF_{CL}} = \frac{49.75 \times 10^3}{(150)(0.952)} = 348.39^\circ \text{ Arms}$$

$$\hat{I}_{Snew} = 348.39 \angle -17.82^\circ \text{ Arms}$$

Example Power Factor Problem

pg 5

h) cont

$$\hat{I}_{s\text{new}} = \hat{I}_{s\text{old}} + \hat{I}_c \quad \text{so } \hat{I}_c = 141.76 \angle 90^\circ \text{ Arms}$$

$$\hat{Z}_c = \frac{\hat{V}_s}{\hat{I}_c} = 1.06 \angle -90^\circ \Omega$$

$$\frac{1}{\omega C} = 1.06 \quad \omega = 2\pi(60) \approx 377 \text{ rad/s}$$

$$C = 2.51 \text{ mF}$$

$$|\hat{I}_{s\text{new}}| = 348.39 \text{ Arms}$$