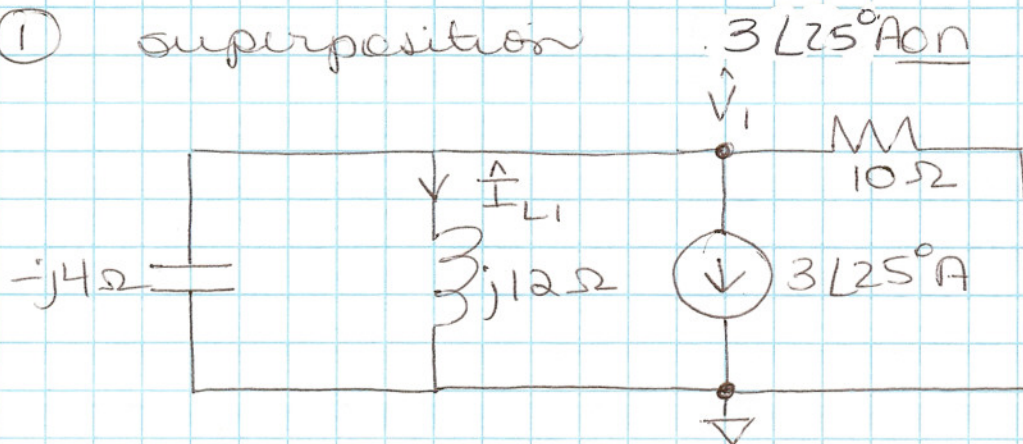


Problem Set #2 - solutions

pg 1

① superposition




$$\hat{I}_{L1} = \frac{\hat{V}_1}{j12}$$

$$\frac{\hat{V}_1}{-j4} + \frac{\hat{V}_1}{j12} + \frac{\hat{V}_1}{10} + 3\angle 25^\circ = 0$$

$$\hat{V}_1 = 15.43\angle 145.96^\circ V$$
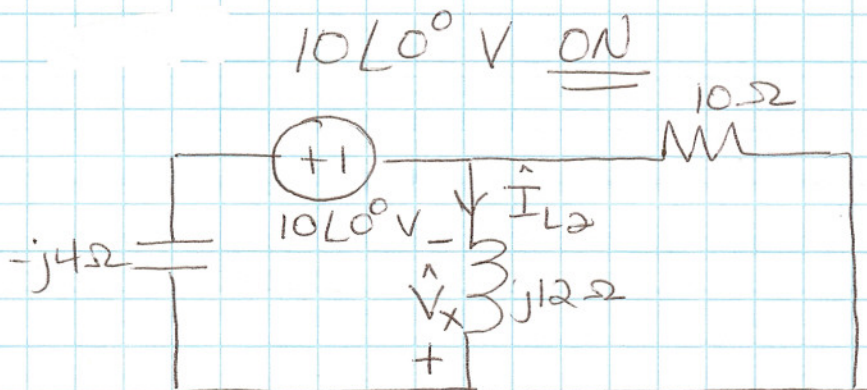
$$\hat{I}_{L1} = 1.28\angle 55.96^\circ A$$



by voltage division

$$\hat{V}_x = \frac{10\angle 0^\circ \cdot (j12\parallel 10)}{-j4 + (j12\parallel 10)}$$

$$\hat{I}_{L2} = \frac{-\hat{V}_x}{j12} = 1.07\angle 120.96^\circ A$$

$$= 12.86\angle 30.96^\circ V$$


$$\hat{I}_{L1} + \hat{I}_{L2} = \hat{I}_L = 1.99\angle 85.15^\circ A$$

Problem set 2

pg 2

① cont using Thw. Equiv. Ckt.

Find $\hat{V}_{oc}$

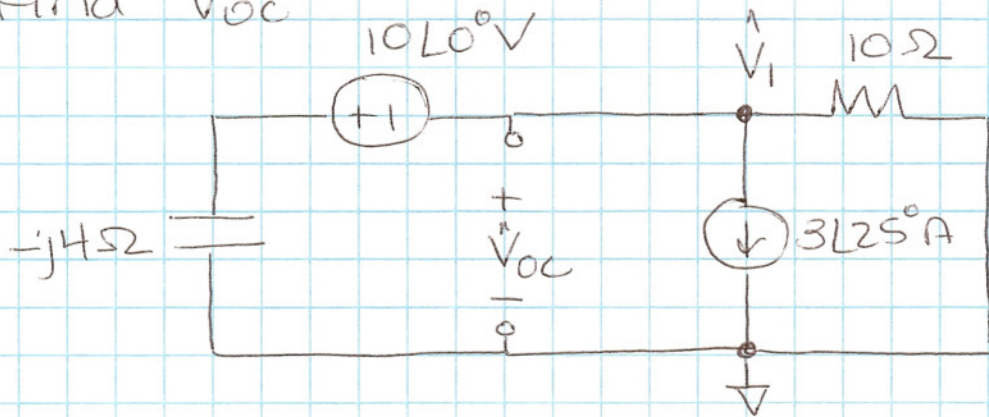


$$\hat{V}_1 = \hat{V}_{oc}$$

$$\frac{\hat{V}_1 + 10\angle 0}{-j4} + (3\angle 25) + \frac{\hat{V}_1}{10} = 0 \quad \hat{V}_1 = 17.26 \angle 165.99^\circ \text{ V}$$


$$\hat{V}_{TH} = \hat{V}_{oc} = 17.26 \angle 165.99^\circ \text{ V}$$

Find Z_{TH} (use quick method)

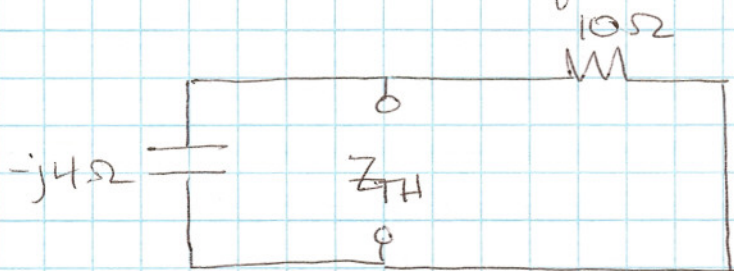

$$Z_{TH} = 10 \parallel -j4 = 3.71 \angle -68.20^\circ \Omega$$

check find $\hat{I}_{sc}$

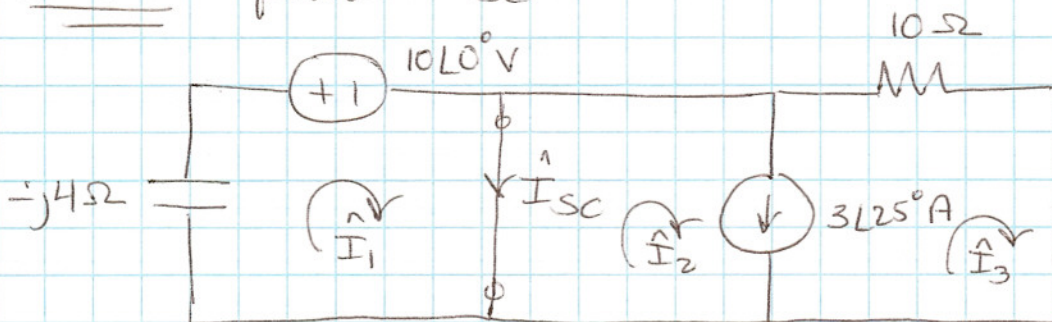

know: $\hat{I}_3 = 0$
 $\hat{I}_2 - \hat{I}_3 = 3\angle 25^\circ$
 $\hat{I}_2 = 3\angle 25^\circ$
 $\hat{I}_{sc} = \hat{I}_1 - \hat{I}_2$


$$m1: -(10\angle 0) - (-j4)\hat{I}_1 = 0 \quad \hat{I}_1 = 2.5 \angle 90^\circ$$

$$\hat{I}_{sc} = 4.65 \angle -125.81^\circ \text{ A}$$

$$\frac{\hat{V}_{oc}}{\hat{I}_{sc}} = 3.71 \angle -68.20^\circ \Omega$$

checks ☺


① cont

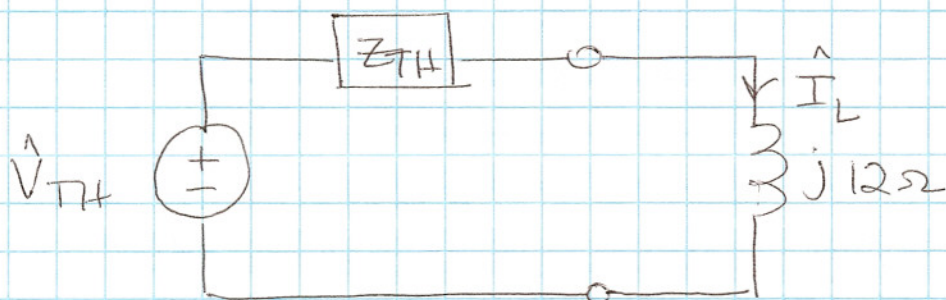

$$\hat{I}_L = \frac{\hat{V}_{TH}}{Z_{TH} + j12} = 1.99 \angle 85.14^\circ \text{ A}$$

checks w/ superposition
😊

Average Power

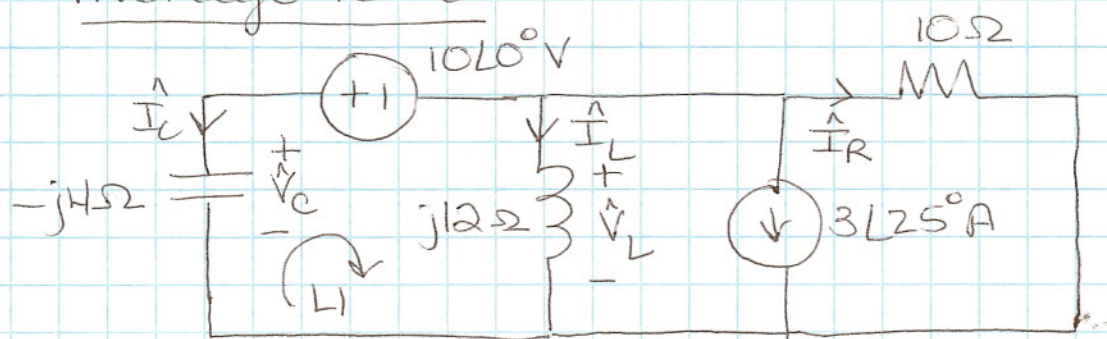

for $\hat{I}_L = 1.99 \angle 85.15^\circ \text{ A}$ $\hat{V}_L = j12 \hat{I}_L = 23.91 \angle 175.15^\circ \text{ V}$

by KVL at loop 1: $\hat{V}_C - 10 \angle 0^\circ - \hat{V}_L = 0$ $\hat{V}_C = 13.97 \angle 171.67^\circ$

$\hat{I}_R = \hat{V}_L / 10 = 2.39 \angle 175.15^\circ \text{ A}$ $\hat{I}_C = \frac{\hat{V}_C}{-j4} = 3.49 \angle -98.32^\circ$

element

P average

Del / Abs

-j4 ohm

0 W

—

j12 ohm

0 W

—

10 ohm

$$\frac{1}{2} (2.39)^2 (10) = 28.56 \text{ W}$$

Abs

10V source

$$P = \frac{1}{2} (10) (3.49) \cos(0 - (-98.32))$$

$$= -2.53 \text{ W}$$

Del

3A source

$$P = \frac{1}{2} (23.91) (3) \cos(175.15^\circ - 25^\circ)$$

$$= -31.11 \text{ W}$$

Abs

① cont

pg 4


$$\Sigma P_{del} = -2.53 \text{ W}$$

$$\Sigma P_{abs} = 28.56 + (-31.11) = -2.54 \text{ W}$$

agrees!

② superposition

$10\angle 0^\circ$ ON

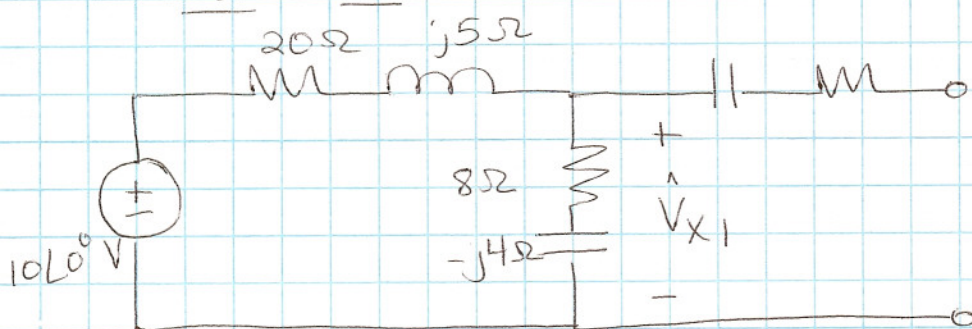


by voltage division


$$\hat{V}_{x1} = \frac{10\angle 0^\circ (8-j4)}{(8-j4) + (20+j5)}$$

$$\hat{V}_{x1} = 3.19 \angle -28.61^\circ \text{ V}$$

$3\angle -115^\circ$ ON

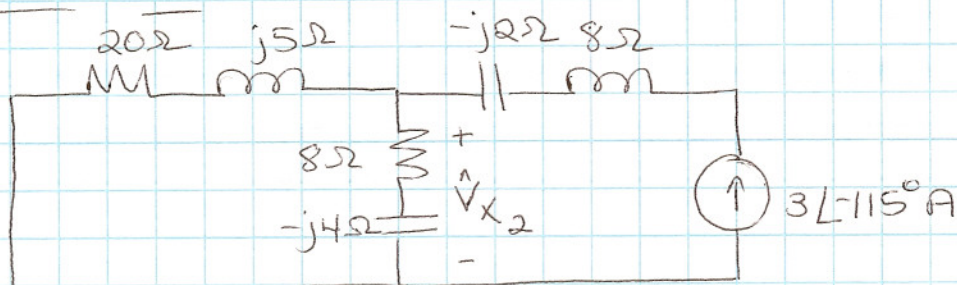

simplify

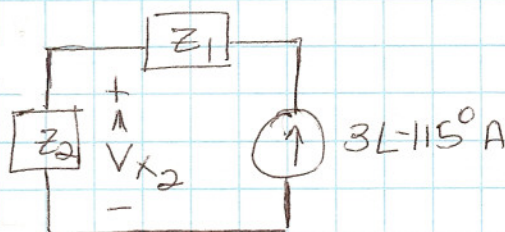

$$Z_1 = 8-j2\Omega$$

$$Z_2 = (20+j5) \parallel (8-j4) = 6.58 \angle -14.57^\circ \Omega$$


$$\hat{V}_{x2} = (3\angle -115^\circ)(Z_2) = 19.74 \angle -129.57^\circ \text{ V}$$

$$\hat{V}_x = \hat{V}_{x1} + \hat{V}_{x2} = 19.39 \angle -120.27^\circ \text{ V}$$

② cont : Thw.

pg 5


Find $\hat{V}_{oc}$

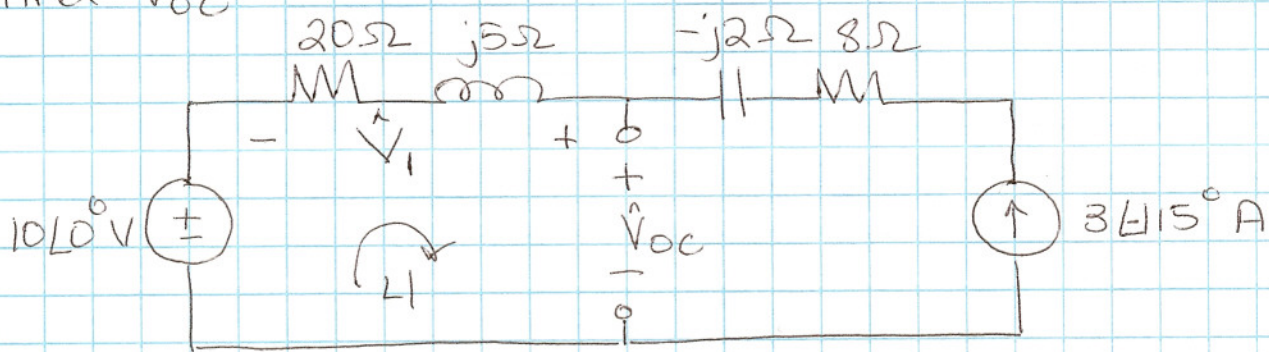

$$\hat{V}_1 = (3\angle-115^\circ)(20+j5) = 61.85\angle-100.96^\circ \text{ V}$$


KVL at L1 : $10\angle 0 + \hat{V}_1 - \hat{V}_{oc} = 0$
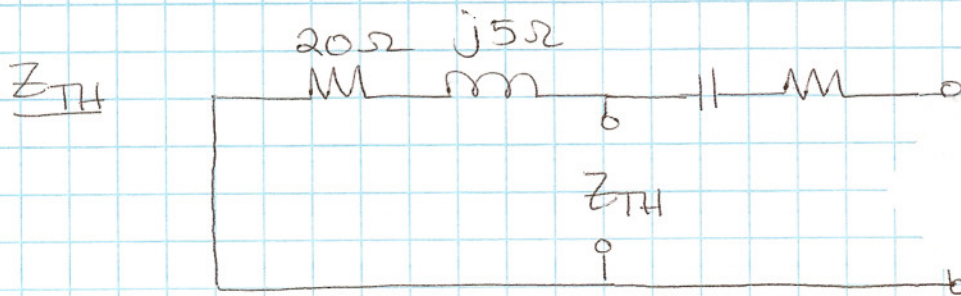
$$\hat{V}_{oc} = 60.74\angle-91.66^\circ \text{ V}$$



$$\underline{Z_{TH} = 20 + j5 \Omega \text{ or } 20.62\angle14.04^\circ \Omega}$$

Find $\hat{I}_{sc}$ to check

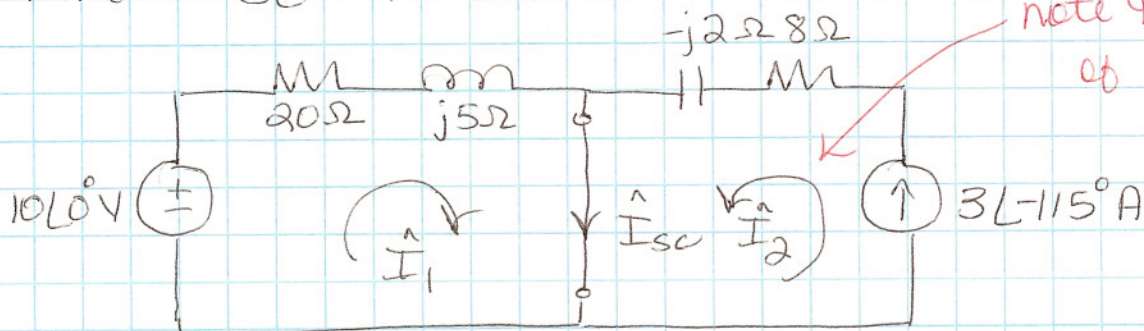

$$\hat{I}_2 = 3\angle-115^\circ \text{ A}$$

$$\hat{I}_{sc} = \hat{I}_1 + \hat{I}_2$$

m1 : $10\angle 0 - (20+j5)\hat{I}_1 = 0$

$$\hat{I}_1 = 0.485\angle-14.04^\circ \text{ A}$$

$$\boxed{\hat{I}_{sc} = 2.95\angle-105.70^\circ \text{ A}}$$


$$Z_{TH} = \frac{\hat{V}_{oc}}{\hat{I}_{sc}} = 20.5\angle14.04^\circ \text{ } \text{checks}$$

(2) cont

pg 6

~~Power~~

Equivalent ckt

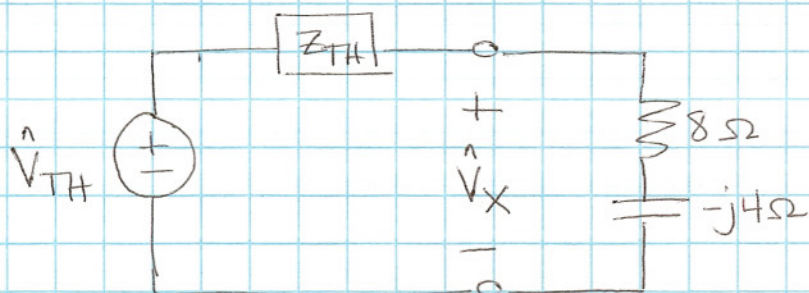


$$\hat{V}_X = \hat{V}_{TH} \cdot \frac{8-j4}{(8-j4)+Z_{TH}}$$

$$\hat{V}_X = 19.39 \angle -120.27^\circ \text{ V}$$

checks w/ superposition

Power

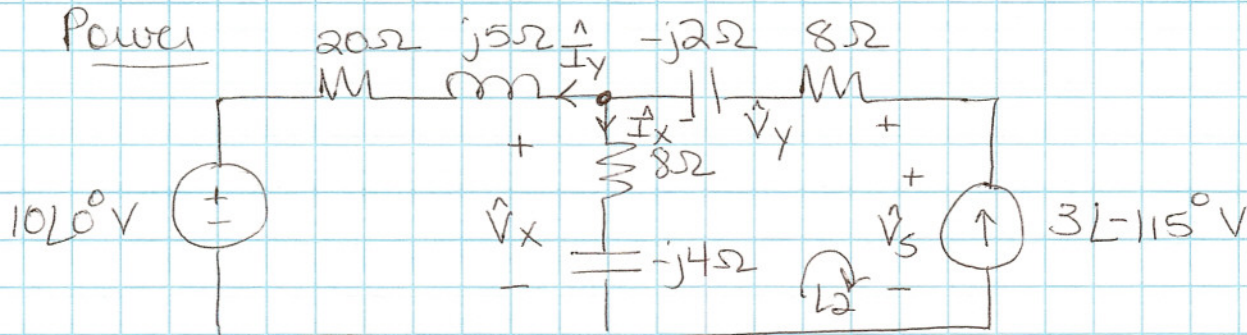

$$\hat{V}_X = 19.39 \angle -120.27^\circ \text{ V} \quad \hat{I}_X = \frac{\hat{V}_X}{8-j4} = 2.17 \angle -93.70^\circ \text{ A}$$

by KCL: $3 \angle -115^\circ = \hat{I}_X + \hat{I}_Y$

$$\hat{I}_Y = 1.26 \angle -153.77^\circ \text{ A}$$

$$\hat{V}_Y = (3 \angle -115^\circ)(8-j2) = 24.74 \angle -129.04^\circ \text{ V}$$

by KVL (LI) $\hat{V}_X + \hat{V}_Y - \hat{V}_S = 0$

$$\hat{V}_S = 44.00 \angle -125.15^\circ \text{ V}$$

element

Power (W)

Del/Abs

j5 ohm
-j2 ohm
-j4 ohm

0
0
0

-
-
-

20 ohm

$$P = \frac{1}{2} (20)(1.26)^2 = 15.88 \text{ W}$$

Abs

8 ohm (middle)

$$P = \frac{1}{2} (8)(2.17)^2 = 18.84 \text{ W}$$

Abs

8 ohm (right)

$$P = \frac{1}{2} (8)(3)^2 = 36 \text{ W}$$

Abs

10 L 0 degree V

$$P = \frac{1}{2} (10)(1.26) \cos(0 + 153.77^\circ)$$

$$P = -5.65 \text{ W abs}$$

OR

$$P = 5.65 \text{ W Del}$$

②

element

Power

Del / Abs


$$3\angle -115^\circ \text{ A}$$

$$P = \frac{1}{2}(44)(3)\cos(-125.14 + 115) \\ = 64.69 \text{ W, del}$$

$$\Sigma P_{\text{del}} = 64.69 + 5.65 = 70.34 \text{ W}$$

$$\Sigma P_{\text{abs}} = 15.88 + 18.84 + 36 = 70.72 \text{ W} \quad \text{OK}$$

③ see work on Probs 1 & 2.

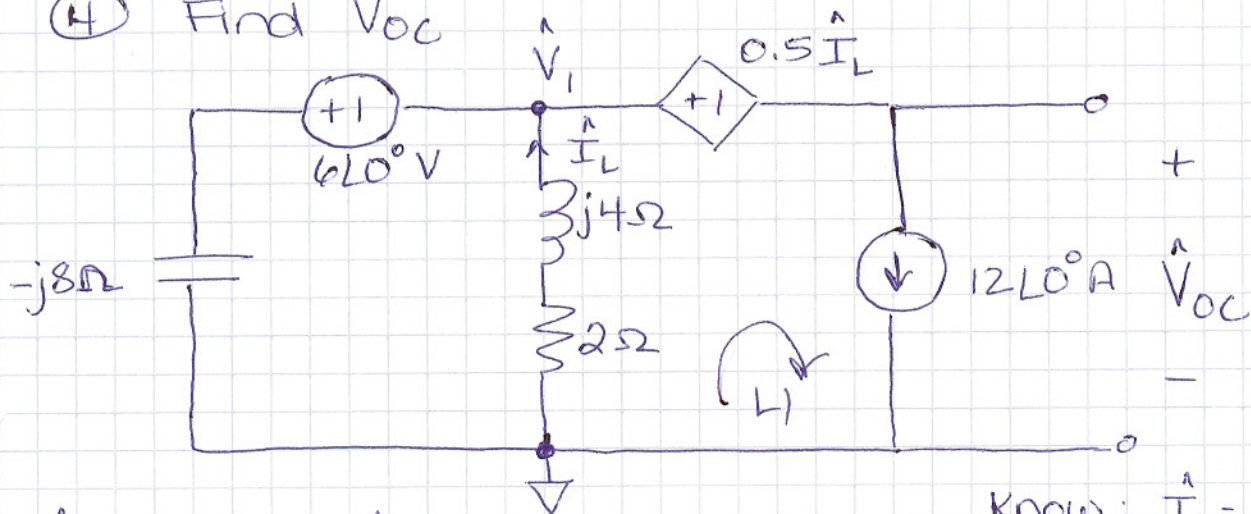④ Find $\hat{V}_{oc}$ 

$$\text{Know: } \hat{I}_L = \frac{-\hat{V}_1}{2+j4}$$

$$\frac{\hat{V}_1 + 6\angle 0}{-j8} + \frac{\hat{V}_1}{2+j4} + 12\angle 0 = 0$$

$$\hat{V}_1 \left(\frac{1}{-j8} + \frac{1}{2+j4} \right) = \frac{6\angle 0}{j8} - 12\angle 0$$

$$\hat{V}_1 = 96.19\angle -139.55^\circ \text{ V}$$


$$\hat{I}_L = 21.51\angle -22.99^\circ \text{ A}$$

$$\text{By KVL around } L1: \hat{V}_1 - 0.5\hat{I}_L - \hat{V}_{oc} = 0$$

$$\hat{V}_{oc} = 101.45\angle -144.99^\circ \text{ V}$$

④ cont

p8

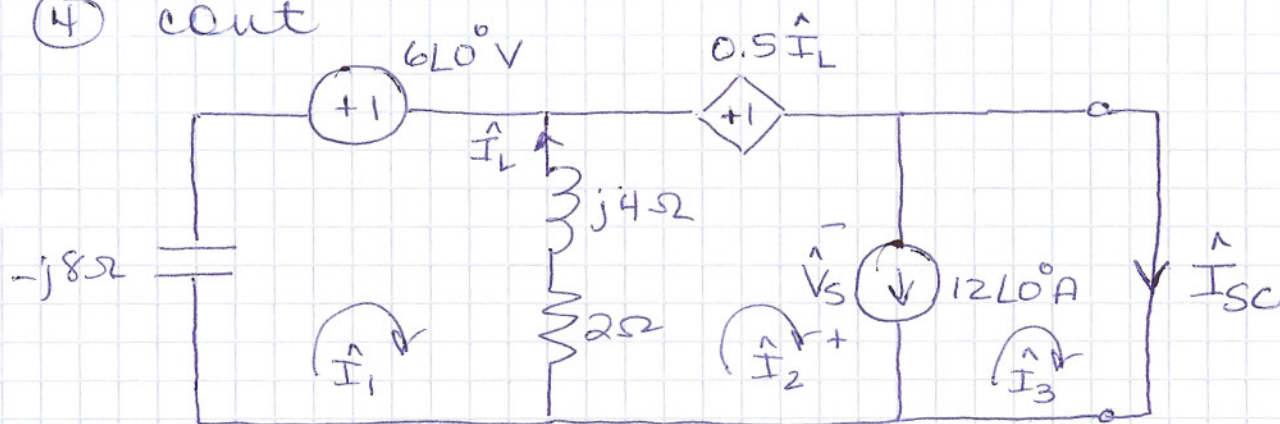

Know $\hat{I}_L = \hat{I}_2 - \hat{I}_1$ $\hat{I}_2 - \hat{I}_3 = 12\angle 0^\circ$
 $\hat{V}_S = 0$ $\hat{I}_3 = \hat{I}_{SC}$

m1: $-(-j8)\hat{I}_1 - 6\angle 0 - (2+j4)(\hat{I}_1 - \hat{I}_2) = 0$

m2: $-(2+j4)(\hat{I}_2 - \hat{I}_1) - 0.5\hat{I}_L + \hat{V}_S = 0$

m1 $\boxed{\hat{I}_1(-2+j4) + \hat{I}_2(2+j4) = 6\angle 0}$

m2 $-(2+j4)(\hat{I}_2 - \hat{I}_1) - 0.5(\hat{I}_2 - \hat{I}_1) = 0$

$\hat{I}_1(2.5+j4) + \hat{I}_2(-2.5-j4) = 0$

or $\boxed{\hat{I}_1 = \hat{I}_2}$

so: $\hat{I}_2(-2+j4) + \hat{I}_2(2+j4) = 6\angle 0$


$\hat{I}_2 = 0.75\angle -90^\circ \text{ A}$

$\hat{I}_3 = \hat{I}_2 - 12\angle 0 = 12.02\angle -176.42^\circ \text{ A}$

$\boxed{\hat{I}_{SC} = 12.02\angle -176.42^\circ \text{ A}}$

$Z_{TH} = \frac{\hat{V}_{OC}}{\hat{I}_{SC}} = \cancel{8.44} 8.44\angle 31.42^\circ$

④

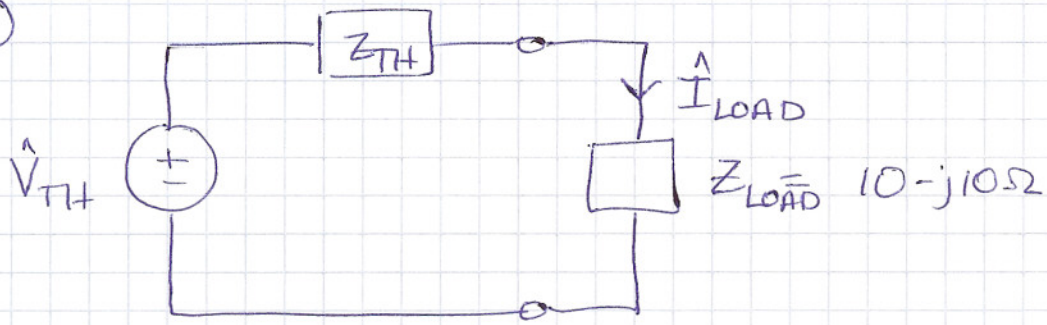


~~$$\hat{I}_{LOAD} = \frac{\hat{V}_{TH}}{Z_{TH} + Z_{LOAD}}$$~~

$$\hat{I}_{LOAD} = \frac{\hat{V}_{TH}}{Z_{TH} + Z_{LOAD}} = 5.61 \angle -126.96^\circ \text{ A}$$

$$P_{LOAD} = \frac{1}{2} (10) (5.61)^2$$

$$= 157.36 \text{ W, abs}$$

④ check

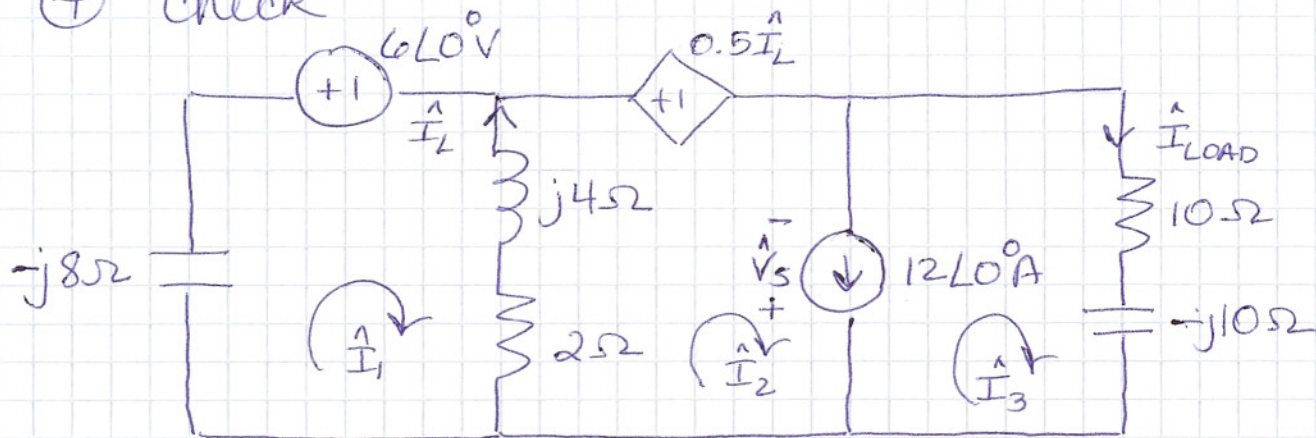

know: $\hat{I}_L = \hat{I}_2 - \hat{I}_1$ $\hat{I}_{LOAD} = \hat{I}_3$
 $12\angle 0 = \hat{I}_2 - \hat{I}_3$

m1: $-(-j8)\hat{I}_1 - 6\angle 0 - (2+j4)(\hat{I}_1 - \hat{I}_2) = 0$

m2: $-(2+j4)(\hat{I}_2 - \hat{I}_1) - 0.5\hat{I}_L + \hat{V}_S = 0$

m3: $-\hat{V}_S - (10-j10)\hat{I}_3 = 0$

m1: $\hat{I}_1(-2+j4) + \hat{I}_2(2+j4) = 6\angle 0$

add m2 & m3 $-(2+j4)(\hat{I}_2 - \hat{I}_1) - 0.5(\hat{I}_2 - \hat{I}_1) - (10-j10)\hat{I}_3 = 0$

$\hat{I}_1(2.5+j4) + \hat{I}_2(-2.5-j4) + \hat{I}_3(-10+j10) = 0$

$\hat{I}_2 - \hat{I}_3 = 12\angle 0$

$$\begin{bmatrix} -2+j4 & 2+j4 & 0 \\ 2.5+j4 & -2.5-j4 & -10+j10 \\ 0 & 1 & -1 \end{bmatrix} \begin{bmatrix} \hat{I}_1 \\ \hat{I}_2 \\ \hat{I}_3 \end{bmatrix} = \begin{bmatrix} 6\angle 0 \\ 0 \\ 12\angle 0 \end{bmatrix}$$

$\hat{I}_1 = 8.67\angle 104.63^\circ \text{ A}$

$\hat{I}_2 = 9.72\angle -27.45^\circ \text{ A}$

$\hat{I}_3 = 5.61\angle -126.95^\circ \text{ A}$

$\hat{I}_L = 16.81\angle -49.96^\circ \text{ A}$

$\hat{V}_S = 79.34\angle 8.05^\circ \text{ V}$

$P_{LOAD} = \frac{1}{2}(10)(5.61)^2 = 157.36 \text{ W, abs}$

$2\Omega: P = \frac{1}{2}(2)(16.81)^2 = 282.58 \text{ W, abs}$

$6\angle 0: P = \frac{1}{2}(6)(8.67)\cos(0-104.63) = -6.57 \text{ W, abs}$

$12\angle 0: P = \frac{1}{2}(79.34)(12)\cos(8.05-0) = 471.35 \text{ W, del}$

$0.5\hat{I}_L: P = \frac{1}{2}(8.40)(9.72)\cos(-49.96+27.45) = 37.71 \text{ W, abs}$

$\Sigma P_{abs} =$