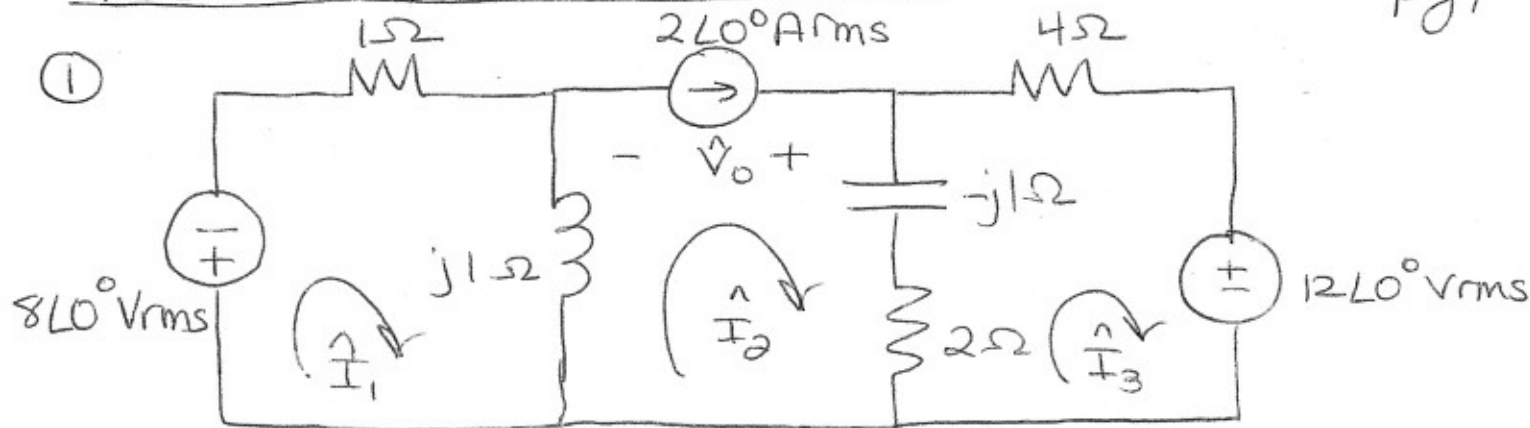


Problem Set 3 - Solutions

EE 313
Pg 1



Know: $\hat{I}_2 = 2\angle 0^\circ \text{ Arms}$

$$m1: -8\angle 0^\circ - 1\hat{I}_1 - j1(\hat{I}_1 - \hat{I}_2) = 0$$

$$m2: -(j1)(\hat{I}_2 - \hat{I}_1) + \hat{V}_0 - (2 - j1)(\hat{I}_2 - \hat{I}_3) = 0$$

$$m3: -(2 - j1)(\hat{I}_3 - \hat{I}_2) - 4\hat{I}_3 - 12\angle 0^\circ = 0$$

Simplify: (m1) $(-1 - j1)(\hat{I}_1) = 8\angle 0^\circ - j1(\hat{I}_2)$

$$(-1 - j1)\hat{I}_1 = 8.25\angle -14.04^\circ$$

$$\boxed{\hat{I}_1 = 5.83\angle 120.96^\circ \text{ Arms}}$$

(m3) $\hat{I}_3(-6 + j1) = 12\angle 0^\circ - (2 - j1)(\hat{I}_2)$

$$\boxed{\hat{I}_3 = 1.36\angle -156.50^\circ \text{ Arms}}$$

(m2) $\hat{V}_0 = j1(\hat{I}_2 - \hat{I}_1) + (2 - j1)(\hat{I}_2 - \hat{I}_3)$

$$\boxed{\hat{V}_0 = 12.37\angle 13.26^\circ \text{ Vrms}}$$

① cont

$$\begin{aligned}
 8\angle 0^\circ V_{rms} : P &= V_{rms} I_{rms} \cos(\theta - \phi) \\
 &= 8(5.83) \cos(0 - 120.96^\circ) \\
 \boxed{P &= -24 \text{ W, Abs}}
 \end{aligned}$$

$$\begin{aligned}
 Q &= V_{rms} I_{rms} \sin(\theta - \phi) \\
 &= 8(5.83) \sin(-120.96^\circ) \\
 \boxed{Q &= -40 \text{ VAR, Abs}}
 \end{aligned}$$

$$\begin{aligned}
 \hat{S} &= (8\angle 0^\circ)(\hat{I}_1)^* \\
 &= (8\angle 0^\circ)(5.83\angle -120.96^\circ) \\
 \boxed{\hat{S} &= 46.64\angle -120.96^\circ \text{ VA, Abs}}
 \end{aligned}$$

$$\begin{aligned}
 1\Omega : P &= |\hat{I}_1|^2 \cdot 1 = (5.83)^2(1) = 34 \text{ W, Abs} \\
 Q &= 0 \text{ VAR} \\
 \hat{S} &= 34\angle 0^\circ \text{ VA}
 \end{aligned}$$

$$\begin{aligned}
 j1\Omega : P &= 0 \text{ W} \\
 Q &= 1(|\hat{I}_1 - \hat{I}_2|)^2 = 1(7.07)^2 = 50 \text{ VAR, Abs} \\
 \hat{S} &= 50\angle 90^\circ \text{ VA abs}
 \end{aligned}$$

$$\begin{aligned}
 2\angle 0^\circ A_{rms} : P &= V_o \cdot 2 \cdot \cos(\theta - \phi) \\
 &= (12.37)(2) \cos(13.26^\circ) \\
 \boxed{P &= 24.08 \text{ W, Del}}
 \end{aligned}$$

$$\begin{aligned}
 \hat{S} &= (12.37\angle 13.26^\circ)(2\angle 0^\circ) \\
 &= 24.74\angle 13.26^\circ \text{ VA Del}
 \end{aligned}$$

$$Q = (12.37)(2) \sin(13.26^\circ)$$

$$Q = 5.67 \text{ VAR, Del}$$

$$Q = 0 \text{ VAR}$$

$$\hat{S} = 21.68\angle 0^\circ \text{ VA, Abs}$$

$$\begin{aligned}
 2\Omega : P &= 2(|\hat{I}_2 - \hat{I}_3|)^2 \\
 &= 2(3.29)^2 \\
 &= 21.68 \text{ W, Abs}
 \end{aligned}$$

(1) cont

$$\begin{aligned}
 -j1\Omega: \quad P &= 0 \text{ W} \\
 Q &= -1(|\hat{I}_2 - \hat{I}_3|)^2 \\
 &= -1(3.29)^2 \\
 &= -10.82 \text{ VAR, Abs}
 \end{aligned}$$

$$\hat{S} = 10.82 \angle -90^\circ \text{ VA}$$

$$\begin{aligned}
 12\angle 0^\circ \text{ Vrms}: \quad P &= 12 I_3 \cos(0 + 156.50) \\
 &= 12(1.36) \cos(156.50) \\
 P &= -14.97 \text{ W, Abs}
 \end{aligned}$$

$$\begin{aligned}
 Q &= 12 I_3 \sin(156.50) & \hat{S} &= (12\angle 0)(1.36\angle 156.50) \\
 Q &= 6.51 \text{ VAR, Abs} & &= 16.32 \angle 156.50^\circ \text{ VA, Abs}
 \end{aligned}$$

$$4\Omega: \quad P = 4|\hat{I}_3|^2 = 4(1.36)^2 = 7.40 \text{ W, Abs}$$

$$Q = 0 \text{ VAR, Abs}$$

$$\hat{S} = 7.40 \angle 0^\circ \text{ VA, Abs}$$

$$\sum P_{\text{del}} = 24.08 \text{ W}$$

$$\sum Q_{\text{del}} = 5.67 \text{ VAR}$$

$$\sum \hat{S}_{\text{del}} = 24.74 \angle 13.26^\circ \text{ VA}$$

checks ☺

$$\sum P_{\text{abs}} = -24 + 34 + 21.68 - 14.97 + 7.40$$

$$\boxed{\sum P_{\text{abs}} = 24.11 \text{ W}}$$


$$\sum Q_{\text{abs}} = -40 + 50 - 10.82 + 6.51$$

$$\boxed{\sum Q_{\text{abs}} = 5.69 \text{ VAR}}$$

$$\begin{aligned}
 \sum \hat{S}_{\text{abs}} &= (46.64 \angle -120.96^\circ) + (34\angle 0) + (50\angle 90) + (21.68\angle 0) \\
 &\quad + 10.82 \angle -90 + 16.32 \angle 156.50 + 7.40 \angle 0
 \end{aligned}$$

$$\boxed{\hat{S}_{\text{abs}} = 24.78 \angle 13.28^\circ \text{ VA}}$$

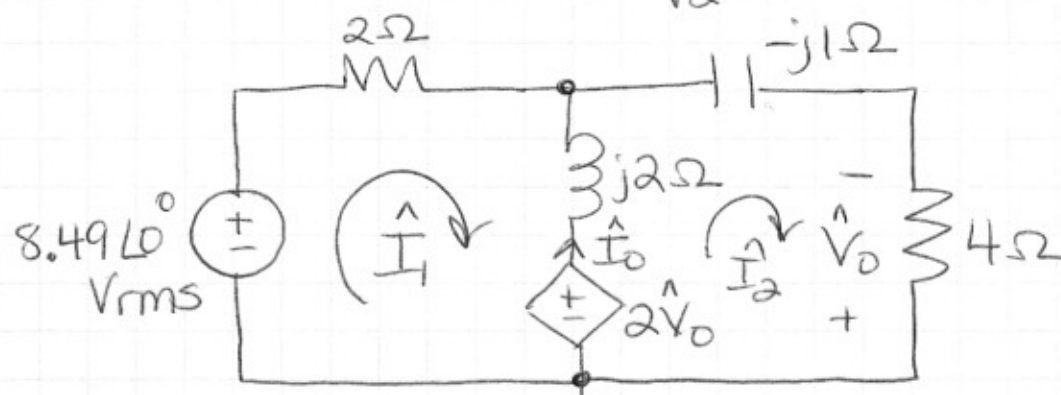(2) $V_m = 12$ $V_{rms} = \frac{12}{\sqrt{2}} = 8.49 \text{ V}_{rms}$



$$\hat{V}_0 = -4\hat{I}_2$$

(note: $\hat{I}_2$ labelled $\hat{I}_0$)

$$m1: 8.49\angle 0^\circ - 2\hat{I}_1 - j2(\hat{I}_1 - \hat{I}_2) - 2\hat{V}_0 = 0$$

$$m2: 2\hat{V}_0 - j2(\hat{I}_2 - \hat{I}_1) - (-j1)\hat{I}_2 - 4\hat{I}_2 = 0$$

$$m1: \hat{I}_1(-2 - j2) + \hat{I}_2(8 + j2) = 8.49\angle 180^\circ$$

$$m2: \hat{I}_1(j2) + \hat{I}_2(-12 - j1) = 0$$

$$\hat{I}_1 = 3.67\angle -16.27^\circ \text{ Arms}$$

$$\hat{V}_0 = 2.44\angle -111.04^\circ \text{ V}_{rms}$$

$$\hat{I}_2 = 0.61\angle 68.96^\circ \text{ Arms}$$

power

$$\begin{array}{l|l} 2\Omega: P = |\hat{I}_1|^2 \cdot 2 = 26.94 \text{ W, Abs} & 4\Omega: P = |\hat{I}_2|^2 \cdot 4 = 1.49 \text{ W, Abs} \\ Q = 0 & Q = 0 \\ \hat{S} = 26.94\angle 0^\circ \text{ VA, Abs} & \hat{S} = 1.49\angle 0^\circ \text{ VA, Abs} \end{array}$$

$$\begin{array}{l} -j1\Omega: P = 0 \\ Q = -1|\hat{I}_2|^2 = -0.37 \text{ VAR, Abs} \\ \hat{S} = 0.37\angle -90^\circ \text{ VA, Abs} \end{array}$$

$$\begin{array}{l} j2\Omega: P = 0 \text{ W} \quad | \quad Q = 2(|\hat{I}_2 - \hat{I}_1|)^2 = 2(3.67)^2 = 26.94 \text{ VAR} \\ \hat{S} = 26.94\angle 90^\circ \text{ VA, Abs} \end{array}$$

(2) cont

$$2\hat{V}_0: \text{ need net current, } \hat{I}_0 = \hat{I}_2 - \hat{I}_1$$

$$= 3.67 \angle 154.19^\circ \text{ Arms}$$

$$P = V_{rms} I_{rms} \cos(\theta - \phi)$$

$$= (|2\hat{V}_0|)(|\hat{I}_0|) \cos(-111.04 - 154.19)$$

$$= (4.88)(3.67) \cos(-265.23)$$

$$P = -1.46 \text{ W, Del}$$

$$Q = (|2\hat{V}_0|)(|\hat{I}_0|) \sin(\theta - \phi)$$

$$= (4.88)(3.67) \sin(-265.23)$$

$$Q = 17.55 \text{ VAR, Del}$$

$$\hat{S} = (2\hat{V}_0)(\hat{I}_0^*) = (4.88 \angle -111.04)(3.67 \angle -154.19)$$

$$\hat{S} = 17.91 \angle -265.23^\circ \text{ VA, Del}$$

$$8.49 \angle 0^\circ \text{ Vrms: } P = (8.49)(3.67) \cos(0 - (-16.27))$$

$$= 29.91 \text{ W, Del}$$

$$Q = (8.49)(3.67) \sin(16.27)$$

$$= 8.73 \text{ VAR, Del}$$

$$\hat{S} = (8.49 \angle 0)(3.67 \angle -16.27)^*$$

$$= (8.49 \angle 0)(3.67 \angle 16.27)$$

$$= 31.16 \angle 16.27^\circ \text{ VA, del}$$

check P


$$\Sigma P_{del} = 29.91 - 1.46 = 28.45 \text{ W} \quad \text{checks } \smile$$

$$\Sigma P_{abs} = 26.94 + 1.49 = 28.43 \text{ W}$$

PS #3 solutions

EE 313

pg 6

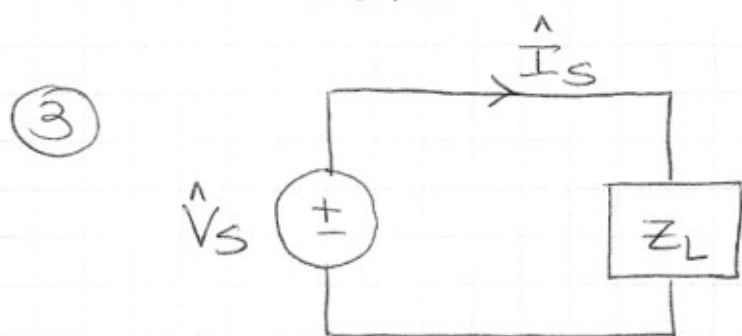

$$\hat{V}_s = 220 \angle 0^\circ \text{ Vrms}$$

$$Z_L: P_L = 44 \text{ kW}$$

$$PF_L = 0.500 \text{ lagging}$$

a) $P_L = V_s I_s \cdot PF_L$

$$44 \times 10^3 = 220 \cdot I_s \cdot 0.5$$


$$\angle Z_L = \cos^{-1}(0.5)$$

$$= 60^\circ$$

$$I_s = 400 \text{ Arms}$$

$$\hat{I}_s = 400 \angle -60^\circ \text{ Arms}$$
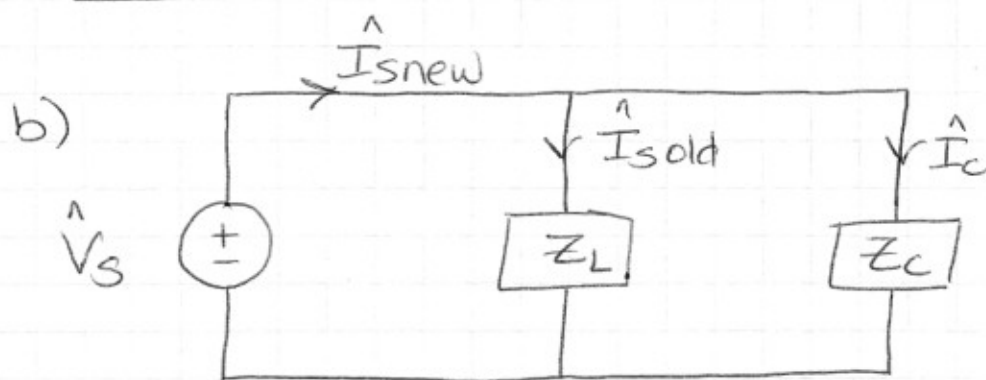
$$Z_L = \frac{\hat{V}_s}{\hat{I}_s} = 0.55 \angle 60^\circ \Omega$$



$$P_S = P_L = 44 \text{ kW}$$

$$PF_{CL} = 0.988 \text{ lag}$$

$$\hat{I}_{\text{sold}} = 400 \angle -60^\circ \text{ Arms}$$

$$\hat{V}_s = 220 \angle 0^\circ \text{ Vrms}$$

$$\angle Z_{CL} = \cos^{-1}(0.988) = 8.89^\circ$$

$$P_S = V_s \cdot I_{\text{snew}} \cdot PF_{CL}$$

$$44 \times 10^3 = 220 \cdot I_{\text{snew}} \cdot 0.988$$

$$I_{\text{snew}} = 202.43 \text{ Arms}$$

$$\hat{I}_{\text{snew}} = 202.43 \angle 8.89^\circ$$

$$\hat{I}_C = \hat{I}_{\text{snew}} - \hat{I}_{\text{sold}}$$


$$= 315.13 \angle 90^\circ \text{ Arms}$$

$$Z_C = \frac{\hat{V}_s}{\hat{I}_C}$$

$$Z_C = 0.70 \angle -90^\circ \Omega$$

PS#3 solutions

EE313
pg 7

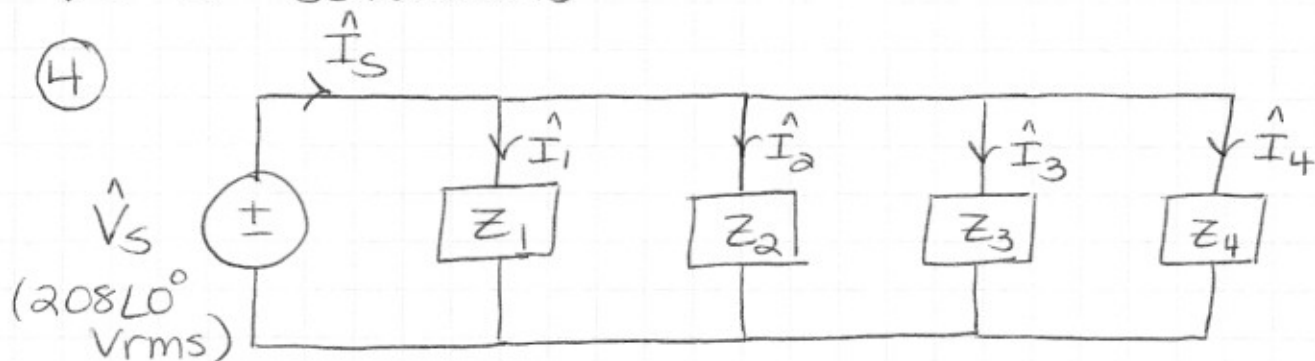

$$P_1 = 18 \text{ kW}$$

$$\text{PF}_1 = 0.5 \text{ lag}$$

$$|\hat{S}_2| = 10 \text{ kVA}$$

$$\text{PF}_2 = 0.2 \text{ lag}$$

$$P_3 = 12 \text{ kW}$$

$$\text{PF}_3 = 1$$

$$Q_4 = 16 \text{ kVAR}$$

$$\text{PF}_4 = 0.3 \text{ lag}$$

a) Load 1 : $P_1 = V_s I_1 \text{PF}_1$

$$\angle Z_1 = \cos^{-1}(0.5) \quad 18 \times 10^3 = 208 I_1 (0.5)$$

$$\angle Z_1 = 60^\circ \quad I_1 = 173.08 \text{ Arms}$$

$$\hat{I}_1 = 173.08 \angle -60^\circ \text{ Arms}$$

$$\boxed{Z_1 = \hat{V}_s / \hat{I}_1 = 1.20 \angle 60^\circ \Omega}$$

Load 2 : $|\hat{S}_2| = V_s I_2 \quad 10 \times 10^3 = (208) I_2$

$$\angle Z_2 = \cos^{-1}(0.2)$$

$$= 78.46^\circ$$

$$I_2 = 48.08 \text{ Arms}$$

$$|Z_2| = \frac{V_s}{I_2} = \frac{208}{48.08} = 4.33 \Omega$$

$$\hat{I}_2 = 48.08 \angle -78.46^\circ \text{ Arms}$$

$$\boxed{Z_2 = 4.33 \angle 78.46^\circ \Omega}$$

Load 3 : $\text{PF} = 1$ purely resistive load.

$$\angle Z_3 = 0^\circ \quad P_3 = V_s I_3 \cdot \text{PF}_3$$

$$12 \times 10^3 = 208 I_3$$

$$I_3 = 57.69 \text{ Arms}$$

$$|Z_3| = \frac{208}{57.69} = 3.61 \Omega$$

$$\hat{I}_3 = 57.69 \angle 0^\circ \text{ Arms}$$

$$\boxed{Z_3 = 3.61 \angle 0^\circ \Omega}$$

PS #3 - Solutions

(4) a) cont

LOAD 4: $Q_4 = V_S I_4 \cdot \sin(\angle Z_4)$

$\angle Z_4 = \cos^{-1}(0.3)$

$\angle Z_4 = 72.54^\circ$

$|Z_4| = \frac{V_S}{I_4} = 2.58 \Omega$

$16 \times 10^3 = 208 \cdot I_4 \cdot \sin(72.54^\circ)$

$I_4 = 80.64 \text{ Arms}$

$\hat{I}_4 = 80.64 \angle -72.54^\circ \text{ Arms}$

$Z_4 = 2.58 \angle 72.54^\circ \Omega$

b) we need $|\hat{I}_S|$, first find $\hat{I}_S$.

$\hat{I}_S = \hat{I}_1 + \hat{I}_2 + \hat{I}_3 + \hat{I}_4$ [note: DO NOT ADD ONLY the magnitudes!!!]

$\hat{I}_S = 326.70 \angle -56.98^\circ \text{ Arms}$

$|\hat{I}_S| \text{ or } I_S = 326.70 \text{ Arms}$

c) method 1 $P_S = V_S I_S \text{ 'PF}_S$ — PF seen by source or by all loads combined.

$P_S = P_1 + P_2 + P_3 + P_4$
 $\uparrow$ $\uparrow$
 given given

$P_2 = V_S I_2 \cdot \text{PF}_2 = (208)(48.08)(.2) = 2.00 \text{ kW}$

-or- $P_2 = |\hat{S}_2| \cdot \text{PF}_2 = 10 \times 10^3 (.2) = 2.00 \text{ kW}$

$P_4 = V_S I_4 \cdot \text{PF}_4 = (208)(80.64)(.3) = 5.03 \text{ kW}$

$P_S = 18 + 2 + 12 + 5.03$

$P_S = 37.03 \text{ kW}$

$\text{PF}_S = \frac{P_S}{V_S I_S} = \frac{37.03 \times 10^3}{(208)(326.70)}$

(4) c) method 1 cont

$$PF_S = 0.545 \text{ lagging}$$

(all loads are inductive or purely resistive. Combined the loads will be inductive)

method 2

$\hat{S}_S \equiv$ complex power delivered by source

$$\hat{S}_S = \hat{V}_S \cdot \hat{I}_S^* = (208 \angle 0)(326.70 \angle +56.98)$$

$$\hat{S}_S = 67.95 \angle 56.98^\circ \text{ kVA}$$

the angle of the complex power is the angle of the loads combined.

$$\angle Z_{CL} = \angle \hat{S}_S = 56.98 \text{ (inductive } 56.98 > 0)$$

$$PF_S = PF_{CL} = \cos(56.98)$$

$$PF_S = 0.545 \text{ lagging}$$

method 3: $Z_{CL} = \frac{\hat{V}_S}{\hat{I}_S} = \frac{208 \angle 0}{326.70 \angle 56.98}$

$$Z_{CL} = 0.64 \angle 56.98^\circ \Omega$$


$$PF_{CL} = PF_S = \cos(56.98)$$

$$PF_S = 0.545 \text{ lagging}$$

④ cont

$$d) \hat{S}_S = \hat{V}_S \cdot \hat{I}_S^* = 67.95 \angle 56.98^\circ \text{ kVA}$$

$$e) Z_C \text{ such that } |\hat{I}_{S\text{new}}| = .8 |\hat{I}_{S\text{old}}|$$

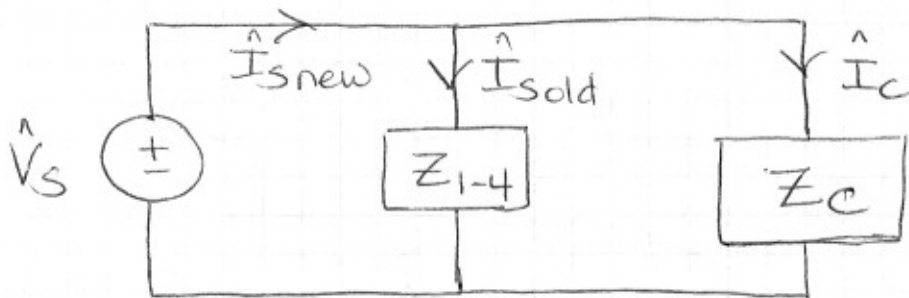

* note
we are
designing
 $\hat{I}_{S\text{new}}$ & solving
for PF_{CL}

$$\hat{I}_{S\text{old}} = 326.70 \angle -56.98^\circ \text{ Arms}$$

$$\hat{S}_S = 67.95 \angle 56.98^\circ \text{ kVA}$$

$$P_S = 37.03 \text{ kW}$$

$$\hat{V}_S = 208 \angle 0^\circ \text{ Vrms}$$

$$|\hat{I}_{S\text{new}}| = .8 (326.70) = 261.36 \text{ Arms}$$

$$P_S = V_S I_{S\text{new}} \cdot \text{PF}_{CL}$$

$$37.03 \times 10^3 = (208)(261.36) \cdot \text{PF}_{CL}$$

$$\text{PF}_{CL} = 0.681 \text{ lagging (we will choose lagging here)}$$

$$\angle Z_{CL} = \cos^{-1}(\text{PF}_{CL}) = \cos^{-1}(0.681)$$


$$\angle Z_{CL} = 47.08^\circ$$

$$\boxed{\hat{I}_{S\text{new}} = 261.36 \angle -47.08^\circ}$$

$$\hat{I}_C = \hat{I}_{S\text{new}} - \hat{I}_{S\text{old}} \text{ (by KCL)}$$

$$\hat{I}_C = 82.54 \angle 90^\circ \text{ Arms}$$
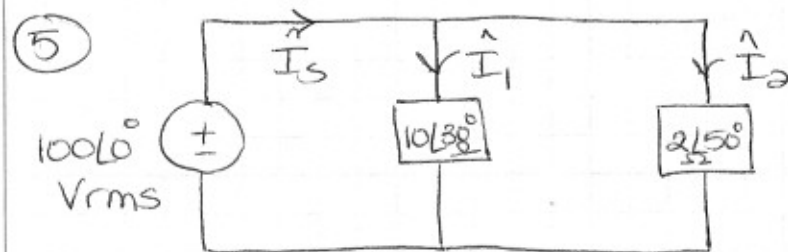
$$\boxed{Z_C = \frac{\hat{V}_S}{\hat{I}_C} = 2.52 \angle -90^\circ \Omega}$$



$$a) \hat{I}_1 = \frac{100 \angle 0^\circ}{10 \angle 38^\circ} = 10 \angle -30^\circ \text{ Arms}$$


$$\hat{I}_2 = \frac{100 \angle 0^\circ}{2 \angle 50^\circ} = 50 \angle -50^\circ \text{ Arms}$$

$$b) P_1 = (100)(10) \cos(30^\circ) = 866.02 \text{ W}$$

$$P_2 = (100)(50) \cos(50^\circ) = 3.21 \text{ kW}$$

$$c) Q_1 = 100(10) \sin(30^\circ) = 500 \text{ VAR}$$
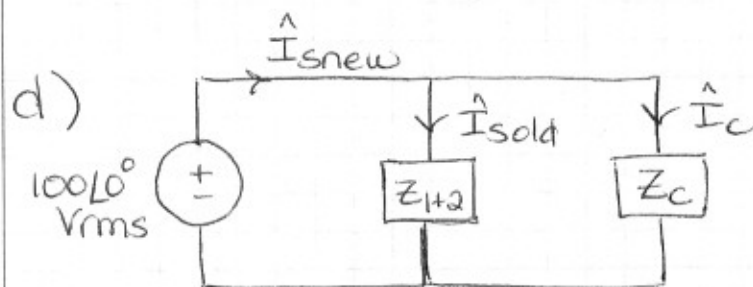
$$Q_2 = 100(50) \sin(50^\circ) = 3.83 \text{ kVAR}$$



$$\begin{aligned} \hat{I}_{\text{sold}} &= \hat{I}_1 + \hat{I}_2 \\ &= 59.50 \angle -46.7^\circ \text{ Arms} \end{aligned}$$

$$P_s = P_1 + P_2$$

$$P_s = 4.08 \text{ kW}$$

$$\text{PF}_{CL} = 0.9 \text{ lag}$$

$$\angle Z_{CL} = \cos^{-1}(0.9) = 25.84^\circ$$

$$4.08 \times 10^3 = 100(I_{\text{snew}})(.9)$$

$$I_{\text{snew}} = 45.29 \text{ Arms}$$

$$\hat{I}_{\text{snew}} = 45.29 \angle -25.84^\circ \text{ Arms}$$

$$\hat{I}_C = 23.56 \angle 90^\circ \text{ Arms}$$

$$Z_C = \frac{100 \angle 0^\circ}{\hat{I}_C} = 4.24 \angle -90^\circ \Omega$$

$$\frac{1}{\omega C} = 4.24$$

$$\omega = 377 \text{ rad/s}$$

$$C = 0.63 \text{ mF}$$