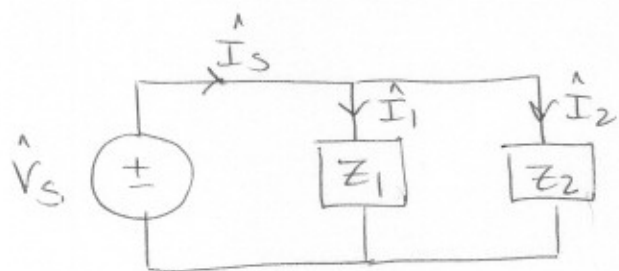


①



$$Z_1: 15 \text{ kW at PF} = 0.5 \text{ lag}$$

$$Z_2: 20 \text{ kVAR at PF} = 0.254 \text{ lag}$$

$$\hat{V}_s = 120 \angle 0^\circ \text{ Vrms}$$

$$a) P_1 = 15 \times 10^3 = 120(I_1)(.5)$$

$$\angle Z_1 = \cos^{-1}(.5) = 60^\circ$$

$$|Z_1| = \frac{V_s}{I_1} = \frac{120}{250} = 0.48 \Omega$$

$$I_1 = 250 \text{ Arms}$$

$$\hat{I}_1 = 250 \angle -60^\circ \text{ Arms}$$

$$Z_1 = 0.48 \angle 60^\circ \Omega$$

$$\angle Z_2 = \cos^{-1}(.254) = 75.29^\circ$$

$$Q_2 = 20 \times 10^3 = 120(I_2) \sin(75.29^\circ)$$

$$I_2 = 172.31 \text{ Arms}$$

$$|Z_2| = \frac{V_s}{I_2} = \frac{120}{172.31} = 0.696 \Omega$$

$$\hat{I}_2 = 172.31 \angle -75.29^\circ \text{ Arms}$$

$$Z_2 = 0.696 \angle 75.29^\circ \Omega$$

$$b) \hat{I}_s = \hat{I}_1 + \hat{I}_2 = 418.68 \angle -66.23^\circ \text{ Arms}$$

$$c) \hat{S}_s = \hat{V}_s \cdot \hat{I}_s^* = (120 \angle 0^\circ)(418.68 \angle 66.23^\circ)$$

$$\hat{S}_s = 50.24 \angle 66.23^\circ \text{ kVA}$$

$$\text{check } P_s = \text{Re}[\hat{S}_s] = 20.25 \text{ kW}$$

$$P_1 = 15 \text{ kW}$$

$$P_2 = \frac{20 \text{ kVAR}}{\sin(75.29^\circ)} \cdot \cos(75.29^\circ) = 5.25 \text{ kW}$$

$$P_s = P_1 + P_2 = 20.25 \text{ kW}$$

check
😊




① cont

d) The angle of the loads combined is the angle of the complex power.

$$PF_{1,2} = \cos(66.23) = 0.403 \text{ lagg.}$$

-01-

$$Z_1 || Z_2 = 0.287 \angle 66.23^\circ \Omega \quad PF = \cos(66.23) = 0.403 \text{ lag.}$$

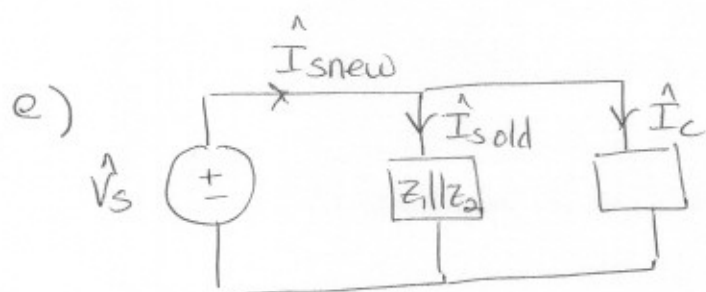

$$PF_{CL} = 0.95 \text{ lag}$$

$$\hat{I}_{sold} = 418.68 \angle -66.23^\circ \text{ Arms}$$

$$P_s = 20.25 \text{ kW}$$

$$20.25 \times 10^3 = 120(I_{snew})(.95)$$

$$\hat{V}_s = 120 \angle 0^\circ \text{ Vrms}$$

$$I_{snew} = 177.63 \text{ Arms}$$

$$\angle Z_{CL} = \cos^{-1}(.95) = 18.19^\circ$$


$$\hat{I}_{snew} = 177.63 \angle -18.19^\circ \text{ Arms}$$

$$\hat{I}_c = \hat{I}_{snew} - \hat{I}_{sold}$$

$$= 327.71 \angle 90^\circ \text{ Arms}$$

$$Z_c = \frac{\hat{V}_s}{\hat{I}_c} = \frac{120 \angle 0^\circ}{327.71 \angle 90^\circ} = 0.366 \angle -90^\circ \Omega$$

$$Z_c = 0.366 \angle -90^\circ \Omega$$

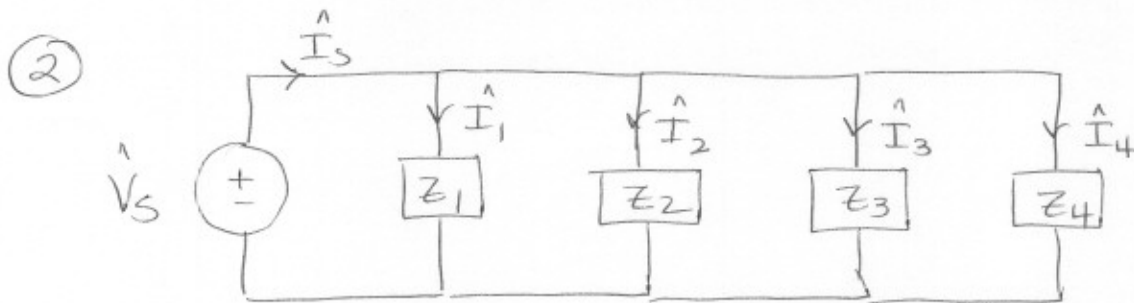

$$\hat{V}_s = 220 \angle 0^\circ \text{ V}_{\text{rms}}$$

a) $\underline{Z_1}$: $\hat{S}_1 = 10 \angle 25^\circ \text{ kVA}$

$$10 \times 10^3 = 220 \hat{I}_1$$

$$\hat{I}_1 = 45.45 \text{ Arms}$$

$$|Z_1| = \frac{220}{45.45} = 4.4 \Omega$$

$$\hat{I}_1 = 45.45 \angle -25^\circ \text{ Arms}$$

$$Z_1 = 4.4 \angle 25^\circ \Omega$$

$\underline{Z_2}$: $P_2 = 2 \text{ kW}$ $\text{PF}_2 = 0.8 \text{ lag}$ $\angle Z_2 = \cos^{-1}(0.8)$
 $= 36.87^\circ$

$$2 \times 10^3 = 220 (\hat{I}_2)(0.8)$$

$$\hat{I}_2 = 11.36 \text{ Arms}$$

$$|Z_2| = \frac{V_s}{\hat{I}_2} = 19.36 \Omega$$

$$\hat{I}_2 = 11.36 \angle -36.87^\circ \text{ Arms}$$

$$Z_2 = 19.36 \angle 36.87^\circ \Omega$$

$\underline{Z_3}$: $P_3 = 3 \text{ kW}$ $Q_3 = 8 \text{ kVAR}$ $\hat{S}_3 = P + jQ$
 $= 8.54 \angle 69.44^\circ \text{ kVA}$
 $\angle Z_3 = 69.44^\circ$

$$8.54 \times 10^3 = 220 \hat{I}_3 \quad \hat{I}_3 = 38.84 \text{ Arms}$$

$$\hat{I}_3 = 38.84 \angle -69.44^\circ \text{ Arms}$$

$$Z_3 = 5.67 \angle 69.44^\circ \Omega$$

$$Z_3 = \frac{220}{38.84} = 5.67 \Omega$$

② cont.

$$Z_4: I_4 = 30 \text{ Arms} \quad Q_4 = 4 \text{ kVAR}$$

$$4000 = 220(30) \sin(\angle Z_4)$$

$$\sin(\angle Z_4) = 0.606$$

$$\angle Z_4 = 37.31^\circ$$

$$|Z_4| = \frac{220}{30} = 7.33 \Omega$$

$$\hat{I}_4 = 30 \angle -37.31^\circ \text{ Arms}$$

$$Z_4 = 7.33 \angle 37.31^\circ \Omega$$

$$b). \quad \hat{I}_S = \hat{I}_1 + \hat{I}_2 + \hat{I}_3 + \hat{I}_4$$

$$\hat{I}_S = 119.15 \angle -42.55^\circ \text{ Arms}$$

$$c). \quad P_S = V_S I_S \cos(\theta - \phi)$$

$$= (220)(119.15) \cos(42.55)$$

$$P_S = 19.31 \text{ kW}$$

$$Q_S = V_S I_S \sin(\theta - \phi)$$

$$= 220(119.15) \sin(42.55)$$

$$Q_S = 17.73 \text{ kVAR}$$

check

$$P_1 = \text{Re}[\hat{S}_1] = 9.06 \text{ kW}$$

$$P_2 = 2 \text{ kW}$$

$$P_3 = 3 \text{ kW}$$

$$P_4 = 220(30) \cos(37.31) = 5.30 \text{ kW}$$

$$\Sigma P = 19.36 \text{ kW}$$

checks

(2) cont

pg 5

$$d) PF_{1-4} \Rightarrow \frac{\cos(\theta - \phi)}{\cos(42.55)} = 0.737 \text{ lag}$$

$$e) P_s = 19.31 \text{ kW}$$

$$\hat{V}_s = 220 \angle 0$$

$$PF_{CL} = 1 \text{ (to minimize current)} \quad \angle Z_{CL} = 0^\circ$$

$$19.31 \times 10^3 = 220 (I_{s\text{new}}) (1)$$


$$I_{s\text{new}} = 87.77 \text{ Arms}$$

$$\hat{I}_{s\text{new}} = 87.77 \angle 0^\circ \text{ Arms}$$

$$\begin{aligned} \hat{I}_C &= \hat{I}_{s\text{new}} - \hat{I}_{s\text{old}} = (87.77 \angle 0) - (119.15 \angle -42.55) \\ &= 80.57 \angle 90^\circ \text{ Arms} \end{aligned}$$

$$Z_C = \frac{\hat{V}_s}{\hat{I}_C} = 2.73 \angle -90^\circ \Omega$$

③

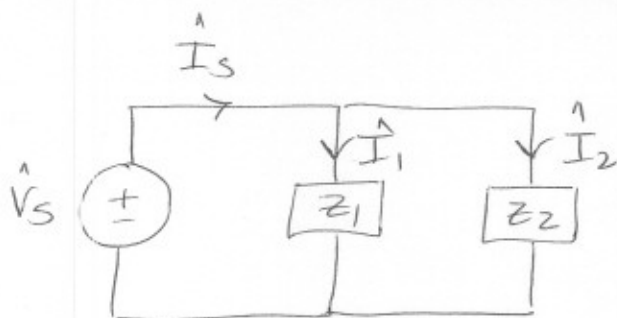

$$I_s = 300 \text{ Arms}$$

$$P_s = 12 \text{ kW}$$

$$PF_s = 0.47 \text{ lag}$$

$$12 \times 10^3 = V_s (300)(0.47) \quad \cos^{-1}(0.47) = 61.97^\circ$$

$$V_s = 85.11 \text{ Vrms} \quad (\text{assume source angle is } 0)$$

$$\hat{V}_s = 85.11 \angle 0^\circ \text{ Vrms}$$

$$\hat{I}_s = 300 \angle -61.97^\circ \text{ Arms}$$

$$Z_1: P_1 = 4 \text{ kW}$$

$$PF_1 = 0.3 \text{ lag}$$

$$\angle Z_1 = \cos^{-1}(0.3) = 72.54^\circ$$

$$4000 = 85.11(I_1)(0.3)$$

$$I_1 = 156.68 \text{ Arms}$$

$$\boxed{\hat{I}_1 = 156.98 \angle -72.54^\circ \text{ Arms}}$$

$$Z_1 = \frac{85.11}{156.98} = 0.54 \Omega$$

$$\boxed{Z_1 = 0.54 \angle 72.54^\circ \Omega}$$

$$\hat{I}_2 = \hat{I}_s - \hat{I}_1$$

$$= (300 \angle -61.97^\circ) - (156.98 \angle -72.54^\circ)$$

$$= 148.50 \angle -50.79^\circ \text{ Arms}$$

$$\boxed{Z_2 = \frac{\hat{V}_s}{\hat{I}_2} = 0.57 \angle 50.79^\circ \Omega}$$

(4)


$$V_L = 208 \text{ Vrms}$$

$$\vec{Z}_{LY} \Rightarrow P_{3\phi} = 48 \text{ kW}$$

$$PF = 0.715 \text{ lag}$$

a)

single phase ckt (Y-Y)

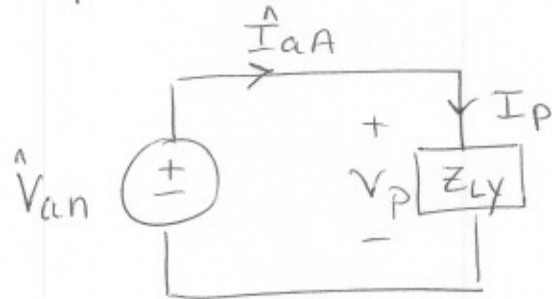

$$|\hat{V}_{an}| = \frac{V_L}{\sqrt{3}} = 120.09 \text{ Vrms}$$

$$V_p = |\hat{V}_{an}| = 120.09 \text{ Vrms}$$

$$P_{1\phi} = \frac{P_{3\phi}}{3} = \frac{48}{3} = 16 \text{ kW}$$

$$16 \times 10^3 = |\hat{V}_{an}| |\hat{I}_{aA}| \cdot PF$$

$$a = V_p I_p \cdot PF$$

$$16 \times 10^3 = 120.09 I_p (0.715)$$

$$I_p = 186.34 \text{ Arms}$$

$$b) \hat{I}_{aA} = I_L \angle -\phi \quad I_L = I_p = 186.34$$

$$\angle Z_L = \cos^{-1}(0.715) = 44.36^\circ$$

$$\hat{I}_{aA} = 186.34 \angle -44.36^\circ \text{ Arms}$$

$$\hat{I}_{bB} = 186.34 \angle -164.36^\circ \text{ Arms}$$

$$\hat{I}_{cC} = 186.34 \angle 75.64^\circ \text{ Arms}$$

④ cont

PS#4 - Solns
and

$$d) \hat{S}_{3\phi} = 3 \cdot \hat{V}_{an} \cdot \hat{I}_{aA}^*$$

$$= 3 (120.09 \angle 0) (186.34 \angle 44.36)$$

$$\hat{S}_{3\phi} = 67.13 \angle 44.36^\circ \text{ kVA}$$