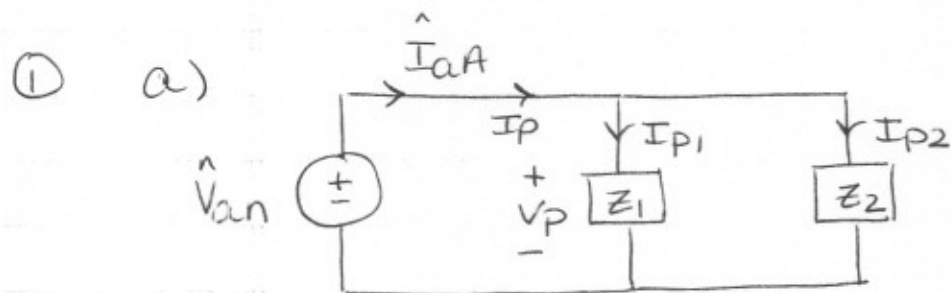


Problem Set #5 - Solutions pg1



$$V_L = 400 \text{ Vrms}$$

$$Z_1: P_{3\phi_1} = 15 \text{ kW } PF_1 = 0.25$$

$$Z_2: \hat{S}_{3\phi_2} = 60 \angle 50^\circ \text{ kVA } \text{lag}$$

$$\left. \begin{aligned} \hat{V}_{ab} &= 400 \angle 30^\circ \\ \hat{V}_{bc} &= 400 \angle -90^\circ \\ \hat{V}_{ca} &= 400 \angle +150^\circ \end{aligned} \right\} \text{Vrms}$$

$$\boxed{\hat{V}_{an} = 230.94 \angle 0^\circ \text{ Vrms}} \quad \text{note:}$$

$$b) V_p = |\hat{V}_{an}| = \frac{V_L}{\sqrt{3}} = \frac{400}{\sqrt{3}}$$

$$\boxed{V_p = 230.94 \text{ Vrms}}$$

$$c) \angle Z_1 = \cos^{-1}(0.25) = 75.52^\circ$$

$$\angle Z_2 = 50^\circ$$

$$P_{3\phi_1} = \sqrt{3} V_L I_{L1} \cdot PF_1$$

$$I_{L1} = \frac{15 \times 10^3}{\sqrt{3} \cdot 400 \cdot 0.25} = 86.60 \text{ Arms}$$

$$\hat{I}_{L1} = 86.60 \angle -75.52^\circ \text{ Arms}$$

$$\hat{S}_{3\phi_2} = \sqrt{3} V_L I_{L2} \angle Z_L$$

$$\sqrt{3} V_L I_{L2} = 60 \times 10^3$$

$$I_{L2} = \frac{60 \times 10^3}{\sqrt{3}(400)} = 86.60 \text{ Arms}$$

$$\hat{I}_{L2} = 86.60 \angle -50^\circ \text{ Arms}$$

$$\hat{I}_{aA} = \hat{I}_{L1} + \hat{I}_{L2} = 168.92 \angle -62.76^\circ \text{ Arms}$$

$$\hat{I}_{bB} = 168.92 \angle 177.24^\circ \text{ Arms}$$

$$\hat{I}_{cC} = 168.92 \angle 57.24^\circ \text{ Arms}$$

Problem Set #5 - solutions pg 2

① cont d) $I_p = |\hat{I}_{aA}| = I_L = 168.92 \text{ Arms}$

e) $\hat{Z}_1 = \frac{\hat{V}_{an}}{\hat{I}_{L1}} = \frac{230.94 \angle 0^\circ}{86.60 \angle -75.52^\circ} = 2.67 \angle 75.52^\circ \Omega$

$\hat{Z}_2 = \frac{\hat{V}_{an}}{\hat{I}_{L2}} = \frac{230.94 \angle 0^\circ}{86.60 \angle -50^\circ} = 2.67 \angle 50^\circ \Omega$

f) $P_{3\phi_s} = \sqrt{3} V_L I_L \cdot PF_{1-2} = \sqrt{3} V_L I_L \cos(\theta - \phi)$


$P_{3\phi_s} = \sqrt{3} (400)(168.92) \cos(62.76)$
 $= 53.57 \text{ kW}$

check $P_{3\phi_s} = P_{3\phi_1} + P_{3\phi_2}$

$P_{3\phi_2} = \text{Re}[\hat{S}_{3\phi_2}]$
 $= 38.57 \text{ kW}$

$= 15 + 38.57$

$= 53.57 \text{ kW} \quad \text{😊}$

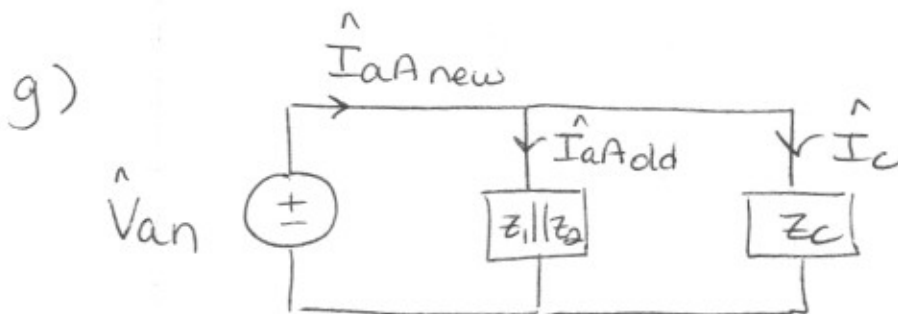

$PF_{CL} = 0.95 \text{ lag}$
 $\angle Z_{CL} = \cos^{-1}(0.95)$
 $= 18.19^\circ$

$I_{L\text{new}} = |\hat{I}_{aA\text{new}}|$

$P_{3\phi_s} = \sqrt{3} V_L I_{L\text{new}} \cdot PF_{CL}$

$I_{L\text{new}} = \frac{53.57 \times 10^3}{\sqrt{3} (400) (0.95)} = 81.39 \text{ Arms}$

Problem Set #5 - Solutions pg 3


① cont

$$\hat{I}_{aA \text{ new}} = 81.39 \angle -18.19^\circ \text{ Arms}$$

$$\hat{I}_c = \hat{I}_{aA \text{ new}} - \hat{I}_{aA \text{ old}} = 124.78 \angle 90^\circ \text{ Arms}$$

$$\boxed{Z_c = \frac{\hat{V}_{an}}{\hat{I}_c} = 1.85 \angle -90^\circ \Omega}$$

②

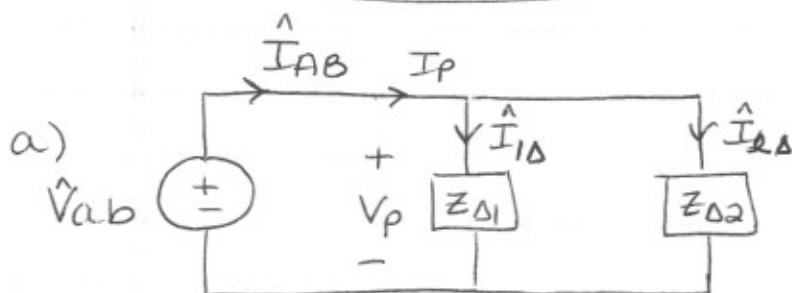

$$|\hat{V}_{an}| = 100 \text{ Vrms}$$

$$Z_{\Delta 1} : \hat{S}_{3\phi_1} = 3.3 \angle 75^\circ \text{ kVA}$$

$$Z_{\Delta 2} : \hat{S}_{3\phi_2} = 6 \angle 10^\circ \text{ kVA}$$

a) $V_L = \sqrt{3} |\hat{V}_{an}| = 173.20 \text{ Vrms}$

$$\hat{V}_{ab} = 173.20 \angle 30^\circ \text{ Vrms}$$

$$\hat{V}_{an} = 100 \angle 0^\circ \text{ Vrms}$$

$$\hat{V}_{bc} = 173.20 \angle -90^\circ \text{ Vrms}$$

$$\hat{V}_{ca} = 173.20 \angle +150^\circ \text{ Vrms}$$

b) $V_p = V_L = 173.20 \text{ Vrms}$

c) $\hat{I}_{aA} = \hat{I}_{AB} - \hat{I}_{cA}$

$$\hat{I}_{AB} = \hat{I}_{1\Delta} + \hat{I}_{2\Delta}$$

$$\hat{S}_{1\phi_1} = \frac{\hat{S}_{3\phi_1}}{3} = 1.1 \angle 75^\circ \text{ kVA}$$

$$\hat{S}_{1\phi_1} = \hat{V}_{ab} \cdot \hat{I}_{1\Delta}^* = 1.1 \angle 75^\circ \text{ kVA}$$

$$\hat{I}_{1\Delta} = 6.35 \angle -45^\circ \text{ Arms}$$

Problem Set #5 - Solutions pg 4

② cont c) $\hat{S}_{1\phi_2} = 2 \angle 10^\circ \text{ kVA}$
 $\hat{V}_{ab} \cdot \hat{I}_{2\Delta}^* = 2 \angle 10^\circ \text{ kVA}$

$$\hat{I}_{2\Delta} = 11.55 \angle 20^\circ \text{ Arms}$$

$$\hat{I}_{AB} = \hat{I}_{1\Delta} + \hat{I}_{2\Delta} = 15.35 \angle -2.02^\circ \text{ Arms}$$

$$\hat{I}_{CA} = 15.35 \angle 117.98^\circ$$

$$\begin{aligned} \hat{I}_{aA} &= 26.59 \angle -32.02^\circ \text{ Arms} \\ \hat{I}_{bB} &= 26.59 \angle -152.02^\circ \text{ Arms} \\ \hat{I}_{cC} &= 26.59 \angle 87.98^\circ \text{ Arms} \end{aligned} \left[\begin{aligned} I_L &= \sqrt{3} I_p \\ &= \sqrt{3} (15.35) \\ &= 26.59 \text{ Arms} \end{aligned} \right.$$

d) $I_p = |\hat{I}_{AB}| = \frac{I_L}{\sqrt{3}} = 15.35 \text{ Arms}$

e) $Z_{1\Delta} = \frac{\hat{V}_{ab}}{\hat{I}_{1\Delta}} = 27.27 \angle 75^\circ \Omega$

$$Z_{2\Delta} = \frac{\hat{V}_{ab}}{\hat{I}_{2\Delta}} = 15 \angle 10^\circ \Omega$$


f) $P_{3\phi_s} = \sqrt{3} V_L I_L \cos(\theta - \phi)$

$$\begin{aligned} &= \sqrt{3} (173.20) (26.59) \cos(32.02^\circ) \\ &= 6.76 \text{ kW} \end{aligned}$$

check $P_{3\phi_1} = \text{Re} [\hat{S}_{3\phi_1}] = 0.854 \text{ kW}$
 $P_{3\phi_2} = \text{Re} [\hat{S}_{3\phi_2}] = 5.91 \text{ kW}$ } $6.76 \text{ kW} \quad \text{ } \circ \circ$

Problem Set #5 - Solutions pg 5

② cont
g)

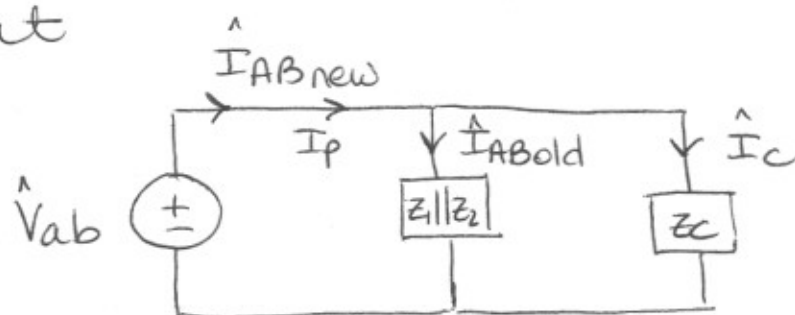

$$PF_{cL} = 0.8 \text{ lag}$$

$$\angle Z_{cL} = 36.87^\circ$$

$$P_{3\phi S} = 6.76 \text{ kW}$$

$$6.76 \times 10^3 = \sqrt{3} V_L I_{L\text{new}} \cdot PF_{cL}$$

$$I_{L\text{new}} = \frac{6.76 \times 10^3}{\sqrt{3} (173.20) (0.8)} = 28.17 \text{ Arms}$$

$$I_{p\text{new}} = \frac{I_{L\text{new}}}{\sqrt{3}} = 16.26 \text{ Arms}$$

$$\hat{I}_{AB\text{new}} = I_{p\text{new}} (\angle(30^\circ - \angle Z_{cL}))$$

$$= 16.26 \angle -6.87^\circ \text{ Arms}$$

$$\hat{I}_c = \hat{I}_{AB\text{new}} - \hat{I}_{AB\text{old}}$$

$$= 1.62 \angle -60^\circ \text{ Arms}$$


$$Z_c = \frac{\hat{V}_{ab}}{\hat{I}_c} = \frac{173.20 \angle 30^\circ}{1.62 \angle -60^\circ} = 107.10 \angle 90^\circ \Omega$$

Problem Set #5 pg 6

③ $|\hat{V}_{an}| = 120 \text{ Vrms}$

$Z_{\Delta} \Rightarrow P_{\Delta} = 24 \text{ kW} \quad \text{PF}_{\Delta} = 0.468 \text{ lag}$

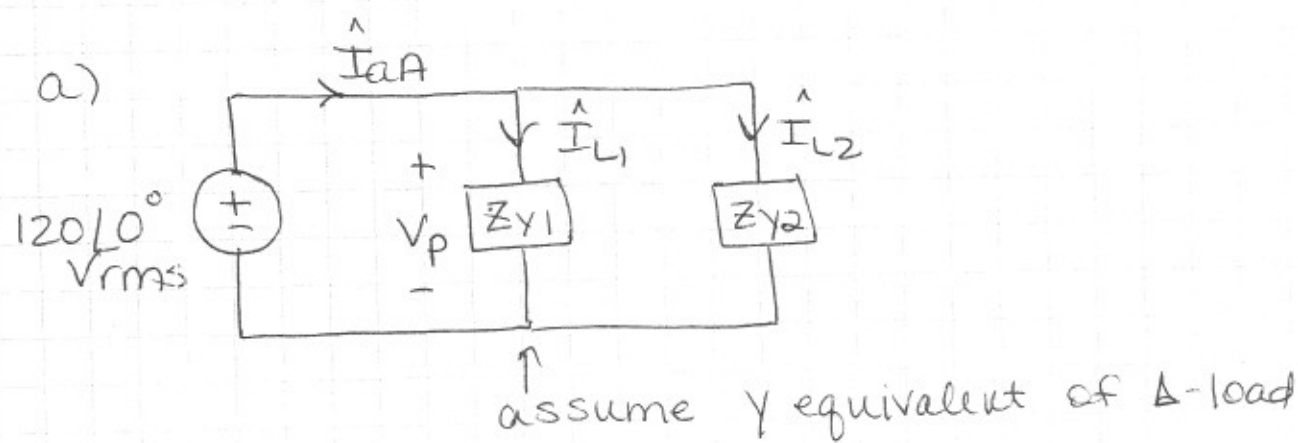$Z_Y \Rightarrow \hat{S}_Y = 12 \angle 30^{\circ} \text{ kVA}$



b) $\hat{V}_{ab} = \sqrt{3}(120) \angle 30^{\circ} = 207.85 \angle 30^{\circ} \text{ Vrms}$

$\hat{V}_{bc} = 207.85 \angle -90^{\circ} \text{ Vrms}$

$\hat{V}_{ca} = 207.85 \angle +150^{\circ} \text{ Vrms}$

c) $V_p = |\hat{V}_{an}| = 120 \text{ Vrms}$

d) find $\hat{I}_{L1}$ & $\hat{I}_{L2}$, first.

$P_{Y1} = 24 \text{ kW} \quad \text{PF}_{Y1} = 0.468 \text{ lag} \Rightarrow \angle Z_{Y1} = 62.10^{\circ}$

$24 \times 10^3 = \sqrt{3} V_L I_{L1} \cdot \text{PF}_1$

$I_L = 142.45 \text{ Arms}$

$\hat{I}_{L1} = 142.45 \angle -62.10^{\circ} \text{ Arms}$

$\hat{S}_{Y2} = 12 \times 10^3 \angle 30^{\circ} \quad \angle Z_{Y2} = 30^{\circ}$

$12 \times 10^3 = \sqrt{3} V_L I_{L2} \quad I_{L2} = 33.33 \text{ Arms}$

Prob Set #5 - Solutions pg 7

$$\textcircled{3} \quad \hat{I}_{L2} = 33.33 \angle -30^\circ \text{ Arms}$$

$$\hat{I}_{aA} = \hat{I}_{L1} + \hat{I}_{L2} = 171.60 \angle -56.18^\circ \text{ Arms}$$

$$\hat{I}_{bB} = 171.60 \angle -176.18^\circ \text{ Arms}$$

$$\hat{I}_{cC} = 171.60 \angle 63.82^\circ \text{ Arms}$$

-Or- $P_{Y1} = 24 \text{ kW}$ $PF_1 = 0.468$ $\angle Z_{Y1} = 62.10$

$$\rightarrow |\hat{S}_{Y1}| = \sqrt{3} V_L I_{L1} = \frac{P_{Y1}}{PF_1} = \frac{24 \times 10^3}{0.468} = 51.28 \text{ kVA}$$

$\angle Z_{Y1} = \angle \hat{S}_{Y1} = 62.10$

so $\hat{S}_{Y1} = 51.28 \angle 62.10^\circ \text{ kVA}$

$$\begin{aligned} \hat{S}_{\text{total}} &= \hat{S}_{Y1} + \hat{S}_{Y2} = 51.28 \angle 62.10^\circ + 12 \angle 30^\circ \\ &= 61.77 \angle 56.18^\circ \text{ kVA} \end{aligned}$$

$$|\hat{S}_{\text{total}}| = \sqrt{3} V_L I_L, \text{ where } I_L = |\hat{I}_{aA}|$$

$$I_L = 171.59 \text{ Arms} \quad (\text{angle is opposite sign of the angle of } \hat{S}_{\text{total}})$$

$$\hat{I}_{aA} = 171.59 \angle -56.18^\circ \text{ Arms} \quad \text{✓ checks!}$$



e) $I_p = I_L$ for Y-Y systems, where $I_L = |\hat{I}_{aA}|$
 $= 171.60 \text{ Arms}$

Problem Set #5 solutions pg 8

$$f) Z_{Y1} = \frac{\hat{V}_{an}}{\hat{I}_{L1}} = 0.84 \angle 62.10^\circ \Omega$$

$$Z_{Y2} = \frac{\hat{V}_{an}}{\hat{I}_{L2}} = 3.6 \angle 30^\circ \Omega$$

Note:

you can calculate the Δ -equivalent of these loads

$$Z_{\Delta 1} = 3Z_{Y1} = 2.53 \angle 62.10^\circ \Omega$$


$$Z_{\Delta 2} = 3Z_{Y2} = 10.80 \angle 30^\circ \Omega$$

$$\begin{aligned} g) P_{3\phi s} &= \sqrt{3} V_L I_L \cdot \cos(\theta - \phi) \\ &= \sqrt{3} (207.85)(171.60) \cos(0 - (-56.18)) \\ &= 34.38 \text{ kW} \end{aligned}$$

$$\text{or from } \hat{S}_{\text{total}} = 61.77 \angle 56.18^\circ \text{ kVA}$$

$$P_{3\phi s} = \text{Re}[\hat{S}_{\text{total}}] = 34.38 \text{ kW checks } \text{☺}$$

h) Again assume a γ -equivalent load.

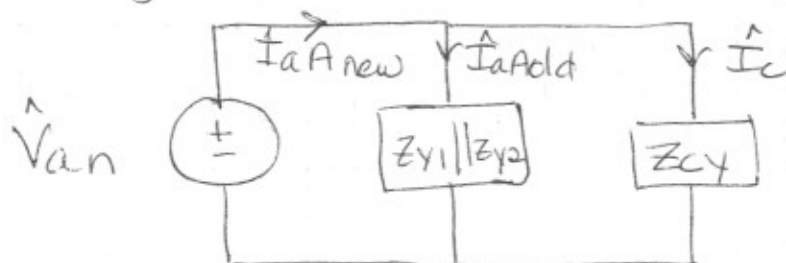

$$\hat{I}_{AAold} = 171.60 \angle -56.18^\circ \text{ Arms}$$

$$P_{3\phi} = 34.38 \text{ kW}$$

$$\begin{aligned} \text{PF}_{CL} &= 0.9 \text{ lag} \\ \angle Z_{CL} &= \cos^{-1}(0.9) \\ &= 25.84^\circ \end{aligned}$$

$$34.38 \times 10^3 = \sqrt{3} V_L I_{L\text{new}} \cdot \text{PF}_{CL}$$

$$I_{L\text{new}} = 106.12 \text{ Arms}$$

$$\hat{I}_{AAnew} = 106.12 \angle -25.84^\circ$$

$$\begin{aligned} \hat{I}_c &= \hat{I}_{AAnew} - \hat{I}_{AAold} \\ &= 96.31 \angle 90^\circ \text{ Arms} \end{aligned}$$

$$Z_{Y} = \hat{V}_{an} - 1.25 \angle -90^\circ \Omega$$


Problem set #5 - solutions pg 9

n) cont

$$Z_{CY} = 1.25 \angle -90^\circ \Omega$$

$$Z_{CA} = 3Z_{CY} = 3.75 \angle -90^\circ \Omega$$

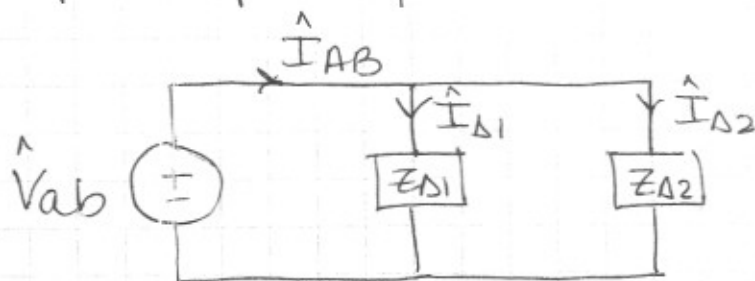repeat for γ - Δ . (I will refer to some answers from previous γ - γ work)



$$b) \hat{V}_{ab} = 207.85 \angle 30^\circ \text{ Vrms}$$

$$c) \text{ for } \gamma\text{-}\Delta \quad V_p = V_L = \sqrt{3} |\hat{V}_{an}| = |\hat{V}_{ab}| = 207.85 \text{ Vrms}$$

$$d) \hat{I}_{aA} = \hat{I}_{AB} - \hat{I}_{cA}$$

find $\hat{I}_{AB}$ by find $\hat{I}_{\Delta 1}$ and $\hat{I}_{\Delta 2}$

$$Z_{\Delta 1}: P_{3\phi} = 24 \text{ kW} \quad PF_1 = 0.468 \quad LZ_{\Delta 1} = 62.10$$

$$24 \times 10^3 = \sqrt{3} V_L I_{L1} \cdot PF_1 \quad I_{L1} = 142.45 \text{ Arms}$$

$$\angle \hat{I}_{\Delta 1} = 30 - LZ_{\Delta 1} = 30 - 62.10 = -32.10$$

$$I_{p1} = |\hat{I}_{\Delta 1}| = \frac{I_{L1}}{\sqrt{3}} = 82.24 \text{ Arms}$$

$$\hat{I}_{\Delta 1} = 82.24 \angle -32.10^\circ \text{ Arms}$$

$$\hat{I}_{\Delta 2} \Rightarrow I_{L2} = 33.33 \text{ Arms} \quad LZ_{\Delta 1} = 30^\circ \text{ (from } \gamma\text{-}\gamma)$$

$$I_{p2} = \frac{I_{L2}}{\sqrt{3}} = 19.24 \text{ Arms} \quad \angle \hat{I}_{\Delta 2} = 30 - 30^\circ = 0^\circ$$

$$\hat{I}_{\Delta 2} = 19.24 \angle 0^\circ \text{ Arms}$$

Problem Set #5 pg 10

③ cont

$$d) \hat{I}_{AB} = \hat{I}_{\Delta 1} + \hat{I}_{\Delta 2} = 99.07 \angle -26.17^\circ \text{ Arms}$$

$$\hat{I}_{BC} = 99.07 \angle \overset{93.83^\circ}{-146.17^\circ} \text{ Arms}$$

$$\hat{I}_{CA} = 99.07 \angle \overset{93.83^\circ}{-106.17^\circ} \text{ Arms}$$

$$\hat{I}_{aA} = \hat{I}_{AB} - \hat{I}_{CA} = 171.59 \angle -56.17^\circ \text{ Arms}$$


(looks familiar ☺)

$$e) I_p = |\hat{I}_{AB}| = \frac{I_L}{\sqrt{3}} = 99.07 \text{ Arms}$$

$$f) Z_{\Delta 1} = \frac{\hat{V}_{ab}}{\hat{I}_{\Delta 1}} = 2.53 \angle 62.10^\circ \Omega$$

$$Z_{\Delta 2} = \frac{\hat{V}_{ab}}{\hat{I}_{\Delta 2}} = 10.80 \angle 30^\circ \Omega$$

(also familiar ☺)

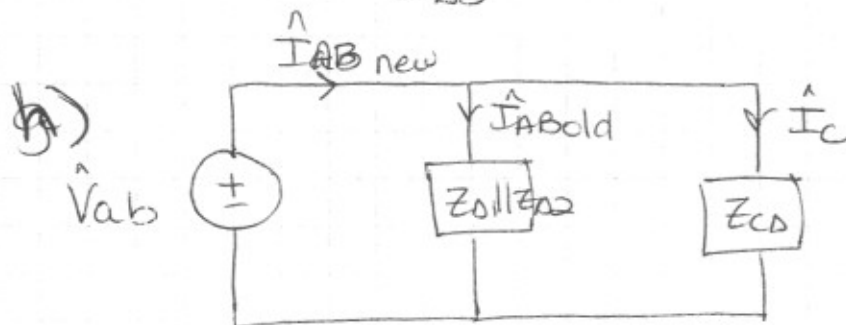

$$\hat{I}_{ABdd} = 99.07 \angle -26.17^\circ \text{ Arms}$$

$$P_{3\phi} \text{ (from before)} = 34.38 \text{ kW}$$

$$PF_{CL} = 0.9 \text{ lag}$$

$$\angle Z_{CL} = 25.84^\circ$$

$$34.38 \times 10^3 = \sqrt{3} V_L I_{L\text{new}} \cdot PF_{CL}$$

$$I_{L\text{new}} = 106.12 \text{ Arms}$$

$$I_{p\text{new}} = |\hat{I}_{AB\text{new}}| = \frac{106.12}{\sqrt{3}} = 61.27 \text{ Arms}$$

$$\begin{aligned} \angle \hat{I}_{AB\text{new}} &= 30^\circ - \angle Z_{CL} \\ &= 30^\circ - 25.84^\circ \\ &= 4.16^\circ \end{aligned}$$

$$\hat{I}_{AB\text{new}} = 61.27 \angle 4.16^\circ \text{ Arms}$$

$$\hat{I}_C = \hat{I}_{AB\text{new}} - \hat{I}_{ABdd}$$

Problem Set #5 pg 11

$$\textcircled{3} \hat{I}_C = 55.59 \angle 120^\circ \text{ Arms}$$

$$Z_{CA} = \frac{\hat{V}_{ab}}{\hat{I}_C} = 3.74 \angle -90^\circ \Omega$$

note $Z_{CA} = 3Z_{cy}$ from previous work


$$\textcircled{4} I_L = 300 \text{ Arms}$$

$$Z_1: 12 \text{ kW} \quad \text{PF} = 0.257 \text{ lag}$$

$$Z_2: 6 \text{ kW} \quad 15 \text{ kVAR}$$

$$\frac{\hat{S}_1 = \frac{12 \text{ kW}}{0.257} =$$

$$|\hat{S}_1| = \frac{P_1}{\text{PF}_1} = \frac{12 \times 10^3}{0.257} = 46.69 \text{ kVA}$$

$$\angle \hat{S}_1 = \cos^{-1}(0.257) = 75.10^\circ$$

$$\hat{S}_1 = 46.69 \angle 75.10^\circ \text{ kVA}$$

$$\hat{S}_2 = P_2 + jQ_2 = 16.15 \angle 68.20^\circ \text{ kVA}$$

$$\hat{S}_{3\phi S} = \hat{S}_{13\phi} + \hat{S}_{23\phi} = 62.76 \angle 73.33^\circ \text{ kVA}$$

$$|\hat{S}_{3\phi S}| = 62.76 \times 10^3 = \sqrt{3} V_L I_L$$

$$V_L = 120.78 \text{ Vrms}$$


$$\hat{V}_{ab} = 120.78 \angle 30^\circ \text{ Vrms}$$

Problem Set #5 pg 12

④ cont

$$|\hat{V}_{an}| = \frac{V_L}{\sqrt{3}} = 69.73 \text{ Vrms}$$
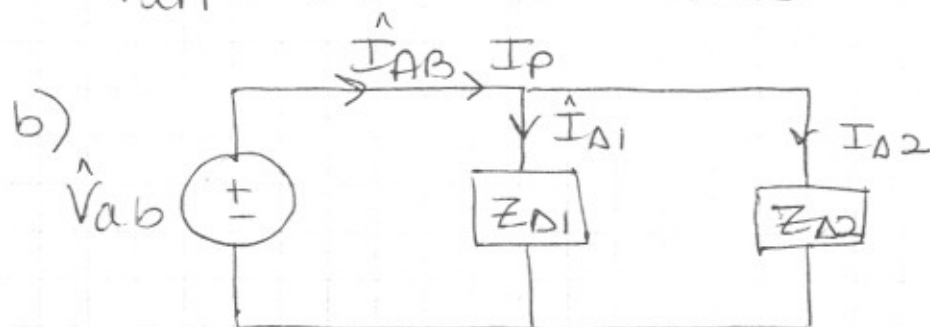
$$\hat{V}_{an} = 69.73 \angle 0^\circ \text{ Vrms}$$



$$\hat{I}_{\Delta 1} : 12 \times 10^3 = \sqrt{3} V_L I_{L1} \cdot \text{PF}_1 \quad \angle Z_1 = 75.10^\circ$$

$$I_{L1} = 223.20 \text{ Arms} \quad \angle I_{\Delta 1} = 30 - 75.10^\circ = -45.10^\circ$$

$$I_{P1} = \frac{I_{L1}}{\sqrt{3}} = 128.86 \text{ Arms}$$

$$\boxed{\hat{I}_{\Delta 1} = 128.86 \angle -45.10^\circ \text{ Arms}}$$

$$\hat{I}_{\Delta 2} : \hat{S}_2 = 16.15 \angle 68.20^\circ \text{ kVA}$$

$$16.15 \times 10^3 = \sqrt{3} V_L I_{L2} \quad I_{L2} = 77.20 \text{ Arms}$$

$$I_{P2} = \frac{I_{L2}}{\sqrt{3}} = 44.57 \text{ Arms} \quad \angle I_{\Delta 2} = 30 - 68.20^\circ = -38.20^\circ$$

$$\boxed{\hat{I}_{\Delta 2} = 44.57 \angle -38.20^\circ \text{ Arms}}$$

$$\begin{aligned} \hat{I}_{AB} &= 44.57 \angle -38.20^\circ + 128.86 \angle -45.10^\circ \\ &= 173.19 \angle -43.33^\circ \text{ Arms} \end{aligned}$$

$$\begin{aligned} \hat{I}_{QA} &= 223.20 \angle -75.10^\circ + 77.20 \angle 68.20^\circ \\ &= 299.98 \angle -73.33^\circ \text{ Arms} \end{aligned}$$

↑ close enough to 300 Arms which was given

Problem Set #5 pg 13

④ cont

$$b) I_p = |\hat{I}_{AB}| = 173.19 \text{ Arms}$$


$$c) Z_{\Delta 1} = \frac{\hat{V}_{ab}}{\hat{I}_{\Delta 1}} = 0.94 \angle 75.10^\circ \Omega$$

$$Z_{\Delta 2} = \frac{\hat{V}_{ab}}{\hat{I}_{\Delta 2}} = 2.71 \angle 68.20^\circ \Omega$$

$$d) Z_{Y1} = \frac{\hat{V}_{an}}{\hat{I}_{L1}} = \frac{1}{3} Z_{\Delta 1} = 0.31 \angle 75.10^\circ \Omega$$

$$Z_{Y2} = \frac{\hat{V}_{an}}{\hat{I}_{L2}} = \frac{1}{3} Z_{\Delta 2} = 0.90 \angle 68.20^\circ \Omega$$

e) assume Y-Y system

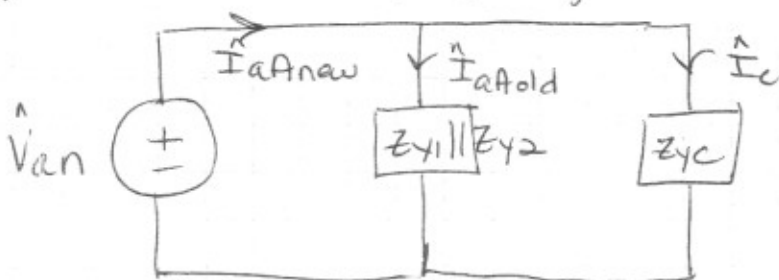

$$\hat{I}_{aAdd} = 300 \angle -73.33^\circ \text{ Arms}$$

$$P_{3\phi} = \text{Re} [S_{3\phi s}]$$

$$= 18 \text{ kW}$$

$$= P_{3\phi 1} + P_{3\phi 2}$$

$$PF_L = 1$$

$$Z_{CL} = 0^\circ$$

$$18 \times 10^3 = \sqrt{3} V_L I_{Lnew} \cdot 1$$

$$I_{Lnew} = 86.04 \text{ Arms}$$

$$\hat{I}_{aAnew} = 86.04 \angle 0^\circ \text{ Arms}$$

$$\hat{I}_c = \hat{I}_{aAnew} - \hat{I}_{aAold} = 287.35 \angle 90^\circ \text{ Arms}$$

$$Z_{cy} = \frac{\hat{V}_{an}}{\hat{I}_c} = 0.243 \angle -90^\circ \Omega$$