
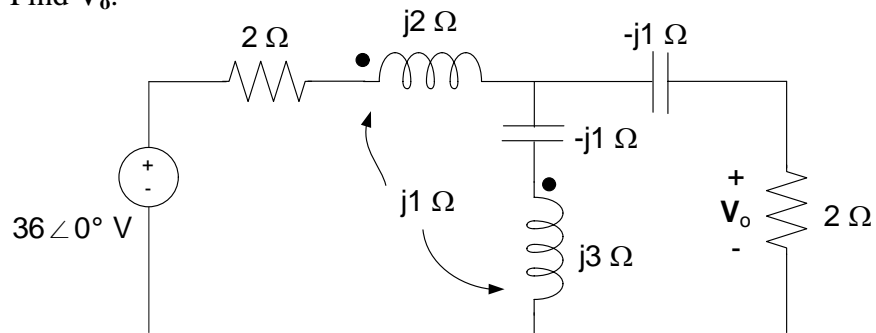


EE 313 – Spring 2007 – Problem Set 6

1. Find V_o .

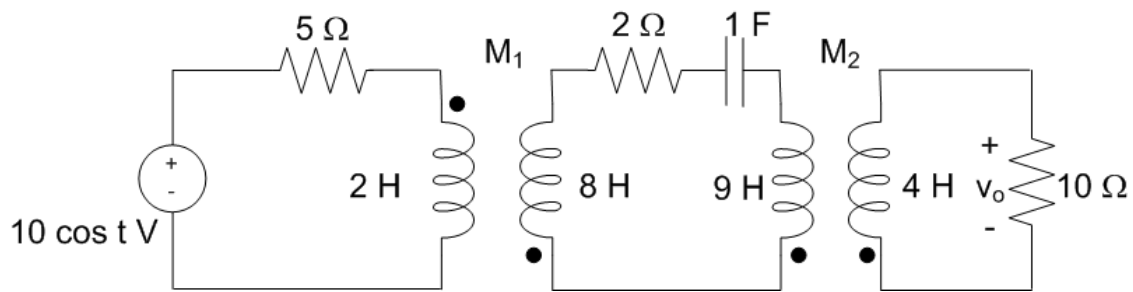


2.




- Find M_1 and M_2 for $k=0.5$ for both pairs of coupled coils.
- Transform the circuit to the frequency domain and calculate V_o .
- Calculate $v_o(t)$.


3. Solve for the voltage V_L

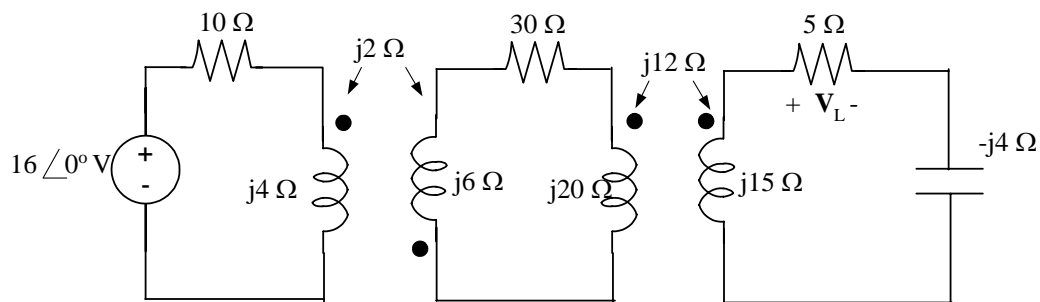

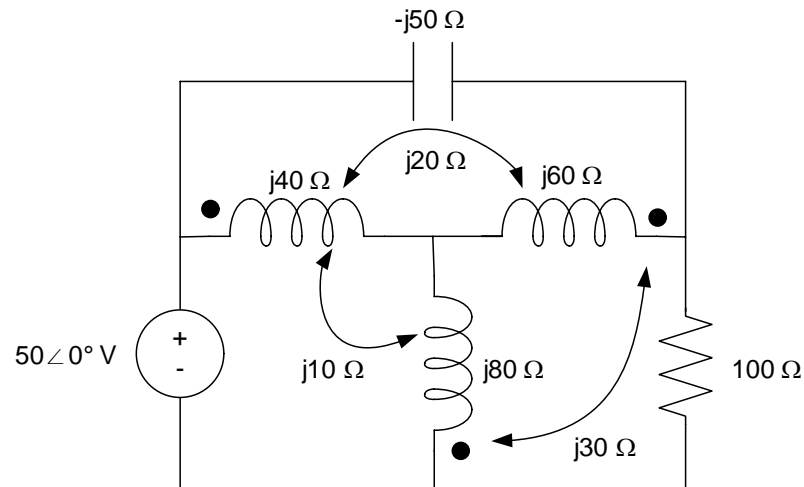
4. For the following problem, write down and simplify the mesh equations required to solve the circuit.



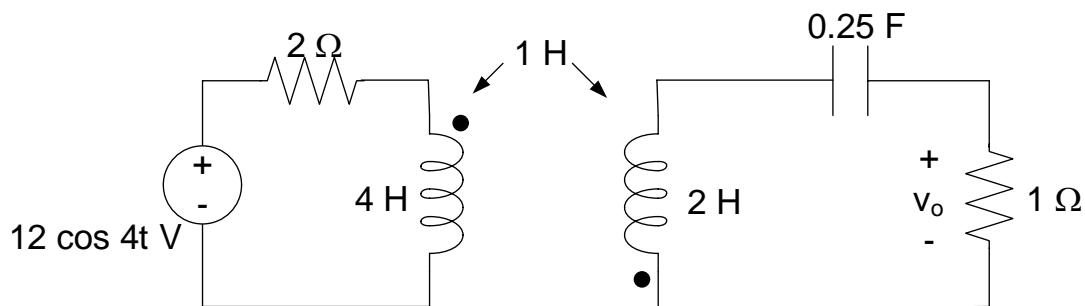5. For the given transformer, find the input impedance ($Z_1 = V_1/I_1$) reflected into the primary



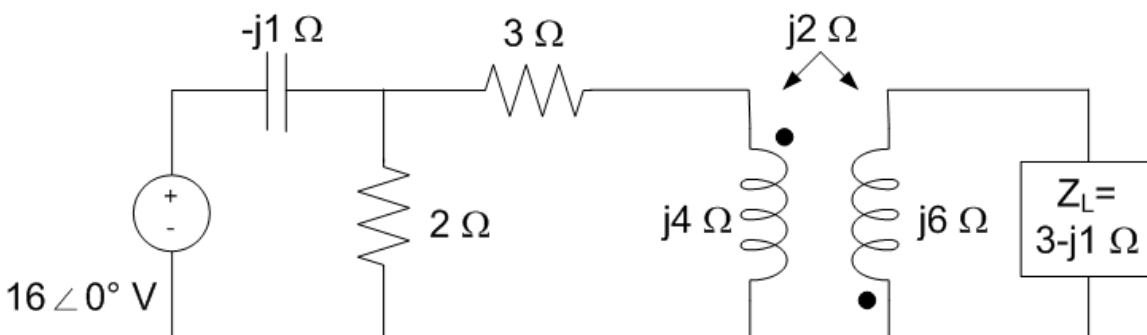6. Consider the following general transformer circuit consisting of a source in the primary and a load in the secondary.



- Find the transformer terminal ratios V_2/V_1 and I_2/I_1 . You need to label these voltages and currents. You may need to re-derive the relationships.
- Does source transfer maximum power to Z_L ? Support your answer.