

CPE/EE 422/522

# Chapter 1 - Review of Logic Design Fundamentals

Dr. Rhonda Kay Gaede

# UAH

UAH


Chapter 1

CPE/EE 422/522

 
## 1.1 Combinational Logic

---


- Combinational Logic has no control inputs. When the inputs to a combinational network change, the output changes \_\_\_\_\_.


 
### 1.1 Combinational Logic - Basic Logic Gates


 
### 1.1 Combinational Logic - Full Adder (Minterm Form)



**Truth table**

X	Y	Cin	Cout	Sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

m-form


Sum =

Cout =

Sum =

Cout =
 
## 1.1 Combinational Logic - Full Adder (Maxterm Form)



Truth table

X	Y	Cin	Cout	Sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Sum =

Sum =

Cout =

Cout =

m-form

Sum =

Cout =

## 1.2 Boolean Algebra and Algebraic Simplification

Operations with 0 and 1:

$$X + 0 = X \quad (1-5) \quad X \cdot 1 = X \quad (1-5D)$$

$$X + 1 = 1 \quad (1-6) \quad X \cdot 0 = 0 \quad (1-6D)$$

Idempotent laws:

$$X + X = X \quad (1-7) \quad X \cdot X = X \quad (1-7D)$$

Involution law:

$$(X')' = X \quad (1-8)$$

Laws of complementarity

$$X + X' = 1 \quad (1-9) \quad X \cdot X' = 0 \quad (1-9D)$$

Commutative laws:

$$X + Y = Y + X \quad (1-10) \quad XY = YX \quad (1-10D)$$

Associative laws:

$$(X + Y) + Z = X + (Y + Z) \quad (1-11) \quad (XY)Z = X(YZ) = XYZ \quad (1-11D)$$

$$= X + Y + Z$$

Distributive laws:

$$X(Y + Z) = XY + XZ \quad (1-12) \quad X + YZ = (X + Y)(X + Z) \quad (1-12D)$$

## 1.3 More Boolean Algebra and Algebraic Simplification

Simplification theorems:

$$XY + XY' = X \quad (1-13) \quad (X + Y)(X + Y') = X \quad (1-13D)$$

$$X + XY = X \quad (1-14) \quad X(X + Y) = X \quad (1-14D)$$

$$(X + Y')Y = XY \quad (1-15) \quad XY' + Y = X + Y \quad (1-15D)$$

DeMorgan's laws:

$$(X + Y + Z + \dots)' = X'Y'Z'\dots \quad (1-16) \quad (XYZ\dots)' = X' + Y' + Z' + \dots \quad (1-16D)$$

$$[f(X_1, X_2, \dots, X_n, 0, 1, +, \cdot)]' = f(X_1', X_2', \dots, X_n', 1, 0, \cdot, +) \quad (1-17)$$

Duality:

$$(X + Y + Z + \dots)^D = XYZ\dots \quad (1-18) \quad (XYZ\dots)^D = X + Y + Z + \dots \quad (1-18D)$$

$$[f(X_1, X_2, \dots, X_n, 0, 1, +, \cdot)]^D = f(X_1, X_2, \dots, X_n, 1, 0, \cdot, +) \quad (1-19)$$

Theorem for multiplying out and factoring:

$$(X + Y)(X' + Z) = XZ + X'Y \quad (1-20) \quad XY + X'Z = (X + Z)(X' + Y) \quad (1-20D)$$

Consensus theorem:

$$XY + YZ + X'Z = XY + X'Z \quad (1-21) \quad (X + Y)(Y + Z)(X' + Z) = (X + Y)(X' + Z) \quad (1-21D)$$

## 1.2 Boolean Algebra with Exclusive OR

$$X \oplus 1 = X'$$

$$X \oplus 0 = X$$

$$X \oplus X = 0$$

$$X \oplus X' = 1$$

$$X \oplus Y = Y \oplus X \quad (\text{Commutative law})$$

$$(X \oplus Y) \oplus Z = X \oplus (Y \oplus Z)$$

$$X(Y \oplus Z) = XY \oplus XZ \quad (\text{Distributive law})$$

$$(X \oplus Y)' = X \oplus Y' = X' \oplus Y = XY + X'Y'$$

### 1.3 Karnaugh Maps

- Convenient way to simplify logic functions of 3, 4, 5, (6) variables

- Four-variable K-map



- Each square

- 1 \_\_\_\_\_
- 0 \_\_\_\_\_
- d \_\_\_\_\_
- - - - -
- - - - -

- adjacent cells

	AB			
CD	00	01	11	10
00	0	4	12	8
01	1	5	13	9
11	3	7	15	11
10	2	6	14	10

### 1.3 Karnaugh Maps - Examples

  

## 1.3 Karnaugh Maps - Sum of Products

---

- Function consists of a sum of \_\_\_\_\_
- Prime implicant  
\_\_\_\_\_  
\_\_\_\_\_
- Prime implicant is \_\_\_\_\_ if it contains a 1 that is not contained in any other prime implicant


## 1.3 Karnaugh Maps - Prime Implicant Selection

---

- Two minimum forms

f =

f =

 

### 1.3 Karnaugh Maps - Selection Procedure

---


1. Choose a 1 (\_\_\_\_\_) that has not been covered yet
2. Find all \_s and \_\_s adjacent to that minterm. (Check the n adjacent squares on an n-variable map.)
3. If a single term covers the minterm and all the adjacent 1s and ds, then that term is an \_\_\_\_\_ prime implicant, so select that term.
4. Repeat steps 1, 2, 3 until all essential prime implicants have been chosen
5. Find a \_\_\_\_\_ set of prime implicants that cover the remaining 1s on the map. If there is more than one such set, choose a set with a \_\_\_\_\_

### 1.4 Designing with NAND and NOR Gates


---

- Implementation of NAND and NOR gates is easier than that of AND and OR gates (e.g., CMOS)

**NAND:**

 

**NOR:**

 


## 1.4 Designing with NAND and NOR Gates (continued)


- Any logic function can be realized using only NAND or NOR gates -
- 
- 1:
  - 0:
  - $a'$ :
  - $ab$ :
  - $a+b$ :
 
## 1.4 Designing with NAND and NOR Gates - Conversion to NOR Gates

- Start with POS (\_\_\_\_\_)
- circle 0s in K-maps
- Find network of OR and AND gates




(a) AND-OR network

 


(b) Equivalent NOR-gate network
 
### 1.4 Designing with NAND and NOR Gates - Conversion to NAND Gates


- Start with SOP (Sum of Products)
  - circle 1s in K-maps
- Find network of OR and AND gates



(a) AND\_OR network

 


(b) First step in NAND conversion

 

(c) Completed conversion
 
### 1.13 Tristate Logic and Busses

- Four kinds of tristate buffers
  - B is a control input used to enable and disable the output



B	A	C
0	0	Hi-Z
0	1	Hi-Z
1	0	0
1	1	1

(a)

B	A	C
0	0	Hi-Z
0	1	Hi-Z
1	0	1
1	1	0

(b)


B	A	C
0	0	0
0	1	1
1	0	Hi-Z
1	1	Hi-Z

(c)

B	A	C
0	0	1
0	1	0
1	0	Hi-Z
1	1	Hi-Z


(d)
 
### 1.13 Tristate Logic and Busses - Data Transfer


 
### 1.6 Flip-Flops and Latches - Sequential Networks

- Have memory (state)
  - Present state depends not only on the \_\_\_\_\_, but also on all previous inputs (history)
  - Future state depends on the \_\_\_\_\_ and \_\_\_\_\_




$$Z(t) = F(X(t), Q(t))$$

$$Q(t^+) = G(X(t), Q(t))$$

Flip-flops are commonly used as storage devices: D-FF, JK-FF, T-FF

 1.6 Flip-Flops and Latches - Clocked D Flip-Flop with Rising-edge Trigger




D	Q	Q <sup>+</sup>
0	0	0
0	1	0
1	0	1
1	1	1

**Q<sup>+</sup> = D**

Next state

The next state in response to the \_\_\_\_\_ of the clock is equal to the \_\_\_\_\_ input before the rising edge

 1.6 Flip-Flops and Latches - Clocked JK Flip-Flop




J	K	Q	Q <sup>+</sup>
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

Next state

- JK = 00 =>
- JK = 10 =>
- JK = 01 =>
- JK = 11 =>
 
### 1.6 Flip-Flops and Latches - Clocked T Flip-Flop




T	Q	Q <sup>+</sup>
0	0	0
0	1	1
1	0	1
1	1	0

Next state

T = 1 =>  
T = 0 =>

 
### 1.6 Flip-Flops and Latches - S-R Latch



S	R	Q	Q <sup>+</sup>
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	-
1	1	1	-



$$Q^+ = S + R'Q$$

 1.6 Flip-Flops and Latches -  
Transparent D Latch




G	D	Q	Q <sup>+</sup>
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

  1.6 Flip-Flops and Latches -  
Transparent D Latch




$$Q^+ = DG + G'Q + (DQ)$$

 1.7 Mealy Sequential Network Design –  
General Model of Mealy Sequential Machine




- (1) X inputs are changed to a new value
- (2) After a delay, the Z outputs and next state appear at the output of CN
- (3) The next state is clocked into the state register and the state changes

 1.7 Mealy Sequential Network Design - 8421  
BCD to Excess3 BCD Code Converter Example



X (inputs)				Z (outputs)			
t3	t2	t1	t0	t3	t2	t1	t0
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0
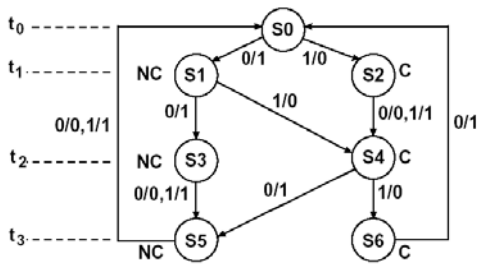
### 1.7 Mealy Sequential Network Design – State Graph and Table for Code Converter



### 1.9 Equivalent States and Reduction of State Tables – Code Converter Example

- I. States which have the same next state (NS) for a given input should be given adjacent assignments (look at the columns of the state table).
- II. States which are the next states of the same state should be given adjacent assignments (look at the rows).
- III. States which have the same output for a given input should be given adjacent assignments.

I. (1,2) (3,4) (5,6) (in the X=1 column, S<sub>1</sub> and S<sub>2</sub> both have NS S<sub>4</sub>; in the X=0 column, S<sub>3</sub> & S<sub>4</sub> have NS S<sub>5</sub>, and S<sub>5</sub> & S<sub>6</sub> have NS S<sub>0</sub>)

II. (1,2) (3,4) (5,6) (S<sub>1</sub> & S<sub>2</sub> are NS of S<sub>0</sub>; S<sub>3</sub> & S<sub>4</sub> are NS of S<sub>1</sub> and S<sub>5</sub> & S<sub>6</sub> are NS of S<sub>4</sub>)


III. (0,1,4,6) (2,3,5)

		Q1	
		0	1
Q2 Q3	00	S0	S1
	01		S2
	11	S5	S3
	10	S6	S4


1.9 Equivalent States and Reduction of State Tables - Code Converter Transition Table

PS	NS		Z		Q1Q2Q3	Q1+Q2+Q3+		Z	
	X = 0	X = 1	X = 0	X = 1		X = 0	X = 1	X = 0	X = 1
S0									
S1									
S2									
S3									
S4									
S5									
S6									

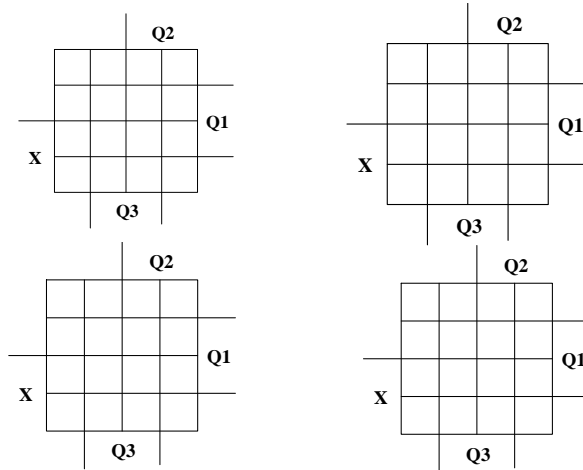1.9 Equivalent States and Reduction of State Tables - Code Converter K-maps




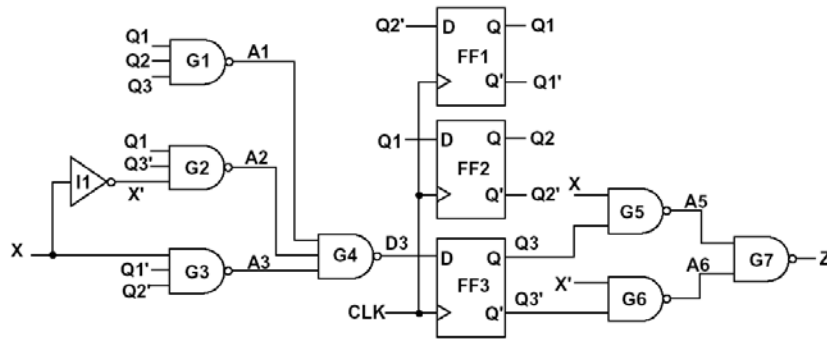
### 1.9 Equivalent States and Reduction of State Tables – Code Converter Realization



  
### 1.10 Sequential Network Timing – Code Converter

- Code converter
  - $X = 0010\_1001 \Rightarrow$
  - $Z = 1110\_0011$



 
## 1.10 Sequential Network Timing – Timing Diagram for Code Converter

Timing diagram assuming a propagation delay  
of 10 ns for each flip-flop and gate  
(State has been replaced with the state of three flip-flops)


 
## 1.11 Setup and Hold Times – D Flip-Flop

- For a real D-FF
  - D input must be stable for a certain amount of time before the active edge of clock cycle =>  $t_{su}$
  - D input must be stable for a certain amount of time after the active edge of the clock =>  $t_{th}$
- Propagation time: from the time the clock changes to the time the output changes



Manufacturers provide minimum  $t_{su}$ ,  $t_{th}$ , and maximum  $t_{plh}$ ,  $t_{phl}$

### 1.11 Setup and Hold Times – Maximum Clock Frequency Calculation

- $t_{c\ max}$  - Max propagation delay through the combinational network
- $t_{p\ max}$  - Max propagation delay from the time the clock changes to the flip-flop output changes  $\{ = \max(t_{plh}, t_{ph}) \}$
- $t_{ck}$  - Clock period

Example:

$$t_{c\ max} + t_{p\ max} \leq t_{ck} - t_{su}$$


$$t_{ck} \geq t_{c\ max} + t_{p\ max} + t_{su}$$

$$t_{p\ max} = 15\ ns, t_{su} = 5\ ns,$$

$$t_{gate} = 15\ ns$$

$$t_{ck} = 2 * 15 + 15 + 5 = 50\ ns$$

$$f_{max} = \frac{1}{50\ ns} = 20\ MHz$$

 

### 1.11 Setup and Hold Times – Hold Time Violations (from Q)



- Occurs if the change in Q that is fed back through the combinational network causes input D to change too soon after the clock edge

Hold time is satisfied if:

$$t_{p\ min} + t_{c\ min} \geq t_h$$


$t_{c\ min}$  - Min propagation delay through the combinational network

  $t_{p\ min}$  - Min propagation delay from the time the clock changes to the flip-flop output changes -  $\{ = \min(t_{plh}, t_{ph}) \}$



 
# 1.11 Setup and Hold Times – Setup Time Violations (from X)

- Occurs if the change in X that is fed back through the combinational network causes input D to change too soon after the clock edge




$$t_x \geq t_{cx\ max} + t_{su}$$

 - $t_{cx\ max}$  -Max propagation delay through the combinational network from input X (or any other input) to the flip-flop input D


 
# 1.11 Setup and Hold Times – Hold Time Violations (from X)

- Occurs if the change in X that is fed back through the combinational network causes input D to change too soon after the clock edge




Make sure that X does not change too soon after the clock.

If X changes at time  $t_y$  after the active edge, hold time is satisfied if


$$t_y \geq t_h - t_{cx\ min}$$

 - $t_{cx\ min}$  -Min propagation delay through the combinational network from input X (or any other input) to the flip-flop input D


 
## Synchronous Design


- Use a clock to synchronize the operation of all flip-flops, registers, and counters in the system
  - all changes occur immediately following the active clock edge
  - clock period must be long enough so that all changes flip-flops, registers, counters will have time to stabilize before the next active clock edge
- Typical design: Control section + Data Section



## Synchronous Design Example

- Data section //  $s = n * (n + a)$  //  $R1 = n, R2 = a // R1 = s$
- Design flowchart for SMUL operation
- Design Control section
- S0 S1 F
 


0	0	B
0	1	B - C0
1	0	B + C0
1	1	A + B

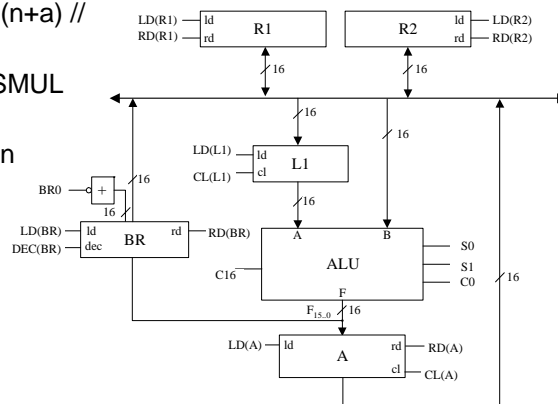
 
## Moore Sequential Networks

Outputs depend only on present state!

$$\begin{aligned}
 X &= x_1 x_2 \dots x_n \\
 Q &= Q_1 Q_2 \dots Q_k \\
 Z &= z_1 z_2 \dots z_m
 \end{aligned}$$




$$Z(t) = F(Q(t))$$

$$Q(t^+) = G(X(t), Q(t))$$

## General Model of Moore Sequential Machine

Outputs depend only on present state!

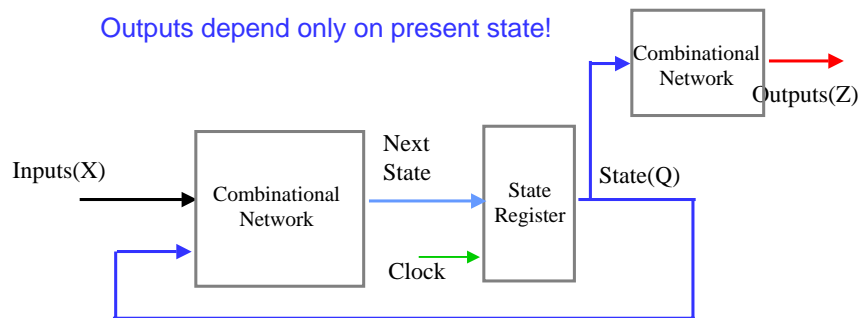

$$\begin{aligned}
 X &= x_1 x_2 \dots x_n \\
 Q &= Q_1 Q_2 \dots Q_k \\
 Z &= z_1 z_2 \dots z_m
 \end{aligned}$$

$$Q(t^+) = G(X(t), Q(t))$$

$$Z(t) = F(Q(t))$$


# Code Converter: Moore Machine

---

# Moore Machine: State Table


---

PS	NS		Z
	X=0	X=1	
S0	S1	S2	0
S1	S3	S4	1
S2	S4	S5	0
S3	S6	S7	1
S4	S7	S8	0
S5	S7	S8	1
S6	S9	S10	0
S7	S9	S10	1
S8	S10	-	0
S9	S1	S2	0
S10	S1	S2	1

 
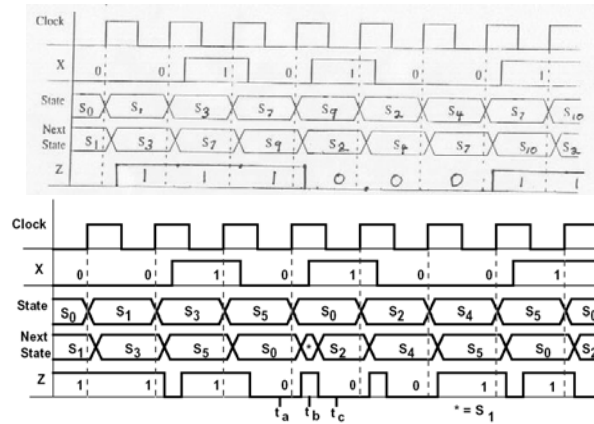
## Moore Machine Timing

- $X = 0010\_1001 \Rightarrow Z = 1110\_0011$



Moore

Mealy

## State Assignments

- I. States which have the same next state (NS) for a given input should be given adjacent assignments (look at the columns of the state table).
- II. States which are the next states of the same state should be given adjacent assignments (look at the rows).
- III. States which have the same output for a given input should be given adjacent assignments.

- Rule I: (S0, S9, S10), (S4, S5), (S6, S7)  
 Rule II: (S1, S2), (S3, S4), (S4, S5), (S6, S7), (S7, S8), (S9, S10)  
 Rule III: (S0, S2, S4, S6, S8, S9), (S1, S3, S5, S7, S10)


- S0 – 0010  
 S1 - 0111  
 ....  
 S10 - 0100

PS	NS		Z
	X=0	X=1	
S0	S1	S2	0
S1	S3	S4	1
S2	S4	S5	0
S3	S6	S7	1
S4	S7	S8	0
S5	S7	S8	1
S6	S9	S10	0
S7	S9	S10	1
S8	S10	-	0
S9	S1	S2	0
S10	S1	S2	1


### State Assignments

PS	NS		Z
	X=0	X=1	
0 0 0 0	0 1 1 1	0 1 1 0	0
0 0 0 1	----	----	-
0 0 1 0	0 1 1 1	0 1 1 0	0
0 0 1 1	----	----	-
0 1 0 0	0 1 1 1	0 1 1 0	1
0 1 0 1	----	----	-
0 1 1 0	1 0 1 1	1 0 0 1	0
0 1 1 1	1 1 1 1	1 0 1 1	1
1 0 0 0	----	----	-
1 0 0 1	1 1 1 0	1 1 0 0	1
1 0 1 0	0 0 0 0	0 1 0 0	0
1 0 1 1	1 1 1 0	1 1 0 0	0
1 1 0 0	0 1 0 0	----	0
1 1 0 1	----	----	-
1 1 1 0	0 0 0 0	0 1 0 0	1
1 1 1 1	1 0 1 0	1 1 1 0	1

### Logic Reduction

 


$$Q_A^+ = Q_D + Q_A' Q_B Q_C$$

 

$$Q_B^+ = Q_C' + Q_B' Q_D + X' Q_A' Q_D + Q_A' Q_B' + X Q_A$$


Logic Reduction

 

$Q_C^+ = X'Q_D + X'Q_A' + Q_A'Q_C' + Q_A'Q_B' + Q_BQ_D$


$Q_D^+ = X'Q_A' + Q_A'Q_BQ_C$

Logic Reduction

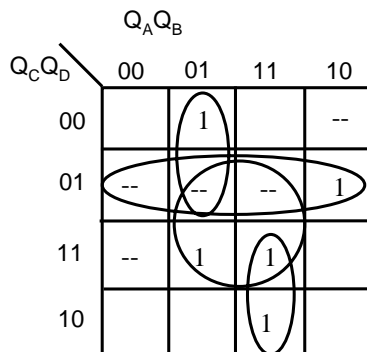


$Z = Q_A'Q_BQ_C' + Q_AQ_BQ_C + Q_C'Q_D + Q_BQ_D$

# Altera Logic Implementation

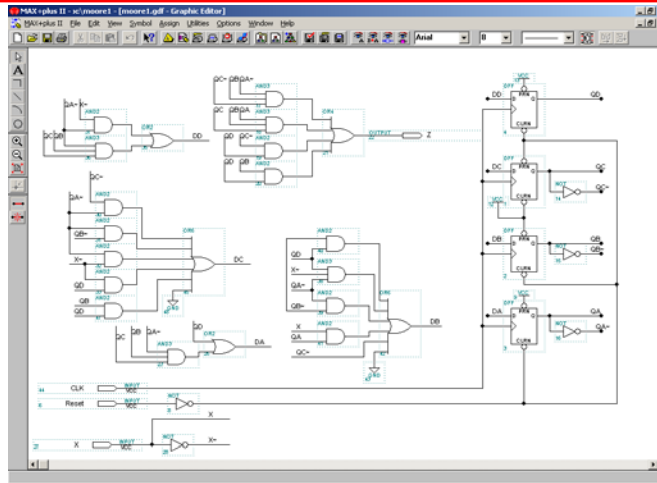


# Altera Simulation


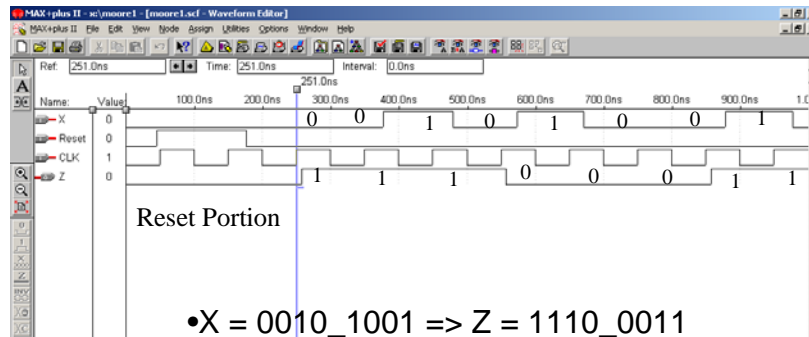

 
## Moore Machine: Another Example – NRZ to Manchester Converter


- Coding schemes for serial data transmission
  - NRZ: \_\_\_\_\_
  - NRZI: \_\_\_\_\_
    - 0 in input sequence – \_\_\_\_\_
    - 1 in input sequence – \_\_\_\_\_
  - RZ: return-to-zero
    - 0 – \_\_\_\_\_; 1 – \_\_\_\_\_
  - Manchester



## NRZ-to-Manchester Converter: Timing

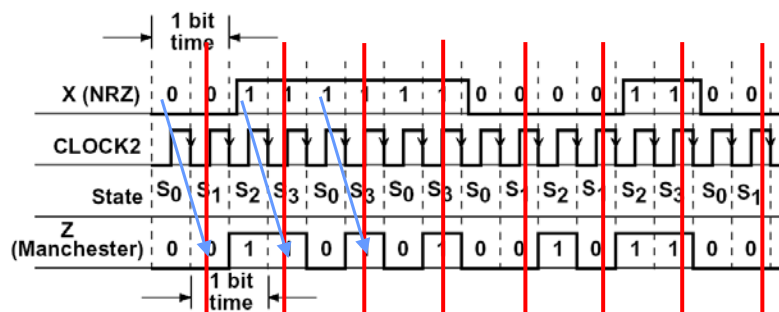 
 
## NRZ-to-Manchester: State Diagram and Table





Present State	Next State		Present Output (Z)
	X = 0	X = 1	
S <sub>0</sub>	S <sub>1</sub>	S <sub>3</sub>	0
S <sub>1</sub>	S <sub>2</sub>	-	0
S <sub>2</sub>	S <sub>1</sub>	S <sub>3</sub>	1
S <sub>3</sub>	-	S <sub>0</sub>	1

## 1.12 Synchronous Design: Control Signal Timing Issues

- Change in state of the flip-flops in control section determined by the propagation delay
- Time control signals change depend upon this FF propagation delay and combinational network delay
- Glitches and spikes may occur in the control signals due to hazards in the network
- Noise may be introduced on the control signals by changing signals in another part of the circuit
- THIS MEANS THAT THERE IS A TIME INTERVAL AFTER THE ACTIVE EDGE OF THE CLOCK WHERE THE STATE OF THE CONTROL SIGNAL IS NOT KNOWN AND MAY NOT BE STABLE
  
### 1.12 Synchronous Design: Timing Chart for System with Falling-edge Devices



(a) Falling-edge device

### 1.12 Synchronous Design: Timing Chart for System with Rising-edge Devices

 


Figure 1-35 Incorrect Design


 


Figure 1-36 Correct Design

 

## Principles of Synchronous Design

---

- Method
  - All clock inputs to flip-flops, registers, counters, etc., are driven directly from the system clock or from the clock ANDed with a control signal
- Result
  - All state changes occur immediately following the active edge of the clock signal
- Advantage
  - All switching transients, switching noise, etc., occur between the clock pulses and have no effect on system performance

## Asynchronous Design


---

- Disadvantage - More difficult
  - Problems
    - Race conditions: \_\_\_\_\_
    - Hazards
  - Special design techniques are needed to cope with races and hazards
- Advantages = Disadvantages of Synchronous Design
  - In high-speed synchronous design propagation delay in wiring is significant => clock signal must be carefully routed so that it reaches all devices at essentially same time
  - Inputs are not synchronous with the clock - need for synchronizers
  - Clock cycle is determined by the worst-case delay
 
## Equivalent States

---

- Two states are equivalent if we cannot tell them apart by observing input and output sequences



$$s_i \equiv s_j \text{ iff } Z_1 = Z_2$$

for every input sequence  $X$

Definition: Two states are equivalent  $s_i \equiv s_j$  if and only if, for every input sequence  $X$ , the output sequences  $Z_1$  and  $Z_2$  are the same.

Page 63 of 77

## Equivalent States

---

### State Equivalence Theorem

- Two states are equivalent  $S_i \equiv S_j$  if and only if for every single input  $X$ , the outputs are the same and the next states are equivalent

Page 64 of 77

## Implication Table Method

1. Construct a chart that contains a square for each pair of states.
2. Compare each pair in the state table. If the outputs associated with states  $i$  and  $j$  are different, place an  $X$  in square  $i-j$  to indicate that  $i \neq j$ .  
If outputs are the same, place the implied pairs in square  $i-j$ .  
If outputs and next states are the same (or  $i-j$  implies only itself),  $i = j$ .
3. Go through the implication table square by square. If square  $i-j$  contains the implied pair  $m-n$ , and square  $m-n$  contains  $X$ , then  $i \neq j$ , and place  $X$  in square  $i-j$ .
4. If any  $X$ s were added in step 3, repeat step 3 until no more  $X$ s are added.
5. For each square  $i-j$  that does not contain an  $X$ ,  $i = j$ .

## State Table Reduction

Present State	Next State		Present Output	
	X = 0	X = 1	X = 0	X = 1
a	c	f	0	0
b	d	e	0	0
c	h	a	0	0
d	b	g	0	0
e	e	b	0	1
f	f	a	0	1
g	c	g	0	1
h	e	f	0	0

- 1) States  $a$  and  $h$  have the same next states and outputs (when  $X=0$  and  $X=1$ )
- 2) Eliminate  $h$  from the table and replace with  $a$
- 3) States  $a$  and  $b$  have the same output  $\Rightarrow$  they are same iff  $c=d$  and  $f=e$ .  
We say  $c-d$  and  $e-f$  are implied pairs for  $a-b$ .  
To keep track of the implied pairs we make an implication chart.



### State Table Reduction

Present State	Next State		Present Output	
	X=0	X=1	X=0	X=1
a	c	f	0	0
b	d	e	0	0
c	a	g	0	0
d	b	g	0	0
e	e	b	0	1
f	f	a	0	1
g	c	g	0	1
h	e	f	0	0

- 4) Make another pass through the chart.  
E-g cell contains c-e and b-g;  
since c-e cell contains x, c!=e => e!=g (put X).
- 5) Repeat the step 4 until no additional squares are X-ed. (Put X in f-g, a-c, a-d, b-c, b-d squares).
- 6) The remaining squares indicate equivalent state pairs => a==b, c==d, e==f.
  
### Hazards in Combinational Networks

- What are hazards in Combinational Networks?
  - Unwanted switching transients at the output (glitches)
- Example
  - ABC = 111, B changes to 0
  - Assume each gate has propagation delay of 10ns



## Hazards in Combinational Networks

---

- Occur when different paths from input to output have different propagation delays
- Static 1-hazard
  - a network output momentarily go to 0 when it should remain a constant 1
- Static 0-hazard
  - a network output momentarily go to 1 when it should remain a constant 0
- Dynamic hazard
  - if an output change three or more times, when the output is supposed to change from 0 to 1 (1 to 0)

## Hazards in Combinational Circuits

---

### Why do we care about hazards?

- Combinational networks
  - don't care – the network will function correctly
- Synchronous sequential networks
  - don't care - the input signals must be stable within setup and hold time of flip-flops
- Asynchronous sequential networks
  - hazards can cause the network to enter an incorrect state
  - circuitry that generates the next-state variables must be hazard-free
- Power consumption is proportional to the number of transitions

## Detection of Static 1 and 0 Hazards

- We only consider hazards which occur when a single input variable changes
- Analysis begins by determining the *Transient Output Function*,  $F^t$ , which represents the behavior of the network under transient conditions.

The *Transient Output Function*,  $F^t$ , is determined in the same way as ordinary (steady-state) output Functions except each variable and its complement are treated as independent variables because under transient conditions these variables may assume the same values.


- Boolean manipulation of  $F^t$  involves the use of theorems that do not involve a variable and its complement on the same side of the expression.

Allowed Theorems: Associate Law, Distributive Laws, DeMorgan's Law,  $XX=X$ ,  $X+XY = X$ , etc.

## Hazards in Combinational Circuits


AB	00	01	11	10
C				
0				1
1		1	1	1

$$f = AB' + BC$$

 

AB	00	01	11	10
C				
0				1
1		1	1	1

$$f = AB' + BC + AC$$

 

To avoid hazards:  
every pair of adjacent 1s should be covered by a 1-term

## Detection of Static 1 Hazards

---

Each product term of  $F^t$  is called a 1-term.

The 1-terms of  $F^t$  are plotted on a Karnaugh map


If two 1's in adjacent squares on the map of  $F^t$  are covered by the same 1-term, changing the input to the network between the corresponding two input states cannot cause a hazard.

If two 1's in adjacent squares on the map are not covered by a single 1-term, a hazard is present.
 
## Detection of Static 1 Hazards

---

$$F^t = abc + (a+d)(a' + c') = abc + aa' + ac' + a'd + c'd$$



## Detection of Static 0 Hazards


---

- Each sum term of  $F^t$  is called a 0-term.
- The 0-terms of  $F^t$  are plotted on a Karnaugh map
- If two 0's in adjacent squares on the map of  $F^t$  are covered by the same 0-term, changing the input to the network between the corresponding two input states cannot cause a hazard.
- If two 0's in adjacent squares on the map are not covered by a single 0-term, a hazard is present.
 
## Detection of Static 0 Hazards

---

$$F^t = abc + (a+d)(a' + c') = (a+d)(a+a'+c')(b+a'+c')(c+a'+c')$$



## Design of Hazard Free Networks

---

To design a network that is free of static and dynamic hazards, the following procedure may be used:

1. Find a sum-of-products expression ( $F'$ ) for the output in which every pair of adjacent 1s is covered by a 1-term. (The sum of all prime implicants will always satisfy this condition.) A two-level AND-OR network based on this  $F'$  will be free of 1-, 0-, and dynamic hazards.
2. If a different form of network is desired, manipulate  $F'$  to the desired form by simple factoring, DeMorgan's laws, etc. Treat each  $x_i$  and  $x_i'$  as independent variables to prevent introduction of hazards.

Alternatively, you can start with a product-of-sums expression in which every pair of adjacent 0s is covered by a 0-term.