

CPE/EE 422/522
Spring 2004
Chapter 1 - Review of Logic
Design Fundamentals
Dr. Rhonda Kay Gaede

UAH


UAH

Chapter 1




CPE/EE 422/522

 1.1 Combinational Logic


¥ Combinational Logic has no control inputs. When the inputs to a combinational network change, the output changes _____.



   1.1 Combinational Logic - Basic Logic Gates



 1.1 Combinational Logic - Full Adder (Minterm Form)



m-form

Sum =

Cout =


Sum =

Cout =

Truth table

X	Y	Cin	Cout	Sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 1.1 Combinational Logic - Full Adder (Maxterm Form)



Truth table

X	Y	Cin	Cout	Sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Sum =

Sum =

Cout =

Cout =

m-form

Sum =

Cout =

1.2 Boolean Algebra and Algebraic Simplification

Operations with 0 and 1:

$$X + 0 = X \quad (1-5) \quad X \cdot 1 = X \quad (1-5D)$$

$$X + 1 = 1 \quad (1-6) \quad X \cdot 0 = 0 \quad (1-6D)$$

Idempotent laws:

$$X + X = X \quad (1-7) \quad X \cdot X = X \quad (1-7D)$$

Involution law:

$$(X')' = X \quad (1-8)$$

Laws of complementarity

$$X + X' = 1 \quad (1-9) \quad X \cdot X' = 0 \quad (1-9D)$$

Commutative laws:

$$X + Y = Y + X \quad (1-10) \quad XY = YX \quad (1-10D)$$

Associative laws:

$$(X + Y) + Z = X + (Y + Z) \quad (1-11) \quad (XY)Z = X(YZ) = XYZ \quad (1-11D)$$

$$= X + Y + Z$$

Distributive laws:

$$X(Y + Z) = XY + XZ \quad (1-12) \quad X + YZ = (X + Y)(X + Z) \quad (1-12D)$$

1.3 More Boolean Algebra and Algebraic Simplification

Simplification theorems:

$$XY + XY' = X \quad (1-13) \quad (X + Y)(X + Y') = X \quad (1-13D)$$

$$X + XY = X \quad (1-14) \quad X(X + Y) = X \quad (1-14D)$$

$$(X + Y)Y = XY \quad (1-15) \quad XY' + Y = X + Y \quad (1-15D)$$

DeMorgan's laws:

$$(X + Y + Z + \dots)' = X'Y'Z'\dots \quad (1-16) \quad (XYZ\dots)' = X' + Y' + Z' + \dots \quad (1-16D)$$

$$[f(X_1, X_2, \dots, X_n, 0, 1, +, \cdot)]' = f(X_1', X_2', \dots, X_n', 1, 0, \cdot, +) \quad (1-17)$$

Duality:

$$(X + Y + Z + \dots)^D = XYZ\dots \quad (1-18) \quad (XYZ\dots)^D = X + Y + Z + \dots \quad (1-18D)$$

$$[f(X_1, X_2, \dots, X_n, 0, 1, +, \cdot)]^D = f(X_1, X_2, \dots, X_n, 1, 0, \cdot, +) \quad (1-19)$$

Theorem for multiplying out and factoring:

$$(X + Y)(X' + Z) = XZ + X'Y \quad (1-20) \quad XY + X'Z = (X + Z)(X' + Y) \quad (1-20D)$$

Consensus theorem:

$$XY + YZ + X'Z = XY + X'Z \quad (1-21) \quad (X + Y)(Y + Z)(X' + Z) = (X + Y)(X' + Z) \quad (1-21D)$$

1.2 Boolean Algebra with Exclusive OR

$$X \oplus 1 = X'$$

$$X \oplus 0 = X$$

$$X \oplus X = 0$$

$$X \oplus X' = 1$$

$$X \oplus Y = Y \oplus X \quad (\text{Commutative law})$$

$$(X \oplus Y) \oplus Z = X \oplus (Y \oplus Z)$$

$$X(Y \oplus Z) = XY \oplus XZ \quad (\text{Distributive law})$$

$$(X \oplus Y)' = X \oplus Y' = X' \oplus Y = XY + X'Y'$$

1.3 Karnaugh Maps

¥ Convenient way to simplify logic functions of 3, 4, 5, (6) variables

¥ Four-variable K-map

— Each square

¥ 1 _____


¥ 0 _____

¥ d _____

— adjacent cells

	AB			
CD \	00	01	11	10
00	0	4	12	8
01	1	5	13	9
11	3	7	15	11
10	2	6	14	10

1.3 Karnaugh Maps - Examples

 

1.3 Karnaugh Maps - Sum of Products

¥ Function consists of a sum of _____

¥ Prime implicant


¥ Prime implicant is _____ if it contains a 1 that is not contained in any other prime implicant

1.3 Karnaugh Maps - Prime Implicant Selection

¥ Two minimum forms

f =

f =

 


1.3 Karnaugh Maps - Selection Procedure

1. Choose a 1 (minterm) that has not been covered yet
2. Find all 1s and ds adjacent to that minterm. (Check the n adjacent squares on an n-variable map.)
3. If a single term covers the minterm and all the adjacent 1s and ds, then that term is an essential prime implicant, so select that term.
4. Repeat steps 1, 2, 3 until all essential prime implicants have been chosen
5. Find a minimum set of prime implicants that cover the remaining 1s on the map. If there is more than one such set, choose a set with a minimum number of literals


1.4 Designing with NAND and NOR Gates

- ¥ Implementation of NAND and NOR gates is easier than that of AND and OR gates (e.g., CMOS)

NAND:

 

NOR:

 

1.4 Designing with NAND and NOR Gates (continued)

¥ Any logic function can be realized using only NAND or NOR gates -


-
- 1:
 - 0:
 - a :
 - ab:
 - a+b:

1.4 Designing with NAND and NOR Gates - Conversion to NOR Gates


¥ Start with POS (Product Of Sums)

- circle 0s in K-maps

¥ Find network of OR and AND gates

 

(a) AND-OR network

 


(b) Equivalent NOR-gate network

1.4 Designing with NAND and NOR Gates - Conversion to NAND Gates


¥ Start with SOP (Sum of Products)

— circle 1s in K-maps


¥ Find network of OR and AND gates

 

(a) AND_OR network

 

(b) First step in NAND conversion

 


(c) Completed conversion

Spring 2004 Slide #17

 1.13 Tristate Logic and Busses

¥ Four kinds of tristate buffers

B is a control input used to enable and disable the output



B	A	C
0	0	Hi-Z
0	1	Hi-Z
1	0	0
1	1	1

(a)

B	A	C
0	0	Hi-Z
0	1	Hi-Z
1	0	1
1	1	0

(b)

B	A	C
0	0	0
0	1	1
1	0	Hi-Z
1	1	Hi-Z

(c)

B	A	C
0	0	1
0	1	0
1	0	Hi-Z
1	1	Hi-Z

(d)

Spring 2004 Slide #18

1.13 Tristate Logic and Busses - Data Transfer

