

CPE/EE 422/522
Spring 2004
Logic Design Building Blocks

Dr. Rhonda Kay Gaede

UAH

UAH

Alternate Source


CPE/EE 422/522

Combinational Circuit Building Blocks

- ¥ Multiplexers
- ¥ Decoders
- ¥ Encoders
- ¥ Code Converters
- ¥ Comparators
- ¥ Adders/Subtractors
- ¥ Multipliers
- ¥ Shifters

Multiplexers: - 2-to-1 Multiplexer

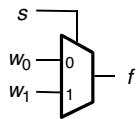
¥ Think of a multiplexer as selecting between multiple sources which may be multiple bits wide.



(a) Graphical symbol

s	f
0	w ₀
1	w ₁


(b) Truth table

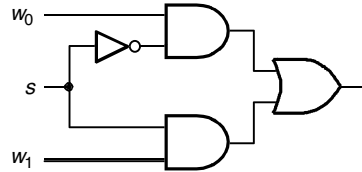

(c) Sum-of-products circuit

$$f = s'w_0 + sw_1$$


Multiplexers: - 4-to-1 Multiplexer

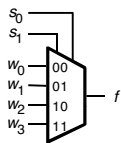

(a) Graphic symbol

s ₁	s ₀	f
0	0	w ₀
0	1	w ₁
1	0	w ₂
1	1	w ₃


(b) Truth table

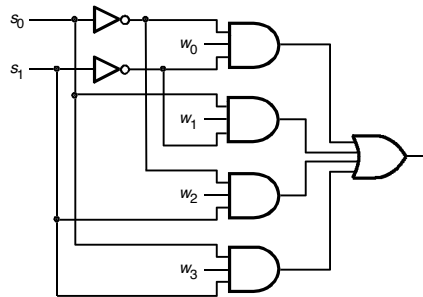

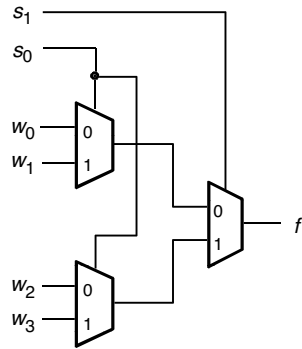
(c) Circuit

f =

Multiplexers - Building Larger Multiplexers




(a) 4-to-1 using 2-to-1

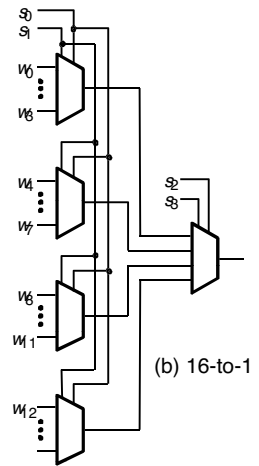

(b) 16-to-1 using 4-to-1

Synthesis of Logic Functions Using Multiplexers

w_1	w_2	f
0	0	0
0	1	1
1	0	1
1	1	0

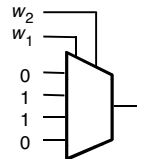


(a) Implementation using a 4-to-1 multiplexer

w_1	w_2	f
0	0	0
0	1	1
1	0	1
1	1	0

w_1	f
0	w_2
1	\bar{w}_2

(b) Modified truth table

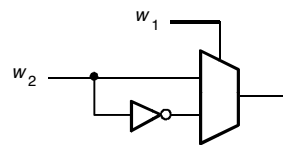


(c) Circuit

Synthesis of Logic Functions Using Multiplexers - Another Example

w_1	w_2	w_3	f
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

w_1	w_2	f
0	0	0
0	1	w_3
1	0	w_3
1	1	1

(a) Modified truth table

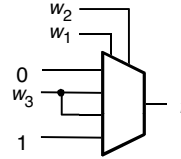


(b) Circuit

Decoders - n-to- 2^n Decoder

¥ If $En = 1$, _____

¥ If $En = 0$, _____

¥ One-hot encoded output

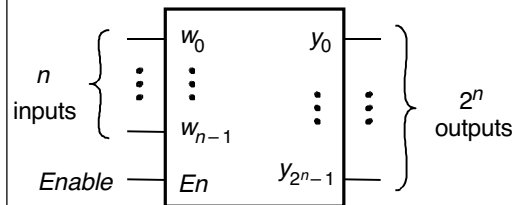

$$y_0 = w_{n-1}' \dots w_1' w_0' En$$

$$y_1 = w_{n-1}' \dots w_1' w_0 En$$

$$y_2 = w_{n-1}' \dots w_1 w_0' En$$


...

$$y_{2^n-1} = w_{n-1} \dots w_1 w_0 En$$


Decoders - 2-to-4 Decoder

En	w_1	w_0	y_0	y_1	y_2	y_3
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1
0	x	x	0	0	0	0

(a) Truth table

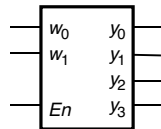

(b) Graphic symbol

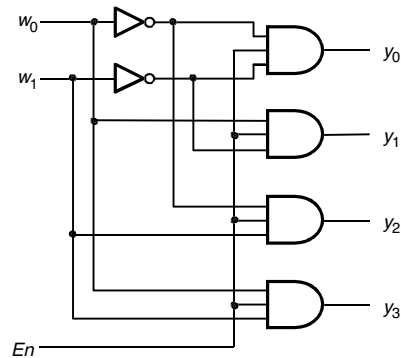

(c) Logic circuit


Encoders

¥ Opposite of decoders

¥ Binary encoders

— Exactly _____ of the input signals should have a value of 1, and outputs present the _____ that identifies which input is equal to 1


¥ Use: reduce the number of bits (transmitting and storing information)

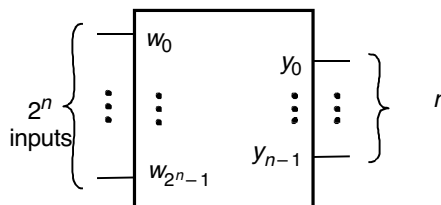

Encoders 4-to-2 Encoder

w_3	w_2	w_1	w_0	y_1	y_0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

(a) Truth table

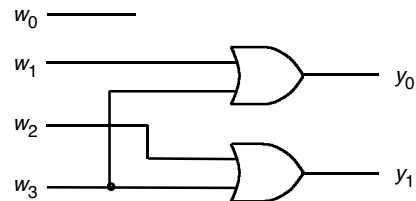

(b) Circuit

Encoders: Priority Encoders

- ¥ Each input has a priority level associated with it
- ¥ The encoder outputs indicate the active input that has the highest priority


(a) Truth table for a 4-to-2 priority encoder

w_3	w_2	w_1	w_0	y_1	y_0	z
0	0	0	0	d	d	0
0	0	0	1	0	0	1
0	0	1	x	0	1	1
0	1	x	x	1	0	1
1	x	x	x	1	1	1


Code Converters

¥ Convert from one type of input encoding to a different output encoding

—E. g., BCD-to-7-segment decoder

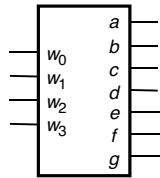

(a) Code converter

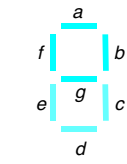

(b) 7-segment display

w_3	w_2	w_1	w_0	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1

(c) Truth table

Spring 2004 Slide #13