

CPE 628

Chapter 3 – Logic and Fault Simulation

Dr. Rhonda Kay Gaede

UAH

UAH


Chapter 3

CPE 628

3.1 Introduction

- **Simulation is the process of _____ the behavior of a circuit design _____ it is physically built.**
- _____ stage
 - _____ Simulation
- _____ development stage
 - _____ Simulation

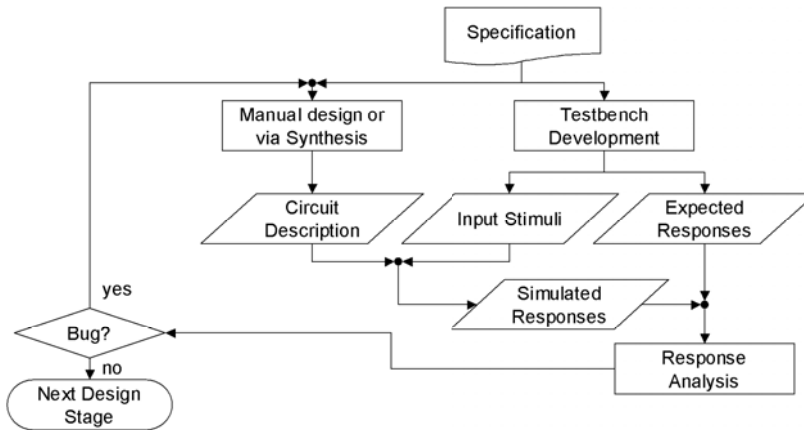
3.1 Introduction – Logic Simulation for Design Verification



3.1 Introduction – Fault Simulation for Test and Diagnosis


- Fault simulation rates the _____ of a set of test patterns in detecting _____ defects expressed in fault _____, or fault _____.
- Fault simulation helps _____ faults so that _____ can be generated.
- In test _____, fault simulation identifies _____ test patterns.

 3.2 Simulation Models – Gate-Level Network




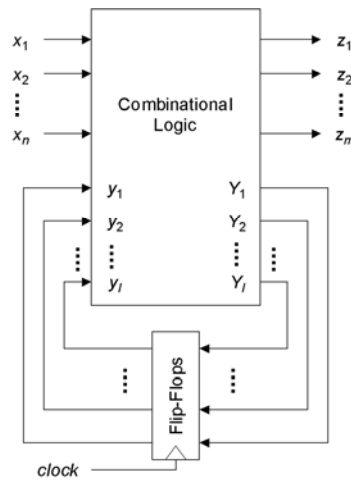3.2 Simulation Models – Sequential Circuits

- x_i : primary input (PI)
- z_i : primary output (PO)
- y_i : pseudo primary input (PPI)
- Y_i : pseudo primary output (PPO)




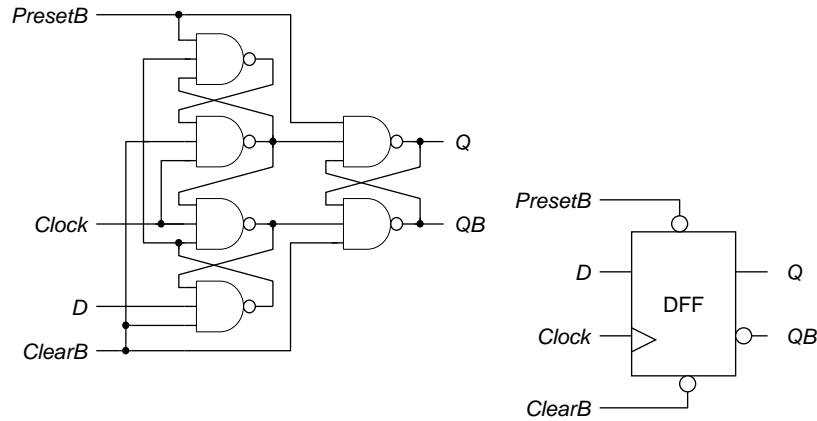3.2 Simulation Models - Sequential Circuits (Gate-Level Description)



3.2 Simulation Models - Logic Symbols (0, 1, U, Z)

AND	0	1	u	OR	0	1	u	NOT	0	1	u
0	0	0	0	0	0	1	u	1	1	0	u
1	0	1	u	1	1	1	1				
u	0	u	u	u	u	1	u				

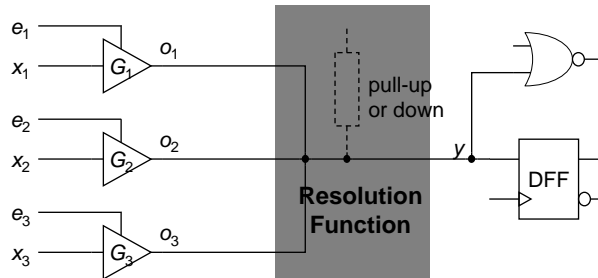

3.2 Simulation Models – Bus Conflict

- Bus conflict occurs if at least ____ drivers drive the bus to _____ binary values
- To simulate _____ behavior, one may insert a _____ for each bus wire
 - May report only the _____ of bus conflict
 - May utilize _____ logic to represent _____ logic states (including logic _____ and _____)

3.2 Simulation Model – Logical Element Evaluation

- _____ of evaluation _____ depends on
 - _____ logic symbols
 - _____ and _____ of logic elements
- Commonly used _____
 - _____
 - _____
 - _____
 - _____

3.2 Simulation Model – Logical Element Evaluation (Truth Table)


- The most _____ and easy to implement
 - For _____ logic, _____ entries for n -input logic element
 - May use the input value as _____
 - Table _____ increases _____ with the number of inputs
- Could be _____ for _____ logic
 - A _____ logic system requires a table of _____ entries for an n -input logic element

3.2 Simulation Model – Logical Element Evaluation (Input Scanning)

- The gate _____ can be determined by the _____ of inputs
 - If any of the inputs is the _____ value, the gate output is $c \oplus i$, where i is the _____ value
 - Otherwise, if any of the inputs is _____, the gate output is _____
 - Otherwise, the gate output is _____

	c	i
AND	0	0
OR	1	0
NAND	0	1
NOR	1	1

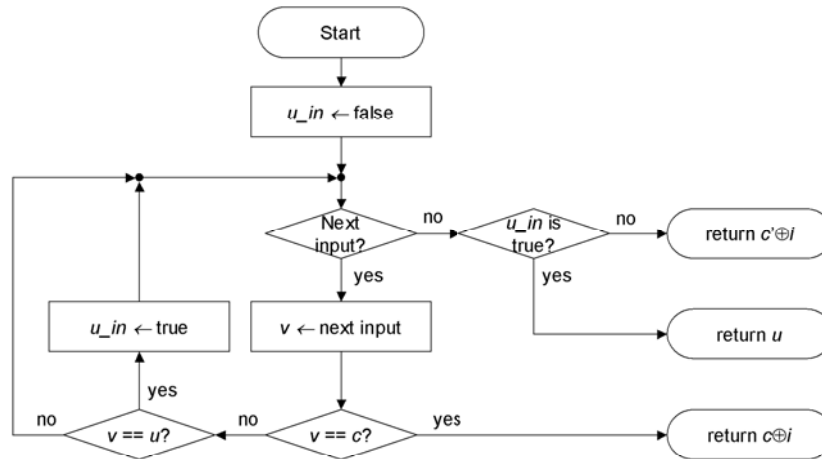3.2 Simulation Model – Logical Element Evaluation (Input Scanning)




3.2 Simulation Model – Logical Element Evaluation (Input Counting)


- Keep the counts of _____ and _____ inputs
 - *c_count*: the number of _____ inputs
 - *u_count*: the number of _____ inputs
- _____ counts during logic _____
 - Example:
One input of a _____ switches from ___ to ___
 - *c_count* --
 - *u_count* ++
- Same rules as _____ used to evaluate gate outputs

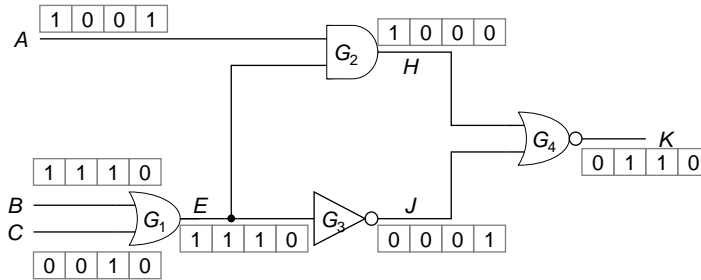3.2 Simulation Model – Logical Element Evaluation (Parallel Gate)

- Exploit the _____ in the host computer
 - A ___-bit computer can perform ___ logic operations in _____.



 3.2 Simulation Model – Timing Models (Gate Delay)




3.2 Simulation Model – Timing Models (Inertial Delay)

□ The _____ input pulse _____ necessary for the output to _____



 3.2 Simulation Model – Timing Models (Wire Delay)

- Wires are inherently _____ and _____
- It takes _____ time for a signal to _____ along a wire



3.2 Simulation Model – Timing Models (Functional Element Delay)

□ For more complicated _____ elements like _____


Input condition				Present state	Outputs		Delays (ns)		Comments
D	Clock	PresetB	ClearB	q	Q	QB	to Q	to QB	
X	X	↓	0	0	↑	↓	1.6	1.8	Asynchronous preset
X	X	0	↓	1	↓	↑	1.8	1.6	Asynchronous clear
1	↑	0	0	0	↑	↓	2	3	Q: 0→1
0	↑	0	0	1	↓	↑	3	2	Q: 1→0

3.3 Logic Simulation – Compiled-Code Simulation


• Translate the logic network into a series of _____

that model the _____ of the individual _____ and the _____ between them.

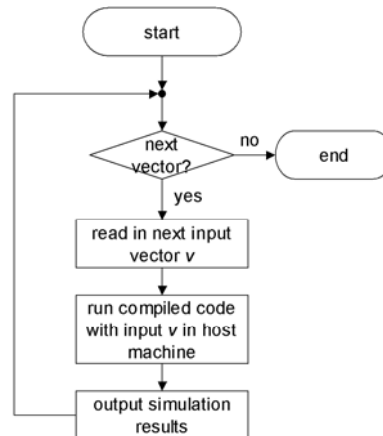
• _____ because the entire network must be executed for every _____ though only a _____ of it is _____



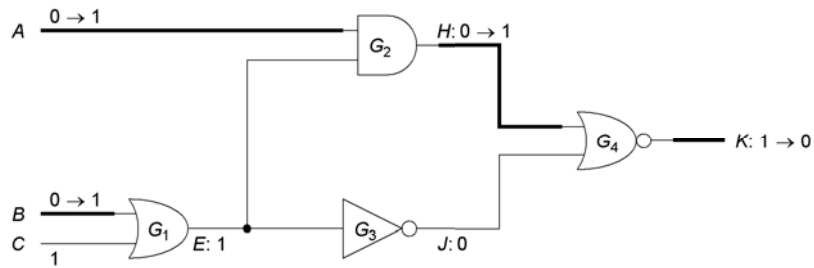3.3 Logic Simulation – Event-Driven Simulation




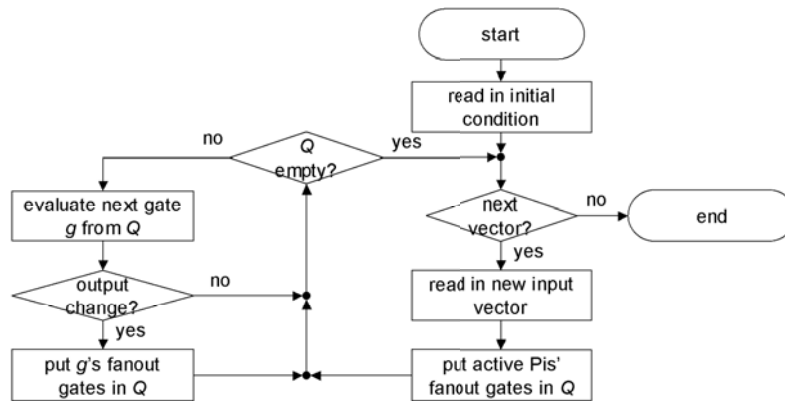3.3 Logic Simulation – Event-Driven Simulation




 3.3 Logic Simulation – Event-Driven Simulation


- Need a _____ scheduler than the _____
- Not only _____ but also _____ to evaluate



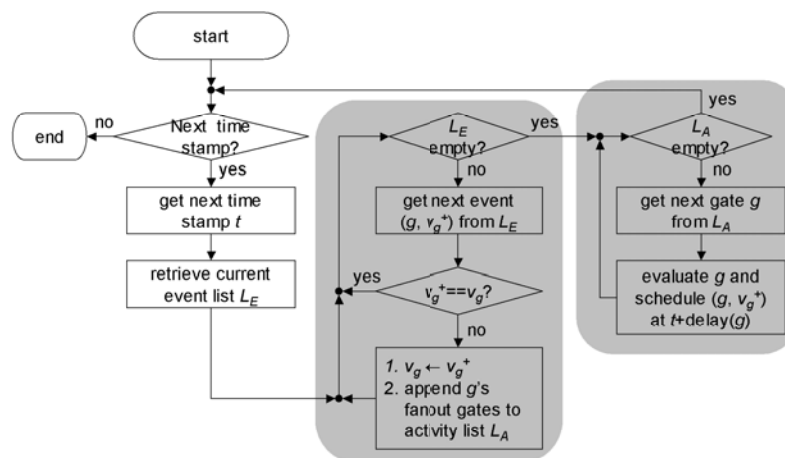3.3 Logic Simulation – Event-Driven Simulation




 3.3 Logic Simulation – Event-Driven Simulation



Delays
 G1 – 8, G2 – 8, G3 – 4,
 G4 – 6
Events
 (A, 1, 0), (C, 0, 2),
 (B, 0, 4), (A, 0, 8)

3.3 Logic Simulation – Hazards

 

Delays
 G1 – 2, G2 – 2,
 G3 – 3, G4 – 2
Events
 (A, 1, 0), (B, 1, 0),
 (C, 0, 0), (B, 0, 1)

Types: Static 0-hazard, static 1-hazard, dynamic 0-hazard, dynamic 1-hazard

3.3 Logic Simulation – Hazards (Static Hazard Detection)


Let $V^1 = v_1^1 v_2^1 \dots v_n^1$ and $V^2 = v_1^2 v_2^2 \dots v_n^2$ be consecutive

Add a $V^+ = v_1^+ v_2^+ \dots v_n^+$ according to the following rule

$$v_i^+ = \begin{cases} v_i^1 & \text{if } v_i^1 = v_i^2 \\ u & \text{if } v_i^1 \neq v_i^2 \end{cases}$$

the $V^1 V^+ V^2$ sequence using logic

 Any signal that is 1u1 or 0u0 indicates the of a hazard.



3.4 Fault Simulation – Introduction

Given

_____ , _____ , _____

Determine

_____ , _____ , _____

Task _____ to

n: Circuit _____ , _____ of logic gates


p: Number of _____

f: Number of _____

Since f is _____ to n , the overall time _____ is $O(pn^2)$

 
3.4 Fault Simulation – Serial Fault Simulation

- First, perform _____ logic simulation on the _____ circuit, obtain Good (_____) response
- For _____, perform _____ and logic simulation, obtain _____ circuit response



Pat. #	Input			Internal					Output		
	A	B	C	E	F	L	J	H	K_{good}	K_f	K_g
P1	0	1	0	1	1	1	0	0	1	0	1
P2	0	0	1	1	1	1	0	0	1	0	1
P3	1	0	0	0	0	0	1	0	0	0	1

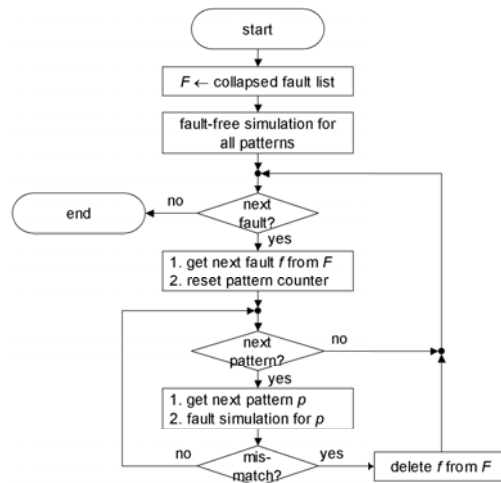3.4 Fault Simulation – Serial Fault Simulation



3.4 Fault Simulation – Serial Fault Simulation(Fault Dropping)

- _____ simulation of the _____ fault
- Example
 - Suppose we are to simulate P_1, P_2, P_3 in order
 - Fault _ is detected by ____
 - Do not simulate _ for ____, ____
- For fault _____
 - Most faults are detected after _____ test patterns have been applied
- For fault _____
 - _____ to obtain the _____ fault simulation _____


3.4 Fault Simulation – Serial Fault Simulation(Pros and Cons)

- Advantages
 - Easy to _____
 - Ability to handle a _____ of fault models
- Disadvantages
 - _____


3.4 Fault Simulation – Parallel Fault Simulation

- Exploit the _____ parallelism of _____ operations
- _____ fault simulation
 - Parallel in _____
- _____ fault simulation
 - Parallel in _____
- Assumption
 - Use _____ logic: _____ is enough to store logic _____
 - Use _____-bit wide _____ word
- Parallel simulation
 - _____ bits for faulty circuits
 - _____ bit for fault-free circuit
- Process _____ and _____ circuit in parallel using bitwise logic operations

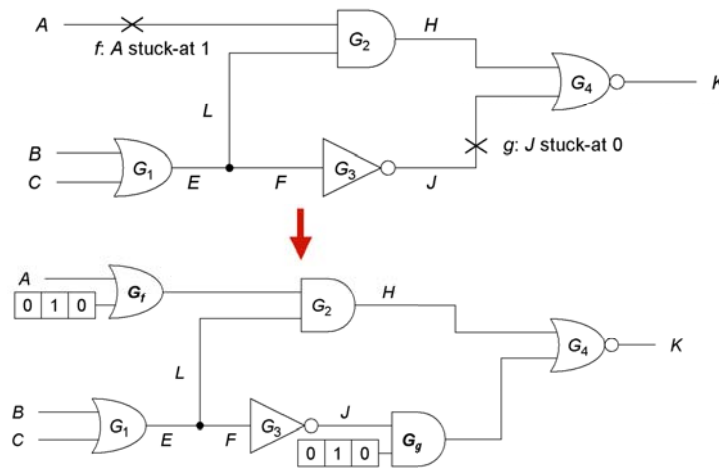3.4 Fault Simulation – Parallel Fault Simulation (Parallel Faults Fault Injection)



 3.4 Fault Simulation – Parallel Fault Simulation(Parallel Faults Example)



Pat #	Input				Internal						Output	
	A	A _f	B	C	E	F	L	J	J _f	H	K	
P ₁	FF	0	0	1	0	1	1	1	0	0	0	1
	f	0	1	1	0	1	1	1	0	0	1	0
	g	0	0	1	0	1	1	1	0	0	0	1
P ₂	FF	0	0	0	1	1	1	1	0	0	0	1
	f	0	1	0	1	1	1	1	0	0	1	0
	g	0	0	0	1	1	1	1	0	0	0	1
P ₃	FF	1	1	0	0	0	0	0	1	1	0	0
	f	1	1	0	0	0	0	0	1	1	0	0
	g	1	1	0	0	0	0	0	1	0	0	1

3.4 Fault Simulation – Parallel Fault Simulation(Parallel Faults Pros and Cons)

Advantages

- A _____ number of faults are detected by _____ when simulating the _____ of test sequence


Disadvantages

- Only applicable to the _____ or _____ models
- Faults cannot be _____ unless all _____ faults are detected


3.4 Fault Simulation – Parallel Fault Simulation(Parallel Patterns)

- Parallel pattern single fault propagation (PPSFP)
- Parallel _____
 - With a _____ data width, _____ are packed into a word and simulated for the _____ or _____ circuit
- Single _____
 - First, _____ simulation
 - Next, for each _____, fault _____ and _____ simulation

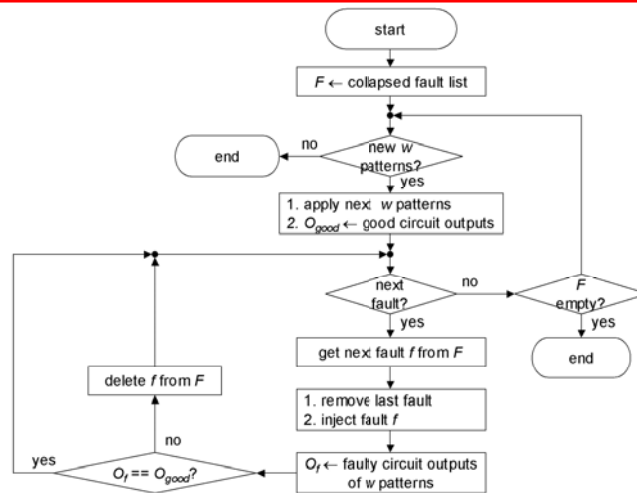3.4 Fault Simulation – Parallel Fault Simulation(Parallel Patterns Algorithm)



 3.4 Fault Simulation – Parallel Fault Simulation(Parallel Patterns Example)



	Input			Internal					Output	
		A	B	C	E	F	L	J	H	K
Fault Free	P ₁	0	1	0	1	1	1	0	0	1
	P ₂	0	0	1	1	1	1	0	0	1
	P ₃	1	0	0	0	0	0	1	0	0
f	P ₁	1	1	0	1	1	1	0	1	0
	P ₂	1	0	1	1	1	1	0	1	0
	P ₃	1	0	0	0	0	0	1	0	0
g	P ₁	0	1	0	1	1	1	0	0	1
	P ₂	0	0	1	1	1	1	0	0	1
	P ₃	1	0	0	0	0	0	0	0	1

3.4 Fault Simulation – Parallel Fault Simulation(Parallel Patterns Pros and Cons)

Advantages

- Fault is _____ as soon as _____
- Best for simulating _____ that come later, where _____ per _____ is lower

Disadvantages


- Not suitable for _____ circuits

3.4 Fault Simulation – Deductive Fault Simulation

- Based on _____ rather than _____
- Fault ___ attached to _____ denoted as ___
 - Set of _____ causing ___ to differ from its _____ value
- Fault _____
 - _____ the fault ___ of a gate _____ from those of the gate _____ based on logic reasoning

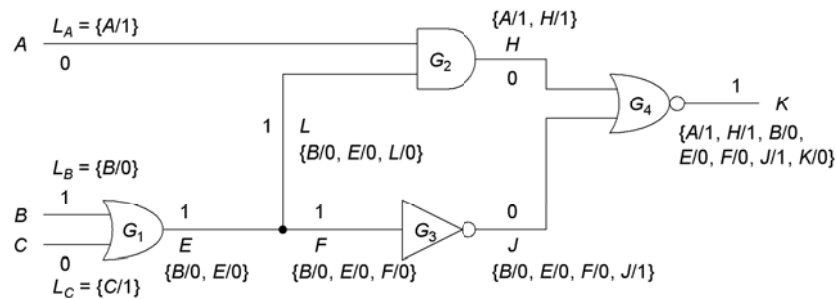3.4 Fault Simulation – Deductive Fault Simulation(Example Pattern 1)

- All gate inputs hold _____ value
- $$L_z = \left(\bigcup_{j \in I} L_j \right) \cup \{z / (c \oplus i)\}$$
- c : _____ value
 - i : _____ value
 - I : set of gate _____
 - z : gate _____
 - S : _____ holding _____ value




3.4 Fault Simulation – Deductive Fault Simulation(Example Pattern 2)

□All gate inputs hold non-controlling value

$$L_z = \left(\bigcup_{j \in I} L_j \right) \cup \{z/(c \oplus i)\}$$

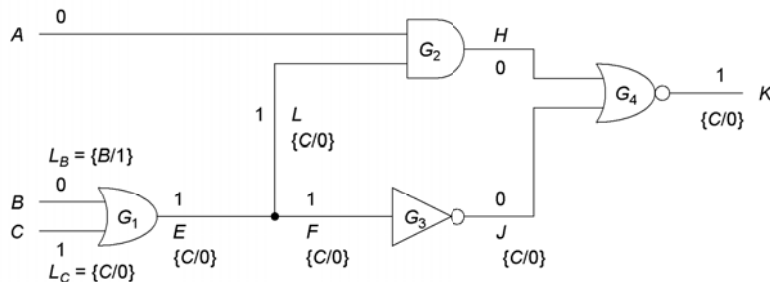c : controlling value
i : inversion value
I : set of gate inputs
z : gate output
S : inputs holding controlling value




3.4 Fault Simulation – Deductive Fault Simulation(Example Pattern 3)


□At least ___ input holds _____ value

$$L_z = \left[\left(\bigcap_{j \in S} L_j \right) - \left(\bigcup_{j \in I-S} L_j \right) \right] \cup \{z/c \oplus i'\}$$

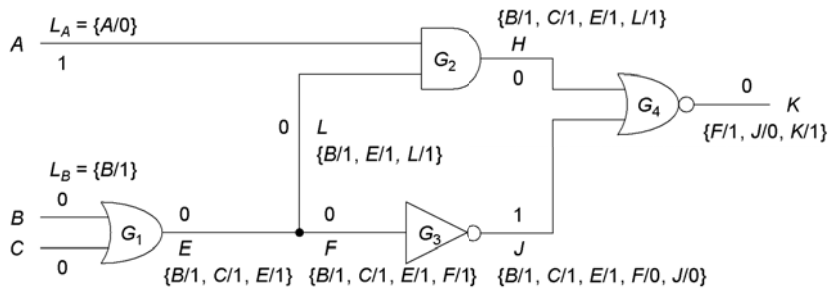c : controlling value
i : inversion value
I : set of gate inputs
z : gate output
S : inputs holding controlling value



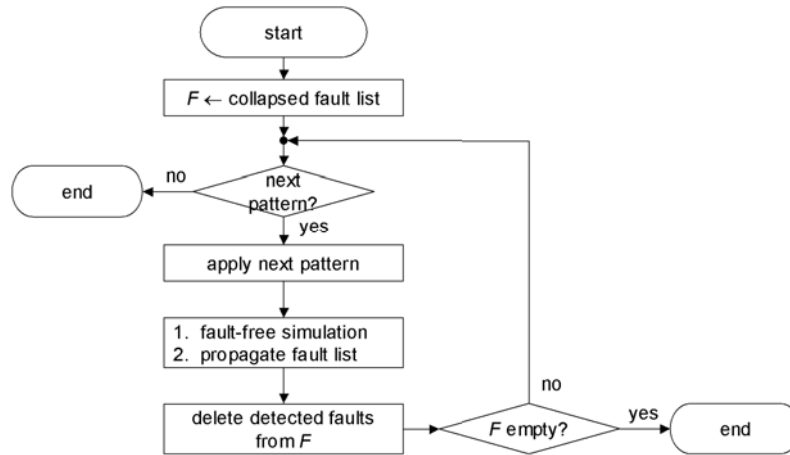3.4 Fault Simulation – Deductive Fault Simulation(Algorithm)



3.4 Fault Simulation – Deductive Fault Simulation(Pros and Cons)

□ Advantages

- Very _____
- Simulate ___ faults in ___

□ Disadvantages

- Not easy to handle _____
- Only for _____ timing model
- Potential _____ problem


3.4 Fault Simulation – Concurrent Fault Simulation

- Simulate only _____ parts of whole circuit
- _____ simulation with _____ - _____ and _____ circuits simulated altogether
- Concurrent _____ for each gate
 - Consist of a set of _____ gates
 - Fault _____ & associated gate _____ values
 - _____ only contains _____ faults
 - Fault _____ from previous stage


3.4 Fault Simulation – Concurrent Fault Simulation(Definitions)

- _____ event
 - Events that happen in _____ circuit
 - Affect both _____ gates and _____ gates
- _____ event
 - Events that occur in the _____ circuit of corresponding fault
 - Affect _____ gates
- _____
 - _____ of new bad gates
- _____
 - _____ of bad gates whose _____ are the _____ as _____ good gates

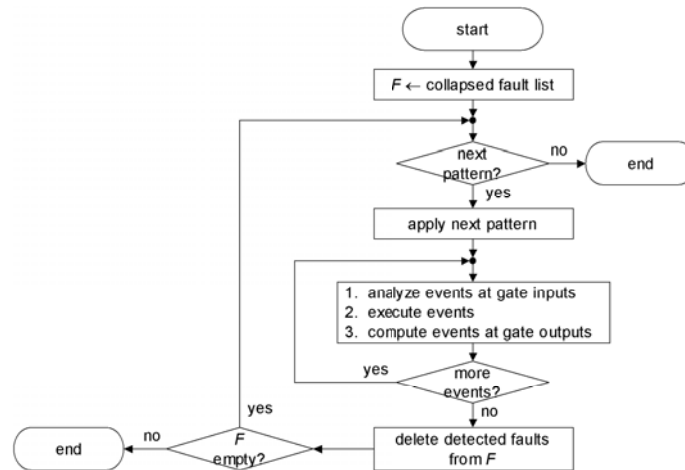
3.4 Fault Simulation – Concurrent Fault Simulation(Algorithm)



 
3.4 Fault Simulation – Concurrent Fault Simulation(Example 1)



 3.4 Fault Simulation – Concurrent Fault Simulation(Example 2)



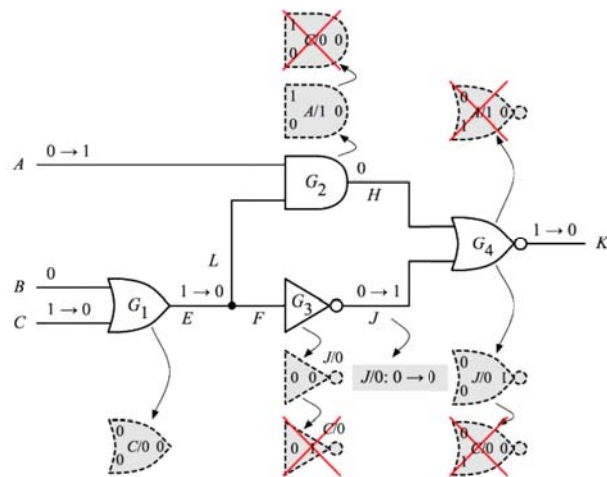3.4 Fault Simulation – Concurrent Fault Simulation(Example 3)



3.4 Fault Simulation – Concurrent Fault Simulation(Pros and Cons)

□ Advantages

- _____

□ Disadvantages

- Potential _____ problem
 - Size of the _____ _____ changes at _____
 - _____

3.4 Fault Simulation – Differential Fault Simulation

□ _____ the _____ of two techniques

- _____ fault simulation
- _____


□ Idea

- Simulate _____ every faulty circuit
- Track only _____ between _____ circuit and _____ one
- Inject _____ as _____
- Easily implemented by _____ - _____ simulator

3.4 Fault Simulation – Differential Fault Simulation(Sequence)

	P_1	P_2	...	P_i	P_{i+1}	...	P_n
<i>Good</i>	G_1	G_2	...	G_i	G_{i+1}	...	G_n
f_1	$F_{1,1}$	$F_{1,2}$...	$F_{1,i}$	$F_{1,i+1}$...	$F_{1,n}$
f_2	$F_{2,1}$	$F_{2,2}$...	$F_{2,i}$	$F_{2,i+1}$...	$F_{2,n}$
.
f_k	$F_{k,1}$	$F_{k,2}$...	$F_{k,i}$	$F_{k,i+1}$...	$F_{k,n}$
f_{k+1}	$F_{k+1,1}$	$F_{k+1,2}$...	$F_{k+1,i}$	$F_{k+1,i+1}$...	$F_{k+1,n}$
.
f_m	$F_{m,1}$	$F_{m,2}$...	$F_{m,i}$	$F_{m,i+1}$...	$F_{m,n}$

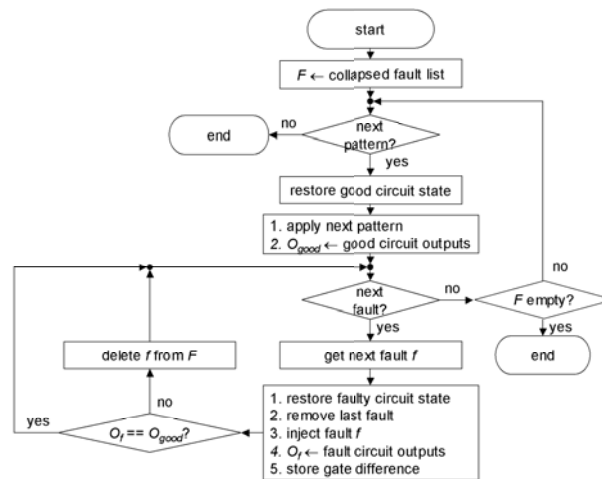3.4 Fault Simulation – Differential Fault Simulation(Algorithm)



3.4 Fault Simulation – Differential Fault Simulation(Pros and Cons)

Advantages

- Suitable for _____ fault simulation

Disadvantages

- Including _____ information makes the _____ problem explode

3.4 Fault Simulation – Fault Detection Decision

- _____ detected fault
 - Outputs of fault-free and faulty circuit are _____
 - 1/0 or 0/1
 - No unknowns, no Z
- _____ detected fault
 - Whether the fault is detected is _____
 - Example: stuck-at-0 on _____ signal of tri-state buffer
- _____ faults
 - Cause circuit to _____
 - Impossible to _____ faulty circuit _____
- _____ faults
 - Catastrophic fault effect
 - Example: stuck-at fault on _____
 - Usually counted as _____

3.4 Fault Simulation – Comparison of Techniques

- _____
 - _____ fault simulation: _____
 - _____ fault simulation: $O(n^3)$, n : num of _____
 - _____ fault simulation: $O(n^2)$
 - _____ fault is faster than _____ fault simulation
 - _____ fault simulation: even faster than _____ fault simulation and _____
- _____ usage
 - _____ fault simulation, _____ fault simulation: no problem
 - _____ fault simulation: _____ memory _____, hard to _____ size
 - _____ fault simulation: more _____ than _____ fault simulation
 - _____ fault simulation: less memory problem than _____ fault simulation

3.4 Fault Simulation – Comparison of Techniques

- _____ - _____ fault simulation to handle unknown (X) and/or high-impedance (Z)
 - _____ fault simulation, _____ fault simulation, _____ fault simulation: easy to handle
 - _____ fault simulation: difficult
- _____ and _____ modeling capability
 - _____ fault simulation: no problem
 - _____ fault simulation, deductive fault simulation: not capable
 - _____ fault simulation: capable
 - _____ fault simulation: capable

3.4 Fault Simulation – Comparison of Techniques

- _____ circuit
 - _____ fault simulation, _____ fault simulation, _____ fault simulation, _____ fault simulation: no problem
 - _____: difficult
 - _____ fault simulation: difficult due to many _____

3.4 Fault Simulation – Comparison of Techniques

- _____ and _____ fault simulation are popular for combinational (_____) circuits
- _____ fault simulation and _____ fault simulation is popular for _____ circuits
- _____ - _____ fault simulation
 - Prevent memory _____ problem
- _____ fault simulation
 - Reduce fault simulation _____

3.5 Concluding Remarks

□ Fault simulation is very important for

- _____
- _____
- _____

□ Popular techniques

- _____, _____, _____, _____, _____

□ Requirements for fault simulation

- _____ speed, _____ memory usage, modeling _____ blocks, _____ circuits